



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2010 / 2011**

COURSE NAME : BASIC ELECTRIC AND ELECTRONICS

COURSE CODE : DKE 3273

PROGRAMME : 3 DDT / DDM

EXAMINATION DATE : APRIL / MAY 2011

DURATION : 3 HOUR

INSTRUCTION : ANSWER FIVE (5) QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF TEN (10) PAGES

Q1 By referring to Figure Q1, show all the calculation to find the value for :

- (a) Total resistance R_T (4 marks)
- (b) The voltage drop across resistance R_2 (V_{R2}), resistance R_3 (V_{R3}), resistance R_4 (V_{R4}) and resistance R_6 (V_{R6}) (8 marks)
- (c) The current flow through resistance R_2 (I_{R2}), resistance R_3 (I_{R3}), resistance R_4 (I_{R4}) and resistance R_6 (I_{R6}) (8 marks)

Q2 (a) Determine the amount of charge, Q , stored by a capacitor if

- (i) $C = 10\mu\text{F}$ and $V = 5\text{V}$
 (ii) $C = 680\text{ pF}$ and $V = 200\text{V}$
 (iii) $C = 0.22\ \mu\text{F}$ and $V = 50\text{ V}$

(6 marks)

(b) Determine the voltage, V , across a capacitor if

- (i) $Q = 2.5\ \mu\text{C}$ and $C = 0.01\ \mu\text{F}$
 (ii) $Q = 10\ \text{mC}$ and $C = 1000\ \mu\text{F}$
 (iii) $Q = 188\ \text{nC}$ and $C = 0.0047\ \mu\text{F}$

(6 marks)

(c) Calculate the capacitance, C , of a capacitor for each set of physical characteristics listed below :

- (i) $A = 0.1\ \text{cm}^2$, $d = 0.005\ \text{cm}$, $K_E = 1$
 (ii) $A = 1\ \text{cm}^2$, $d = 5 \times 10^{-6}\ \text{cm}$, $K_E = 6$

(8 marks)

Q3 By referring to Figure Q3, assume a charging current of $2.4\ \text{mA}$ flows for $1\ \text{ms}$, determine :

- (a) Total equivalent capacitance, C_{EQ} (4 marks)
- (b) The charge stored in each capacitor C_1 (Q_{C1}), C_2 (Q_{C2}) and C_3 (Q_{C3}) (6 marks)
- (c) The voltage across each capacitor C_1 (V_{C1}), C_2 (V_{C2}) and C_3 (V_{C3}) (6 marks)
- (d) The total charge, Q_T stored by the equivalent capacitor, C_{EQ} (4 marks)

- Q4** (a) Refer to Figure Q4(a), two coils connected in series have a self-inductance of $L_1 = 20\text{mH}$ and $L_2 = 60\text{mH}$ respectively. The total inductance of the combination was found to be $L_T = 100\text{mH}$. Determine the amount of mutual inductance (L_T) that exists between the two coils assuming that they are aiding each other.

(10 marks)

- (b) Refer to Figure Q4(b), calculate the equivalent inductance, L_{EQ} of the following inductive circuit, if given $L_1 = 20\text{mH}$, $L_2 = 40\text{mH}$, $L_3 = 30\text{mH}$, $L_4 = 20\text{mH}$, $L_5 = 50\text{mH}$, $L_6 = 40\text{mH}$ and $L_7 = 100\text{mH}$

(10 marks)

- Q5** Refer to Figure Q5, calculate;

- (a) The secondary voltage , V_S (4 marks)
- (b) The secondary current, I_S (4 marks)
- (c) The secondary power, P_S (4 marks)
- (d) The primary power, P_P (4 marks)
- (e) The primary current, I_P (4 marks)

- Q6** Refer to Figure Q6, determine;

- (a) The total equivalent resistance, R_{EQ} (4 marks)
- (b) The branch currents, I_1 and I_2 (4 marks)
- (c) The total current, I_T (4 marks)
- (d) The power dissipated at each resistors, P_1 and P_2 (4 marks)
- (e) The total power supplied by the source, P_T (4 marks)

- Q7** (a) Figure Q7(a) shows a transistor biasing circuit do the following :
- (i) Calculate the collector saturation current ($I_{C(sat)}$) (1 mark)
 - (ii) Calculate the collector–emitter cut-off voltage ($V_{CE(off)}$) (1 mark)
 - (iii) Calculate the collector current at the Q-point (I_{CQ}) (3 marks)
 - (iv) Calculate the voltage at the Q-point (V_{CEQ}) (1 mark)
 - (v) Draw the DC load line for the transistor circuit (4 marks)
- (b) Figure Q7(b) shows a n-channel JFET circuit. What is the value of R_S ? (2 marks)
- (c) Referring to Figure Q7(b), for the values of R_S calculated in question Q7(b), determine:
- (i) gate voltage (V_G) (2 marks)
 - (ii) source voltage (V_S) (2 marks)
 - (iii) gate-source voltage (V_{GS}) (2 marks)
 - (iv) drain voltage (V_D) (2 marks)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2010/2011
COURSE : BASIC ELECTRIC AND
ELECTRONICS

PROGRAMME : 3 DDT / DDM
COURSE CODE : DKE3273

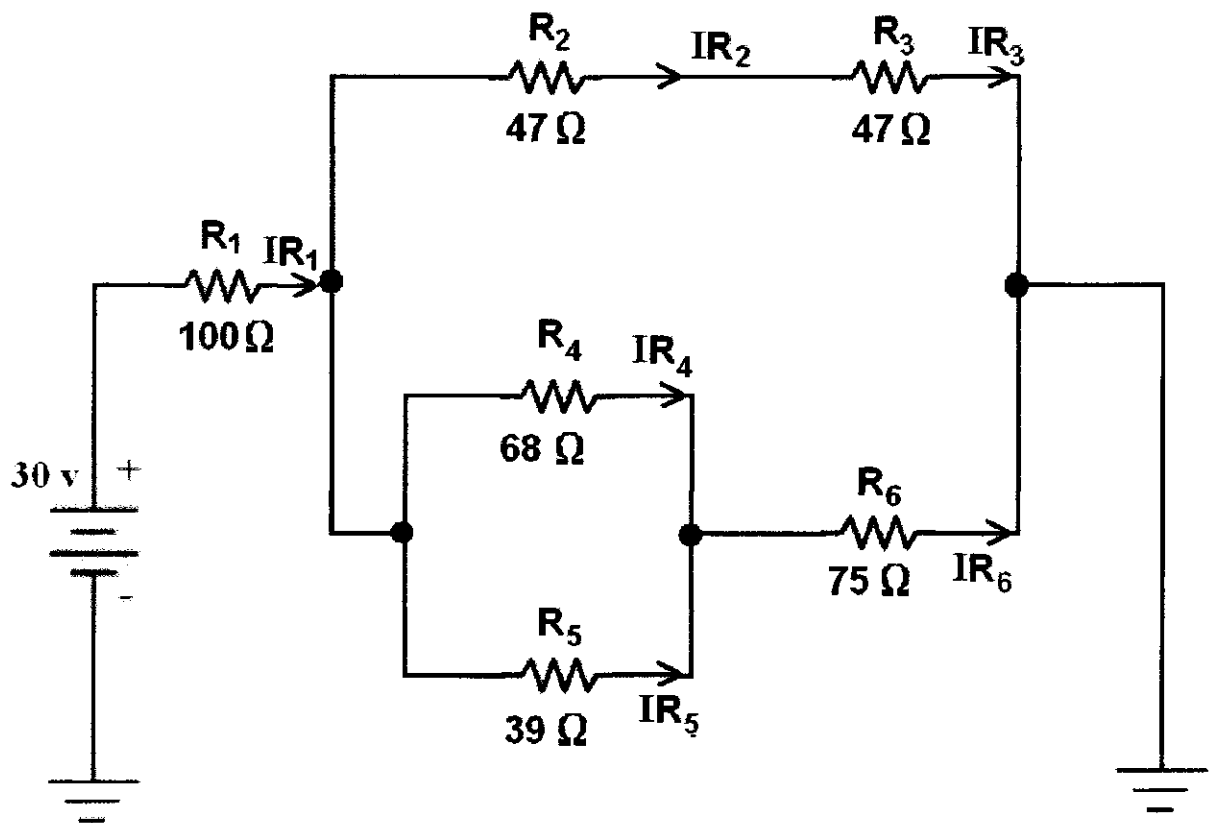


Figure Q1

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2010/2011
COURSE : BASIC ELECTRIC AND
ELECTRONICS

PROGRAMME : 3 DDT / DDM
COURSE CODE : DKE3273

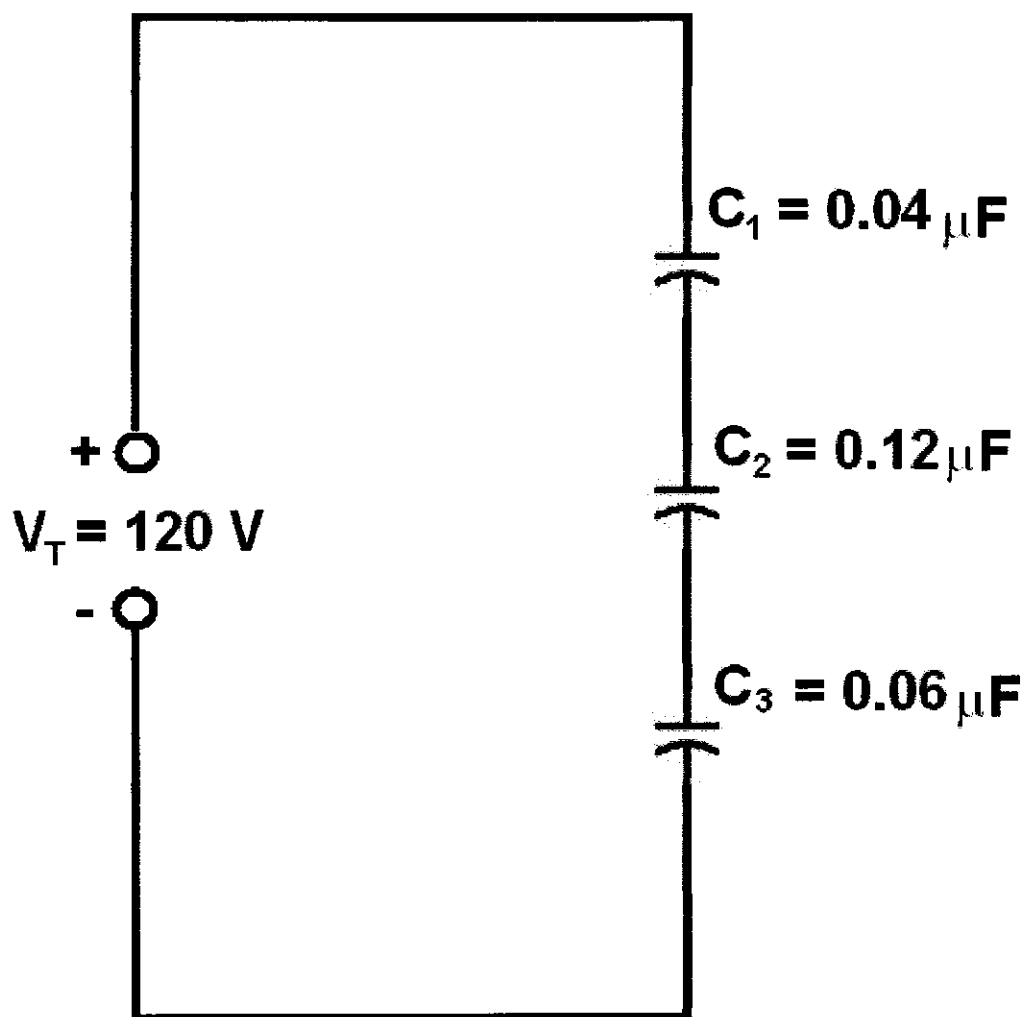


Figure Q3

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2010/2011
 COURSE : BASIC ELECTRIC AND ELECTRONICS

PROGRAMME : 3 DDT / DDM
 COURSE CODE : DKE3273

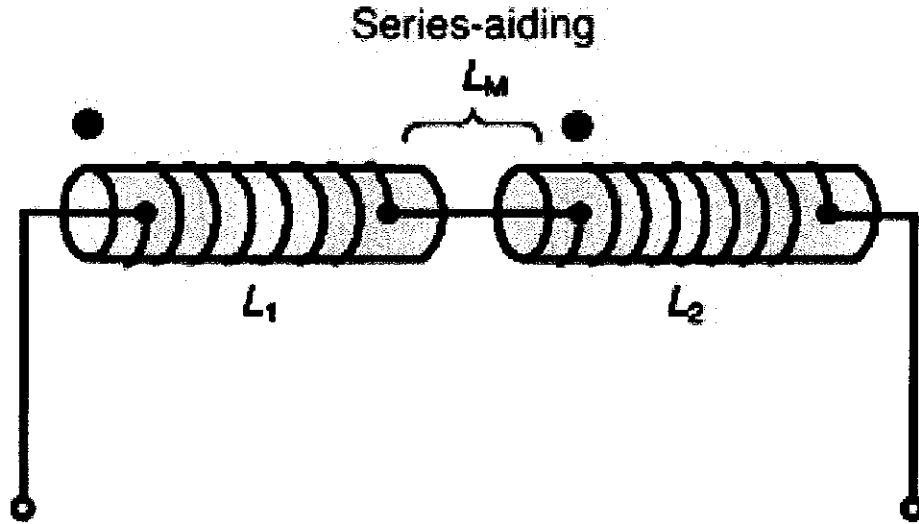


Figure Q4 (a)

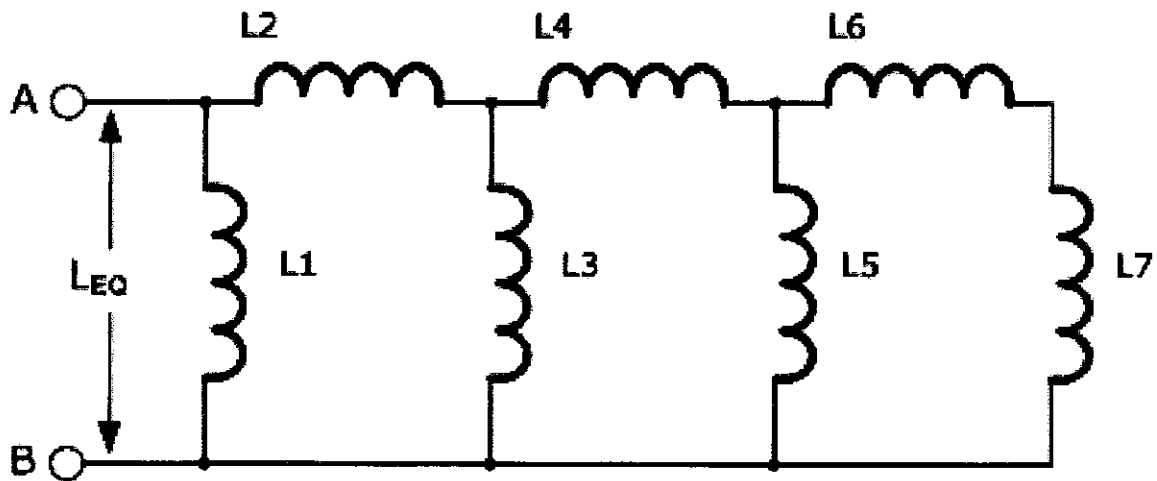


Figure Q4 (b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2010/2011
COURSE : BASIC ELECTRIC AND
ELECTRONICS

PROGRAMME : 3 DDT / DDM
COURSE CODE : DKE3273

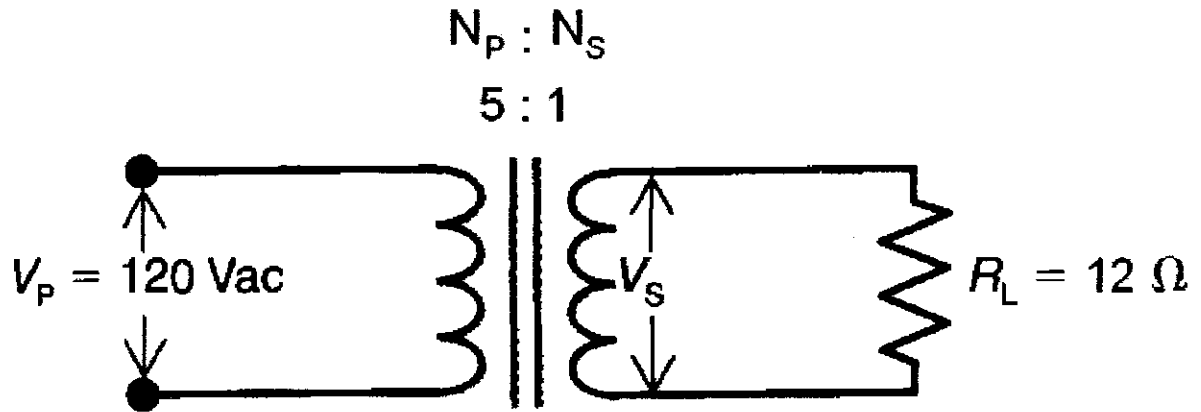


Figure Q5

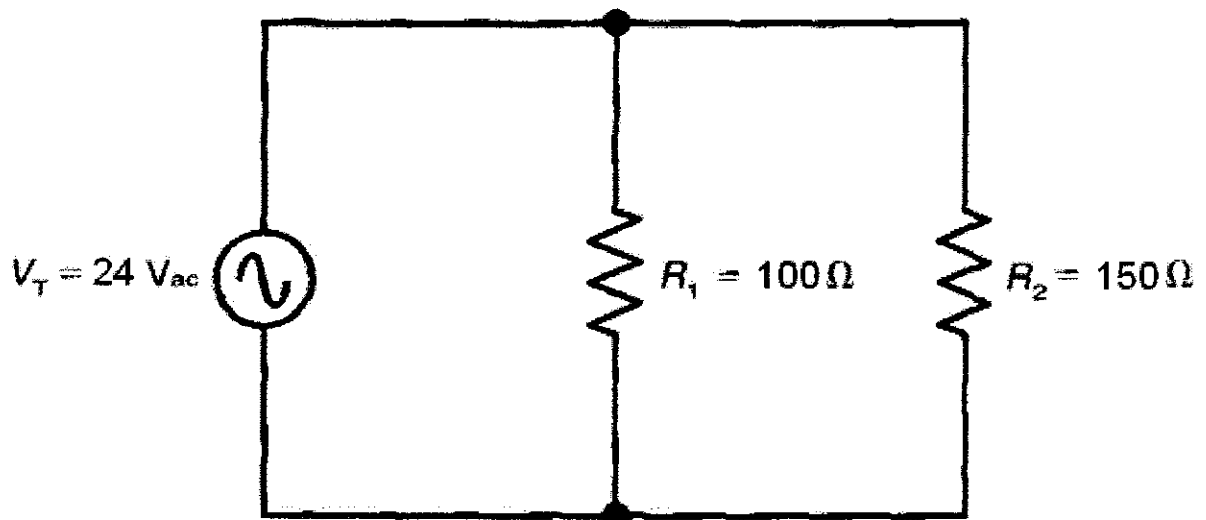


Figure Q6

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2010/2011
 COURSE : BASIC ELECTRIC AND ELECTRONICS

PROGRAMME : 3 DDT / DDM
 COURSE CODE : DKE3273

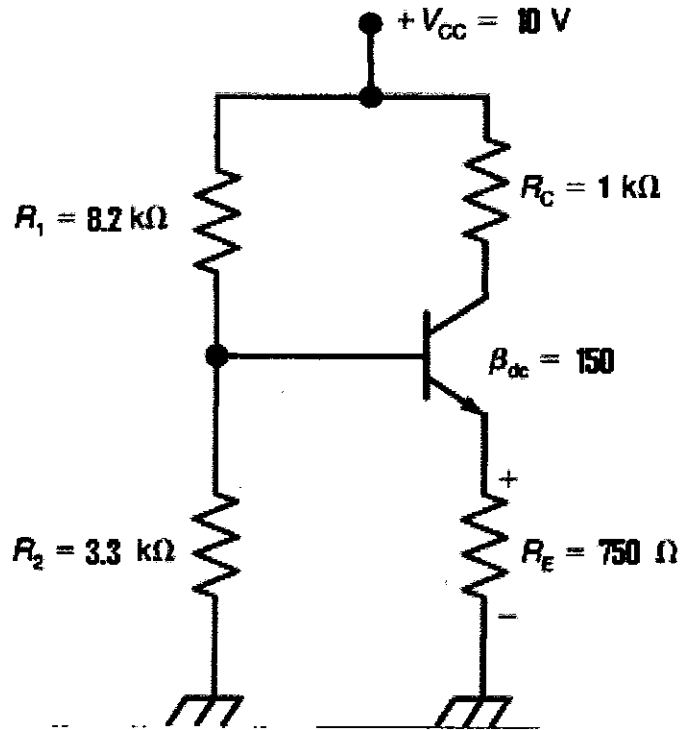


Figure Q7 (a)

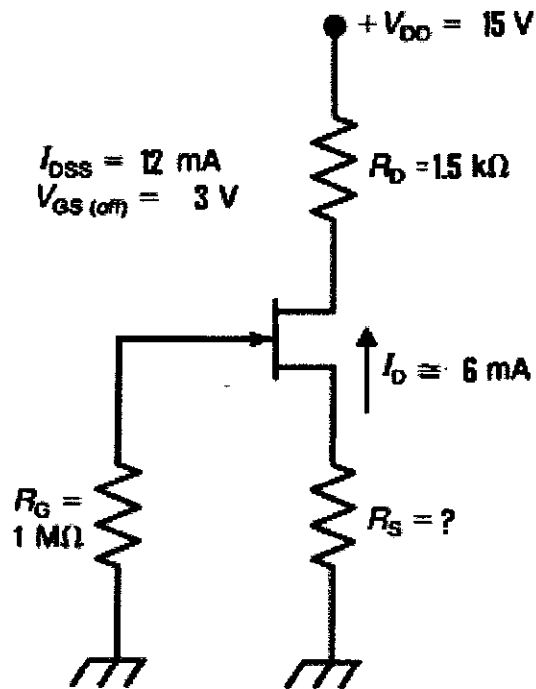














Figure Q7 (b)

References :

Band Color	Digit	Multiplier	Tolerance
Black	 0	1	---
Brown	 1	10	±1%
Red	 2	100	±2%
Orange	 3	1,000	±3%
Yellow	 4	10,000	±4%
Green	 5	100,000	---
Blue	 6	1,000,000	---
Violet	 7	10,000,000	---
Gray	 8	100,000,000	---
White	 9	---	---
Gold	 ---	0.1	±5%
Silver	 ---	0.01	±10%
None	---	---	±20%