

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2017/2018**

COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY

COURSE CODE : BNJ 10903

PROGRAMME CODE : BNG/BNH/BNK/BNL/BNM

EXAMINATION DATE : JUNE / JULY 2018

DURATION : 3 HOURS

INSTRUCTION : ANSWER ALL QUESTIONS

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

- Q1** (a) Analyse the circuit shown in **Figure Q1(a)** and determine  $V_x$ . (5 marks)
- (b) Determine the equivalent resistance of the circuit shown in **Figure Q1(b)**. Hence calculate  $I_x$  and power dissipated in any of the  $5\ \Omega$  resistor. (8 marks)
- (c) Analyse circuit in **Figure Q1(c)** and determine the voltage  $v_o$  using either Mesh or Superposition analysis. (7 marks)

- Q2** (a) The voltage across a  $4\ \mu\text{F}$  capacitor is

$$v(t) = \begin{cases} 5000t, & 0 < t < 2\ \text{ms} \\ 20 - 5000t, & 2 < t < 6\ \text{ms} \\ -40 + 5000t, & 6 < t < 8\ \text{ms} \end{cases},$$

as shown in **Figure Q2(a)**.

- (i) Determine and plot the capacitor current. (7 marks)
- (ii) Calculate the capacitor energy and power at  $t = 3\ \text{ms}$ . (3 marks)
- (b) An inductor is an electrical component designed to store energy in its magnetic field.
- (i) Give an example of inductor application in an automobile. (1 mark)
- (ii) Name and describe the example of the devices that uses the phenomenon of mutual induction. (2 marks)
- (c) Consider the circuit in **Figure Q2(c)**. Under DC conditions, calculate
- (i)  $i$ ,  $v_c$ , and  $i_L$ . (4 marks)
- (ii) The energy stored in the capacitor and inductor. (3 marks)

**TERBUKA**

- Q3** (a) Determine the reluctance of a piece of Mu-metal of length 150 mm when the relative permeability is 4000. Calculate the absolute permeability of the Mu-metal. (4 marks)

- (b) A coil of 300 turns is wound uniformly on a ring of non-magnetic material. The ring has a mean circumference of 40 cm and a uniform cross-sectional area of 4 cm<sup>2</sup>. If the current in the coil is 5 A, calculate:
- (i) the magnetic field strength
  - (ii) the flux density
  - (iii) the total magnetic flux in the ring
- (6 marks)
- (c) A transformer can change electrical energy of a given voltage into electrical energy at a different voltage level. It consists of two coils arranged in such a way that the magnetic field surrounding one coil cuts through the other coil.
- (i) Sketch the basic transformer structure. Identify and label the core, primary winding and secondary winding.
- (4 marks)
- (ii) An ideal transformer is rated at 2400/120 V, 9.6 kVa, and has 50 turns on the secondary side. Calculate the turn ratio, the number of turns on the primary side and the current rating for the primary and secondary winding.
- (6 marks)

**Q4** (a) From sinusoidal voltage equation

$$v(t) = 2 \sin(50t + 1.57) \text{ V ,}$$

determine :

- (i) the peak voltage
  - (ii) the frequency
  - (iii) the period
  - (iv) the rms value
  - (v) phase angle
- (5 marks)
- (b) Determine the input impedance of the circuit shown in **Figure Q4(b)**. Hence calculate  $I_x$ .
- (7 marks)
- (c) Derive the nodal equations of the network shown in **Figure Q4(c)**.
- (6 marks)
- (d) State **TWO (2)** characteristics of AC system.
- (2 marks)

**TERBUKA**

**Q5** (a) Describe the function of the electronic devices below:

- (i) Diode
- (ii) Sensor
- (iii) Power inverter

(6 marks)

(b) In digital system, different gates are connected to perform different functions. Such circuits are called combinational logic circuit. **Figure Q5(b)** shows a combinational logic circuit.

(i) Obtain the complete Boolean expression for  $Z$ .

(6 marks)

(ii) Using the Boolean expression for  $Z$ , build a truth table for the circuit and evaluate  $Z$  for each input combination.

(8 marks)

- **END OF QUESTIONS** -

**TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION: SEM II / 2017/2018  
COURSE NAME : ELECTRICAL AND  
ELECTRONIC TECHNOLOGY

PROGRAMME CODE: BNG/BNH/BNK/BNL/BNM  
COURSE CODE : BNJ10903

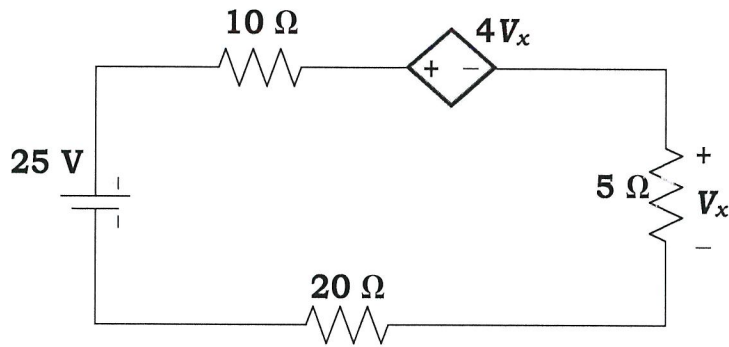


Figure Q1(a)

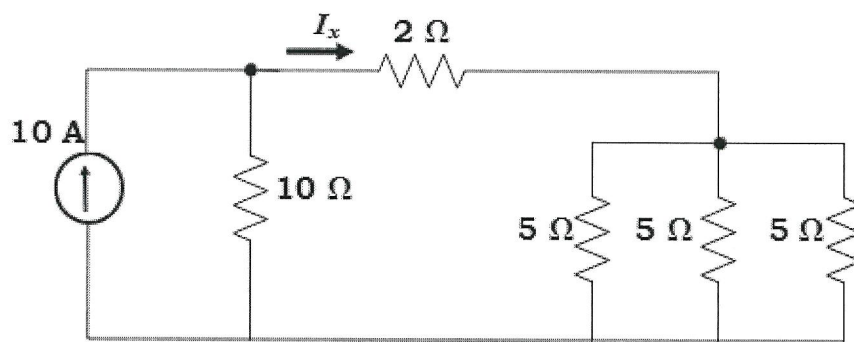


Figure Q1(b)

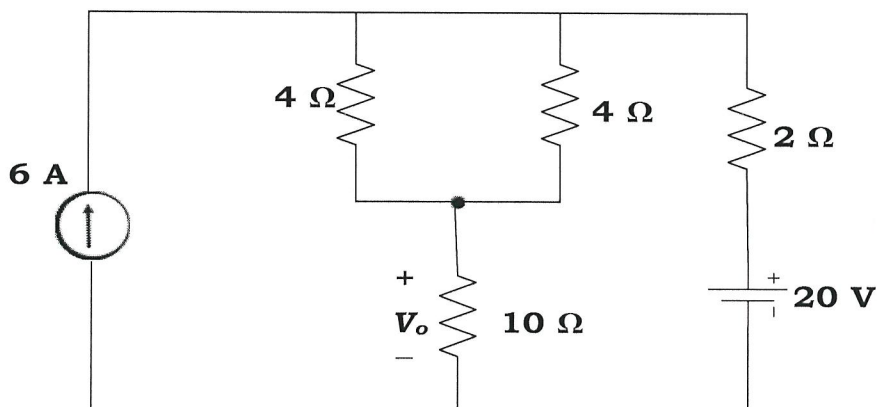


Figure Q1(c)

**TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION: SEM II / 2017/2018  
COURSE NAME : ELECTRICAL AND  
ELECTRONIC TECHNOLOGY

PROGRAMME CODE: BNG/BNH/BNK/BNL/BNM  
COURSE CODE : BNJ10903

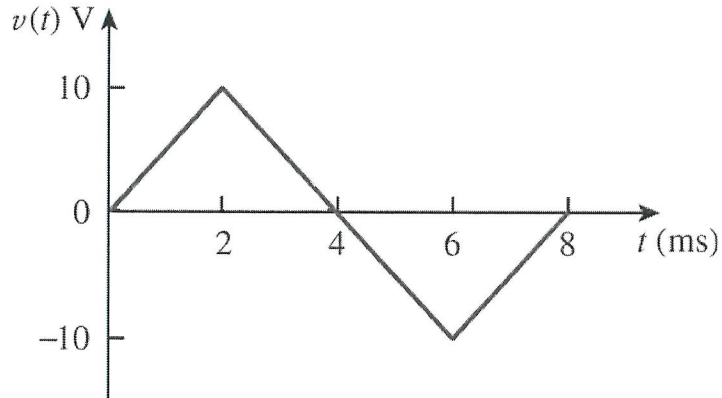


Figure Q2(a)

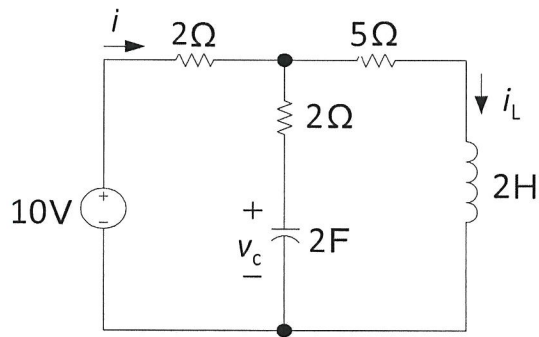


Figure Q2(c)

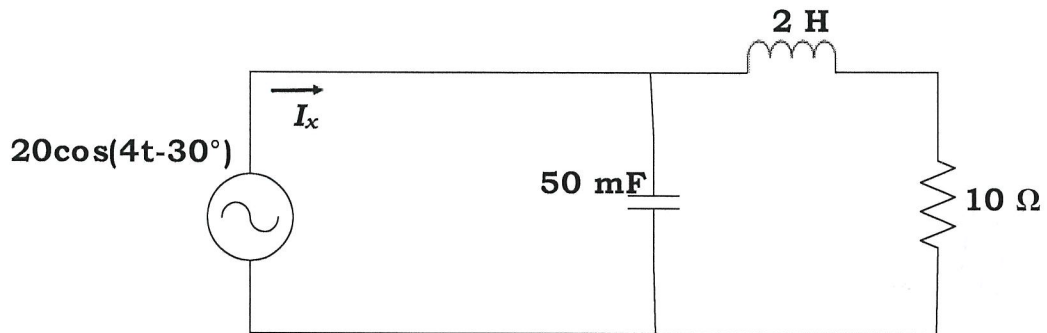


Figure Q4(b)

TERBUKA



FINAL EXAMINATION

SEMESTER / SESSION: SEM II / 2017/2018

PROGRAMME CODE: BNG/BNH/BNK/BNL/BNM

COURSE NAME : ELECTRICAL AND  
ELECTRONIC TECHNOLOGY

COURSE CODE : BNJ10903

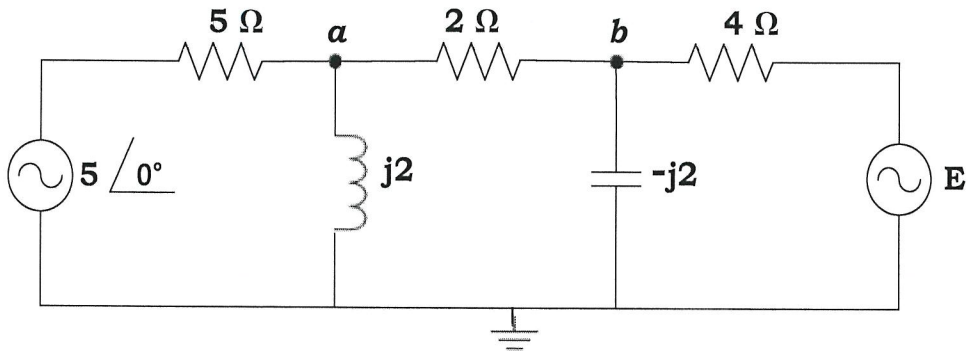


Figure Q4(c)

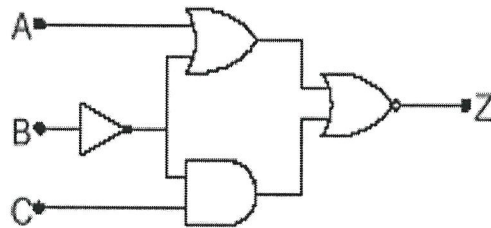


Figure Q5(b)

**TERBUKA**

## FINAL EXAMINATION

SEMESTER / SESSION: SEM II / 2017/2018  
 COURSE NAME : ELECTRICAL AND  
 ELECTRONIC TECHNOLOGY

PROGRAMME CODE: BNG/BNH/BNK/BNL/BNM  
 COURSE CODE : BNJ10903

## LIST OF FORMULA

## CAPACITOR AND INDUCTOR

$$C = \frac{\epsilon A}{d}$$

$$i = C \frac{dv}{dt}$$

$$L = \frac{N^2 \mu A}{l}$$

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$\tau = RC$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt + v(t_0)$$

$$w = \frac{1}{2} C v^2$$

$$v = L \frac{di}{dt}$$

$$w = \frac{1}{2} L i^2$$

$$\tau = \frac{L}{R}$$

## PHASOR REALTIONSHIP

$$v(t+T) = v(t)$$

$$f = \frac{1}{T}$$

$$z = x + jy = r \angle \phi = r(\cos \phi + j \sin \phi)$$

## ALTERNATING CURRENT POWER CALCULATION

$$P(t) = v(t)i(t)$$

Instantaneous power

$$P = \frac{1}{2} \operatorname{Re}[VI^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Average power

$$i_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$P_{RMS} = I_{RMS}^2 R = \frac{V_{RMS}^2}{R}$$

## TRANSFORMERS

$$\frac{V_P}{V_S} = \frac{N_P}{N_S}$$

TERBUKA











FINAL EXAMINATION

SEMESTER / SESSION: SEM II / 2017/2018  
 COURSE NAME : ELECTRICAL AND  
 ELECTRONIC TECHNOLOGY

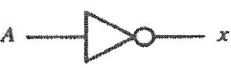PROGRAMME CODE: BNG/BNH/BNK/BNL/BNM  
 COURSE CODE : BNJ10903

LOGIC GATES

Name	Graphic symbol	Algebraic function	Truth table															
AND		$x = A \cdot B$ or $x = AB$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>x</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	x	0	0	0	0	1	0	1	0	0	1	1	1
A	B	x																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$x = A + B$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>x</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	x	0	0	0	0	1	1	1	0	1	1	1	1
A	B	x																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$x = A'$	<table border="1"> <thead> <tr> <th>A</th> <th>x</th> </tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	A	x	0	1	1	0									
A	x																	
0	1																	
1	0																	
Buffer		$x = A$	<table border="1"> <thead> <tr> <th>A</th> <th>x</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td></tr> </tbody> </table>	A	x	0	0	1	1									
A	x																	
0	0																	
1	1																	
NAND		$x = (AB)'$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>x</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	x	0	0	1	0	1	1	1	0	1	1	1	0
A	B	x																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$x = (A + B)'$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>x</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	x	0	0	1	0	1	0	1	0	0	1	1	0
A	B	x																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$x = A \oplus B$ or $x = A'B + AB'$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>x</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	x	0	0	0	0	1	1	1	0	1	1	1	0
A	B	x																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$x = (A \oplus B)'$ or $x = A'B' + AB$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>x</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	x	0	0	1	0	1	0	1	0	0	1	1	1
A	B	x																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

TERBUKA