



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2017/2018**

COURSE NAME : ELECTRICAL MACHINE AND DRIVES
COURSE CODE : BNR 31403
PROGRAMME CODE : BND
EXAMINATION DATE : JUNE/JULY 2018
DURATION : 3 HOURS
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

TERBUKA

THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES

- Q1** (a) A terminal characteristic of a machine is a plot of the machine's output quantities versus each other. For a motor, the output quantities are shaft torque and speed, so the terminal characteristic of a motor is a plot of its output torque versus speed.
- (i) Draw and label clearly the speed-torque characteristic of a series and shunt DC motor. (3 marks)
 - (ii) Based on your drawing in **Q1(a)(i)**, explain clearly the main disadvantages of DC series motor as can see from the speed-torque characteristic. (2 marks)
 - (iii) Suggest **ONE (1)** solution to avoid the problem stated in **Q1(a)(ii)** to happen. (1 marks)
- (b) A 50 hp, 250 V, 1200 r/min, DC shunt motor with compensating windings has an armature resistance which including the brushes, compensating windings, and interpoles of 0.06Ω . Its field circuit has a total resistance $R_{adj}+R_F$ of 50Ω , which produces a no load speed of 1200 rpm. There are 1200 turns per pole on the shunt field winding as shown in **Figure Q1(b)**.
- (i) Find the speed of the motor when the input current is 100 A. (3 marks)
 - (ii) Find the speed of the motor when the input current is 300 A. (3 marks)
 - (iii) Plot the torque-speed characteristic of this motor. (7 marks)
- (c) A series-connected DC motor has an armature resistance of 0.5Ω and field winding resistance of 1.5Ω . In driving a certain load at 1200 rpm, the current drawn by the motor is 20 A from a voltage source of 220 V. The rotational loss is 150 W. Find the output power and efficiency. (6 marks)
- Q2** (a) Explain how a synchronous motor starts up. When should the DC excitation be applied. (6 marks)
- (b) A 100 kW synchronous motor has the parameters as shown in **Figure Q2(b)**. Draw the phasor diagram and determine :
- (i) Active power per phase
 - (ii) Apparent power per phase
 - (iii) The AC line current
 - (iv) The value and phase of E_o
 - (v) Draw the phasor diagram

TERBUKA

(10 marks)

- (c) A 480 V 200 kVA 0.8 power-factor-lagging, 60 Hz two-pole Y-connected synchronous generator has a synchronous reactance of 0.25Ω and an armature resistance of 0.03Ω . At 60 Hz, its friction and windage losses are 6 kW, and its core losses are 4 kW. The field circuit has a dc voltage of 200 V, and the maximum I_F is 10 A. The resistance of the field circuit is adjustable over the range from 20 to 200 Ω . The OCC of this generator is shown in **Figure Q4(c)**. Determine:
- (i) the field current required to make terminal voltage, V equal to 480 V when the generator is running at no load. (1 marks)
 - (ii) the internal generated voltage of this machine at rated conditions. (4 marks)
 - (iii) the field current required to make V_T equal to 480 V when the generator is running at rated conditions. (3 marks)
 - (iv) the power and torque supplied by the prime mover. (6 marks)
 - (v) the efficiency of the generator at rated load. (2 marks)

- Q5** (a) The physical layout of three single-phase transformer is illustrated in **Figure Q5(a)**. Analyse the layout and sketch the corresponding three-phase schematic diagram for the primary and secondary sides of the transformer. (6 marks)
- (b) A 80 kV: 13.2 kV three-phase transformer connected in Y-Y configuration is supplying a commercial building in a city. The load draws 90 MW of power at a lagging power factor of 81 %. Analyse the circuit and calculate :
- (i) The apparent power drawn by the load (2 marks)
 - (ii) The apparent power supplied by the HV line (consider losses in transformer is small) (2 marks)
 - (iii) The current in both HV and LV line (3 marks)
 - (iv) The current in primary and secondary winding (3 marks)
- (c) Discuss advantages of three-phase autotransformer. **TERBUKA** (5 marks)
- (d) Sketch the equivalent circuit of an induction motor and label all parameters completely. (4 marks)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2017/2018
 COURSE : ELECTRICAL MACHINE AND DRIVES

PROGRAMME CODE : BND
 COURSE CODE : BNR 31403


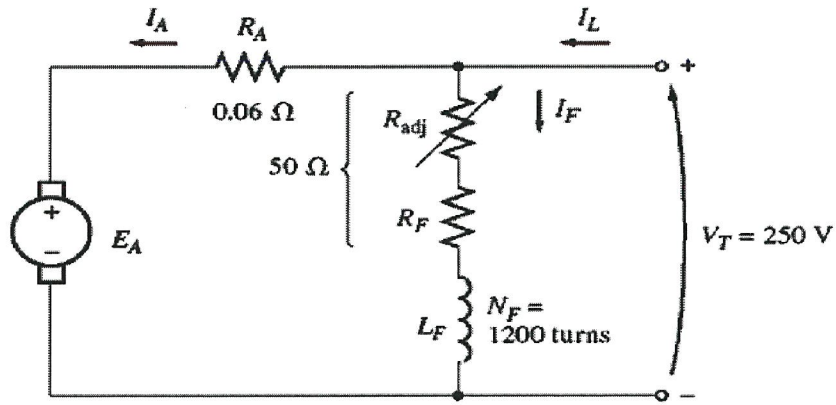


Figure Q1 (b)

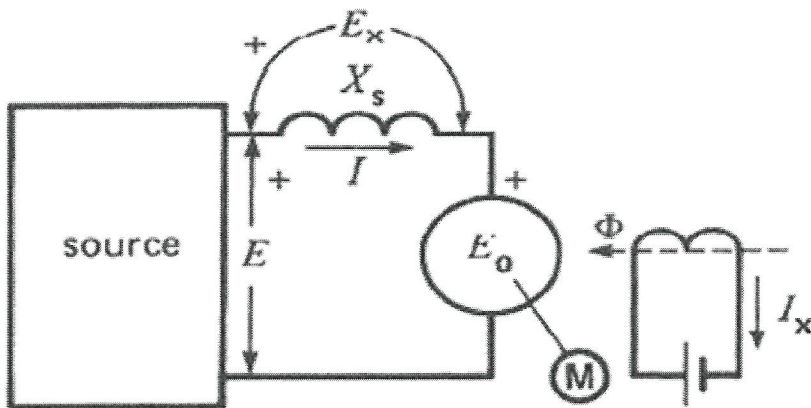

$E = 2.4 \text{ kV}$
 $X_s = 3 \Omega$
 Power factor = 0.85 leading

Figure Q2 (b)

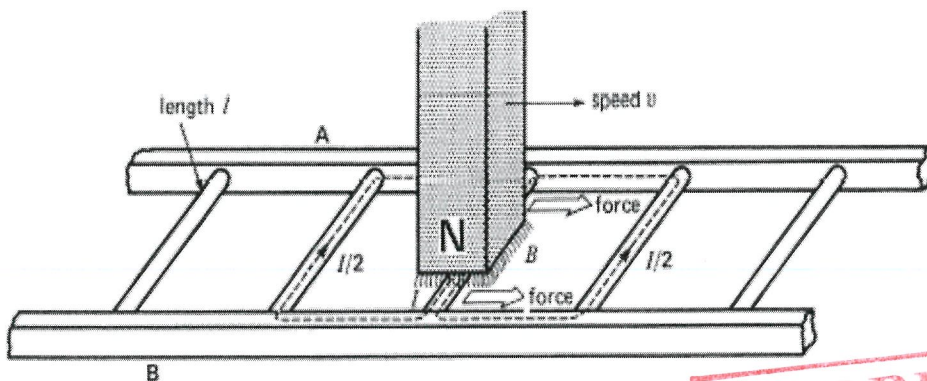


Figure Q3 (a)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2017/2018
 COURSE : ELECTRICAL MACHINE AND DRIVES

PROGRAMME CODE : BND
 COURSE CODE : BNR 31403



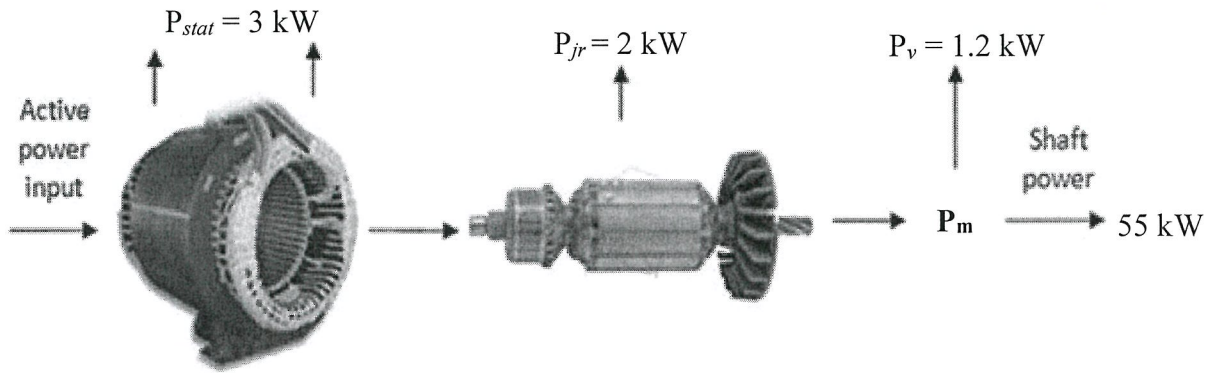


Figure Q3(d)

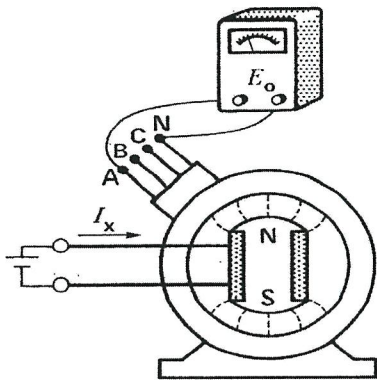

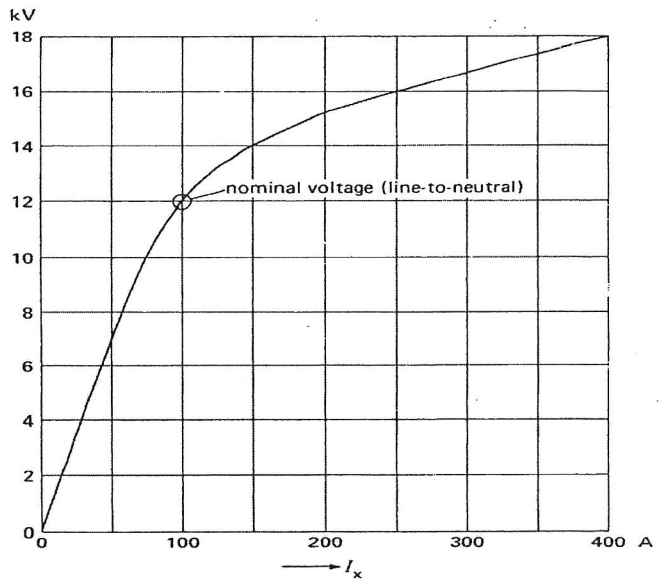(a) Generator operating at no-load.
 I_x is the generator variable
 exciting current



(b) No-load saturation curve of a 36 MVA,
 21kV 3-phase generator

Figure Q4 (b)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II/ 2017/2018 PROGRAMME CODE : BND
 COURSE : ELECTRICAL MACHINE AND DRIVES COURSE CODE : BNR 31403

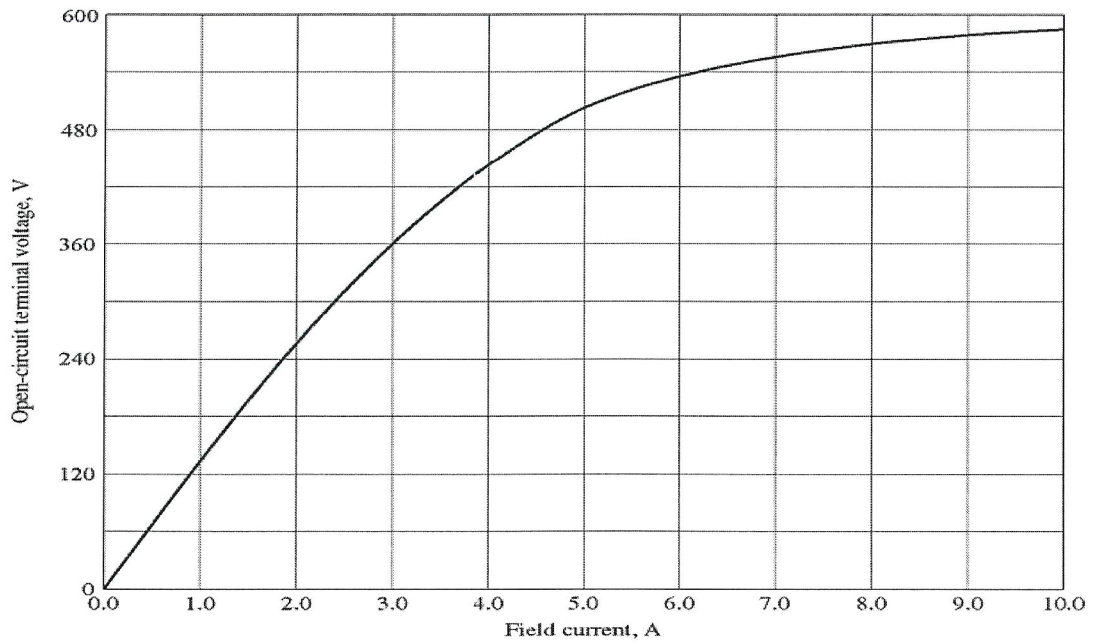


Figure Q4 (c)

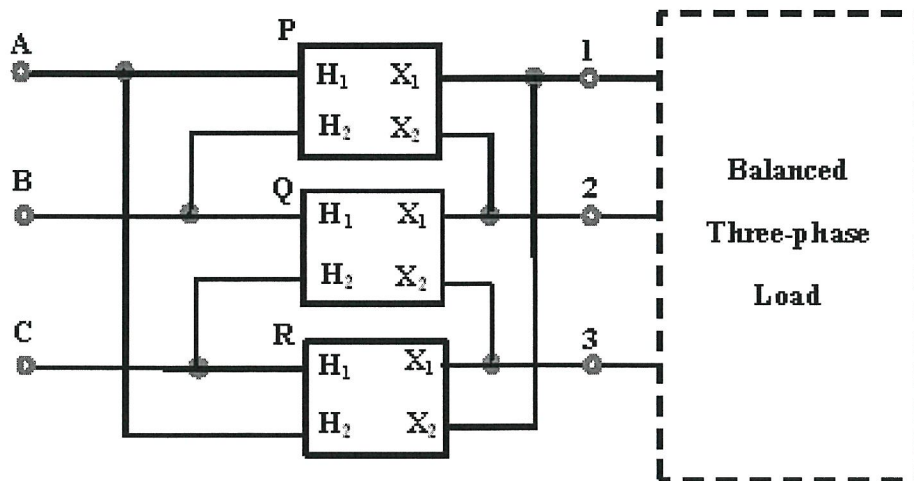


Figure Q5 (a)

TERBUKA