



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2017/2018**

COURSE NAME : ELECTRONIC DEVICES AND  
CIRCUITS II / ELECTRONIC  
DEVICES AND CIRCUITS

COURSE CODE : BNR 25903 / BNR 22303

PROGRAMME CODE : BNE

EXAMINATION DATE : JUNE / JULY 2018

DURATION : 3 HOURS

INSTRUCTION : ANSWER ALL QUESTIONS

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

- Q1** (a) Explain the significance of zero output impedance and infinite input impedance of an ideal op-amp. (2 marks)
- (b) From amplifier circuit in **Figure Q1(b)**:
- (i) Calculate all voltage drops with polarity markings. (2 marks)
- (ii) Calculate all currents and show the current direction. (2 marks)
- (iii) Calculate the overall voltage gain,  $A_V$  as a ratio and as in decibel unit. (2 marks)
- (c) **Figure Q1(c)** shows an inverting op-amp with additional of output resistor,  $R_3$ . The circuit parameters are  $R_1 = 5 \text{ k}\Omega$ ,  $R_2 = 25 \text{ k}\Omega$ ,  $R_3 = 12.5 \text{ k}\Omega$  and  $R_L = 5 \text{ k}\Omega$ .
- (i) Derive the expression for  $V_{out}$  in terms of the input voltage,  $V_{in}$  (1 marks)
- (ii) Derive the expression for  $I_3$  in terms of the input voltage,  $V_{in}$ . (3 marks)
- (iii) Explain the situation of  $I_3$  if  $R_3$  is doubled for example  $25 \text{ k}\Omega$ . (1 marks)
- (d) Show the connection of an LM124 quad op-amp as a three-stage amplifier with gains of +15, -22, and -30. Use a  $420 \text{ k}\Omega$  feedback resistor for all stages. Calculate the output voltage results for an input of  $V_{in} = 80 \text{ }\mu\text{V}$ . Refer **Appendix A** for pin configuration. (7 marks)
- Q2** (a) With the aid of diagram, explain the crossover distortion situation that usually occur in class B amplifier. Suggest a components to be added in order to reduce the crossover distortion. (5 marks)
- (b) Sketch the collector current waveform when amplifier operating as class A, class B, class C and class AB. (4 marks)
- (c) If the input voltage to the power amplifier of **Figure Q2(c)** is  $8 \text{ V}_{\text{rms}}$ , calculate:
- (i) Power input,  $P_i$  (dc). (2 marks)
- (ii) Power output,  $P_o$  (ac). (2 marks)

**TERBUKA** (2 marks)

- (iii) Efficiency, %  $\eta$ . (2 marks)
- (iv) Power dissipated by both power output transistors. (2 marks)
- (d) A 2N3055 power transistor dissipates 20 W during operation. The amplifier circuit is designed to operate over an ambient temperature range of 0°C to 80°C. The worst case condition exists when the ambient temperature is 80°C. The temperature case to heat sink thermal resistance is 0.5 °C/W and the heat sink is rated for a thermal resistance of 3 °C /W. Calculate the case temperature of the transistor for worst case operating conditions. (3 marks)
- Q3** (a) Describe the operation of the circuit in **Figure Q3(a)**. (4 marks)
- (b) Digital-to-analog conversion can be achieved using a number of different methods. One popular scheme uses a network of resistors called a ladder network. Sketch a ladder network using 01101 input and 15 k $\Omega$  resistors. (5 marks)
- (c) Draw the circuit of a one-shot using a 555 timer to provide one time period of 20  $\mu$ s. If  $R_A = 7.5$  k $\Omega$ , determine the value of capacitor,  $C$ . (5 marks)
- (d) **Figure Q3(d)** shows the PLL connected to work as a FM demodulator.
- (i) Calculate the center frequency of the circuit. (1 marks)
- (ii) Find the value of capacitor,  $C_I$  in the circuit to obtain a center frequency of 100 kHz. (2 marks)
- (iii) Find the lock range for  $R_I = 4.7$  k $\Omega$  and  $C_I = 0.001$   $\mu$ F. (3 marks)
- Q4** (a) With the aid of diagram, describe the principles of oscillator operation in electronic systems. (4 marks)
- (b) State **TWO (2)** types of sine wave oscillator. Define **TWO (2)** examples for each of oscillator. (4 marks)

**TERBUKA**

- (c) For the circuit shown in **Figure Q4(c)**,
- (i) Find  $t_H$  and  $t_L$  for the output,  $V_O$ . (3 marks)
- (ii) Determine the duty cycle. (1 marks)
- (iii) Clearly draw and label the waveforms of  $V_C$  and  $V_O$ . (3 marks)
- (d) Design a phase-shift oscillator for a frequency of 800 Hz. The capacitors are to be 10 nF. (5 marks)

- Q5** (a) With the aid of diagram, show the relation between  $V_o$ ,  $V_{in}$ ,  $V_{ut}$  and  $V_{lt}$  of Schmitt trigger. (4 marks)
- (b) **Figure Q5(b)** shows the circuit of a Schmitt Trigger and its transfer characteristic respectively. Based on these figures, determine  $V_{REF}$  and  $R_2$ . (5 marks)
- (c) Transfer function for two type of active filter are:

$$H(s) = \frac{28.3 \times 10^8}{2s^2 + (5.684 \times 10^4)s + (8.08 \times 10^8)}$$

$$H(s) = \frac{6.25s^2}{2.5s^2 + (2.222 \times 10^4)s + (9.875 \times 10^7)}$$

- (i) State type of filter for each transfer function. (2 marks)
- (ii) Find the cut-off frequency for each filter. (3 marks)
- (d) Design a second order low pass Butterworth filter with cut-off frequency of 1 kHz. Select  $C = 0.0047 \mu\text{F}$ . Draw the frequency response of the circuit. (6 marks)

**TERBUKA**

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2017/2018  
COURSE NAME : ELECTRONIC DEVICES AND  
CIRCUITS II / ELECTRONIC DEVICES  
AND CIRCUITS

PROGRAMME CODE : BNE  
COURSE CODE : BNR 25903 /  
BNR 22303

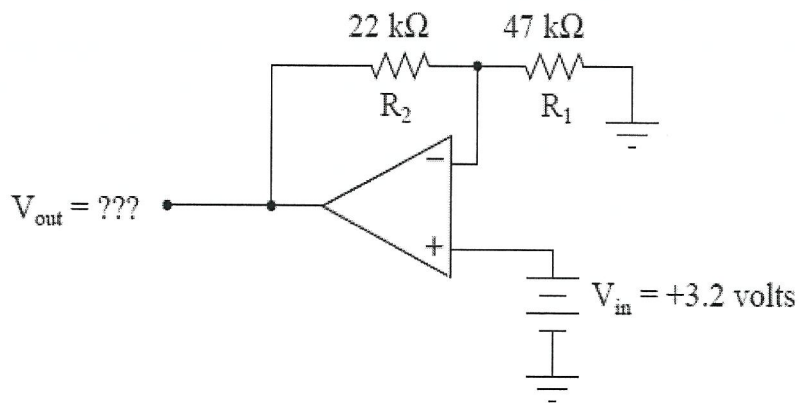


Figure Q1(b)

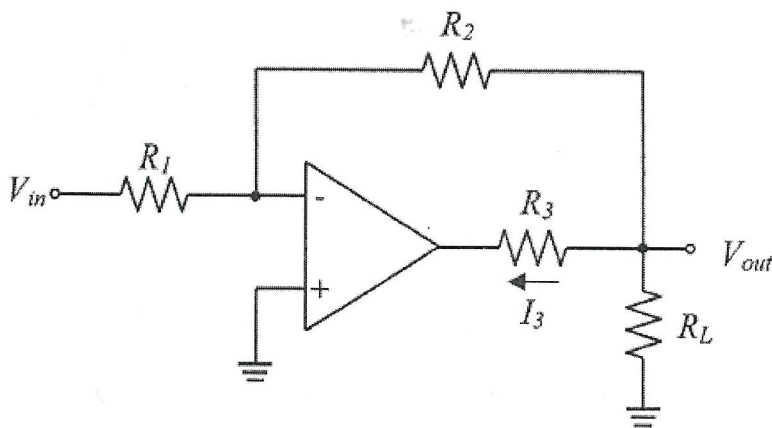


Figure Q1(c)

**TERBUKA**



FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2017/2018  
COURSE NAME : ELECTRONIC DEVICES AND  
CIRCUITS II / ELECTRONIC DEVICES  
AND CIRCUITS

PROGRAMME CODE : BNE  
COURSE CODE : BNR 25903 /  
BNR 22303

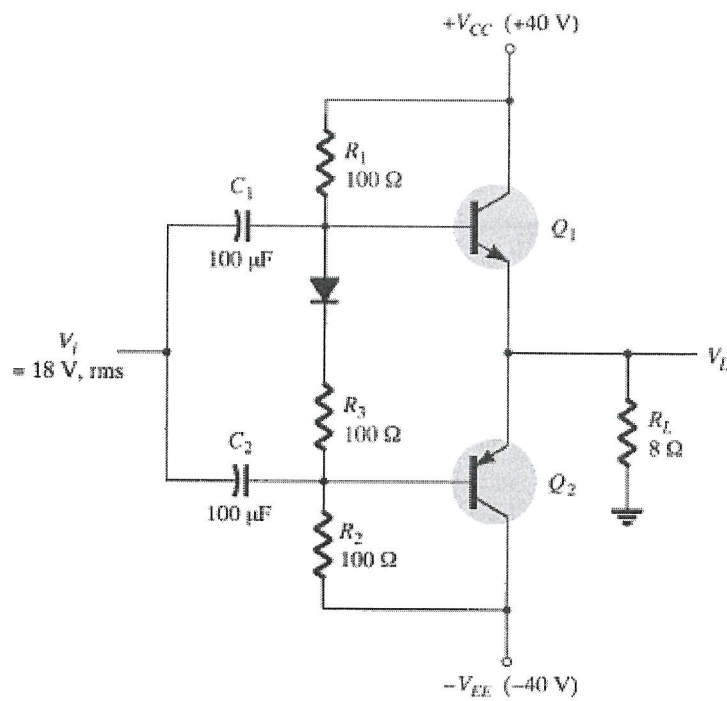


Figure Q2(c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2017/2018  
 COURSE NAME : ELECTRONIC DEVICES AND CIRCUITS II / ELECTRONIC DEVICES AND CIRCUITS

PROGRAMME CODE : BNE  
 COURSE CODE : BNR 25903 / BNR 22303

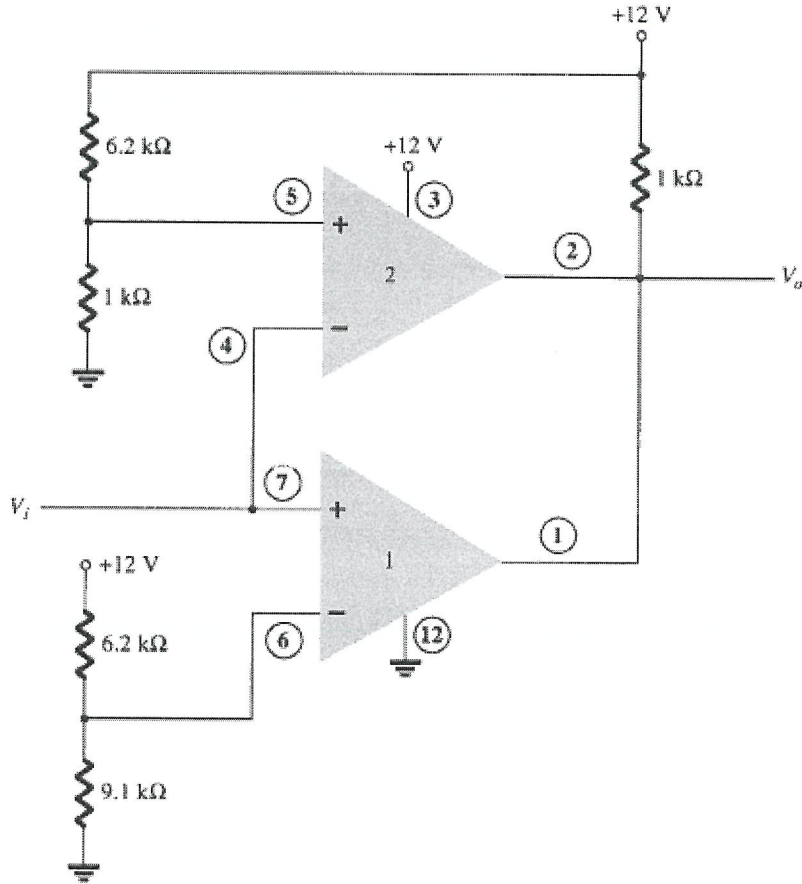


Figure Q3(a)

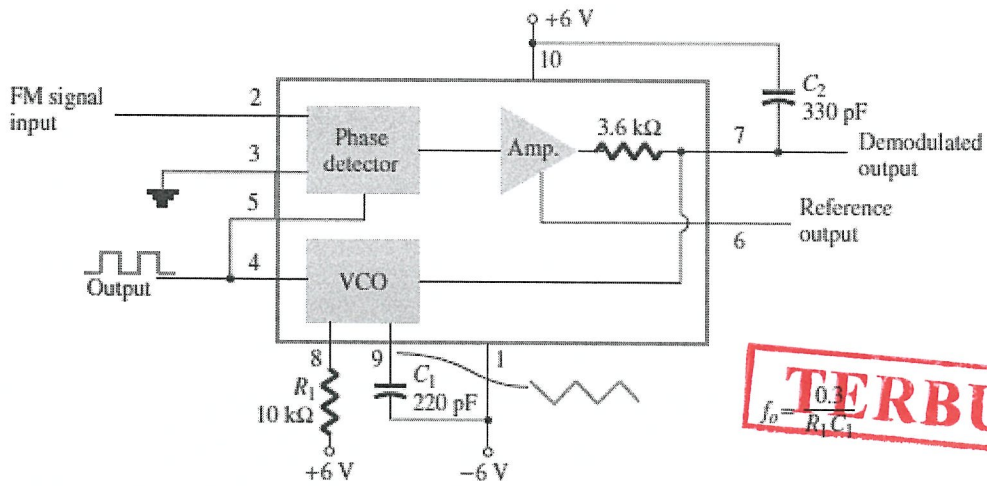


Figure Q3(d)

TERBUKA

**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2017/2018  
 COURSE NAME : ELECTRONIC DEVICES AND  
 CIRCUITS II / ELECTRONIC DEVICES  
 AND CIRCUITS

PROGRAMME CODE : BNE  
 COURSE CODE : BNR 25903 /  
 BNR 22303

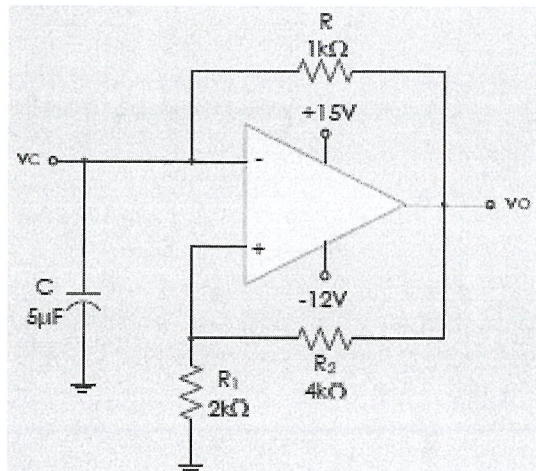


Figure Q4(c)

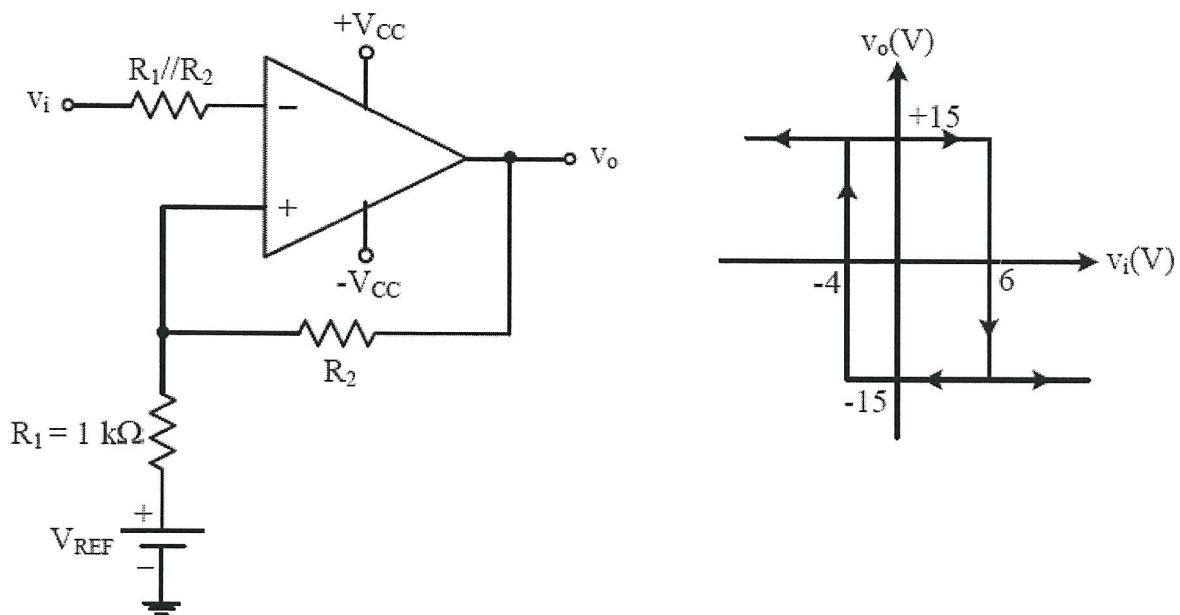


Figure Q5(b)

**TERBUKA**



**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2017/2018  
 COURSE NAME : ELECTRONIC DEVICES AND  
 CIRCUITS II / ELECTRONIC DEVICES  
 AND CIRCUITS

PROGRAMME CODE : BNE  
 COURSE CODE : BNR 25903 /  
 BNR 22303

**APPENDIX A**

Philips Semiconductors

Product specification

**Low power quad op amps**

**LM124/224/324/324A/  
 SA534/LM2902**

**DESCRIPTION**

The LM124/SA534/LM2902 series consists of four independent, high-gain, internally frequency-compensated operational amplifiers designed specifically to operate from a single power supply over a wide range of voltages.

**UNIQUE FEATURES**

In the linear mode, the input common-mode voltage range includes ground and the output voltage can also swing to ground, even though operated from only a single power supply voltage.

The unity gain crossover frequency and the input bias current are temperature-compensated.

**FEATURES**

- Internally frequency-compensated for unity gain
- Large DC voltage gain: 100dB
- Wide bandwidth (unity gain): 1MHz (temperature-compensated)
- Wide power supply range Single supply: 3V<sub>DC</sub> to 30V<sub>DC</sub> or dual supplies: ±1.5V<sub>DC</sub> to ±15V<sub>DC</sub>
- Very low supply current drain: essentially independent of supply voltage (1mW/op amp at +5V<sub>DC</sub>)
- Low input biasing current: 45nA<sub>DC</sub> (temperature-compensated)
- Low input offset voltage: 2mV<sub>DC</sub> and offset current: 5nA<sub>DC</sub>
- Differential input voltage range equal to the power supply voltage
- Large output voltage: 0V<sub>DC</sub> to V<sub>CC</sub>-1.5V<sub>DC</sub> swing

**PIN CONFIGURATION**

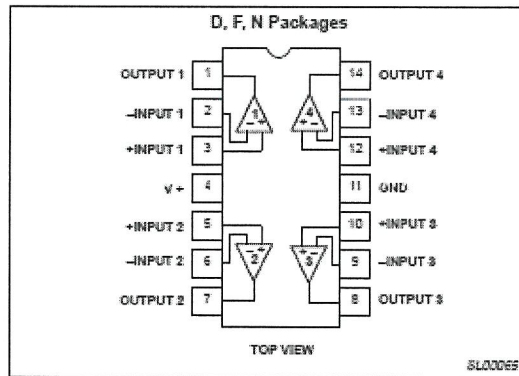


Figure 1. Pin Configuration

**TERBUKA**