



UTHM
Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2018/2019**

COURSE NAME : ELECTRONIC DEVICES AND
CIRCUITS II / ELECTRONIC
DEVICES AND CIRCUITS

COURSE CODE : BNR 25903 / BNR 22303

PROGRAMME CODE : BNE

EXAMINATION DATE : JUNE / JULY 2019

DURATION : 3 HOURS

INSTRUCTION : ANSWER **ALL** QUESTIONS

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

- Q1**
- (a) Explain the significance of zero output impedance and infinite input impedance of an ideal op-amp. (2 marks)
- (b) Refer to amplifier circuit in **Figure Q1(b)**.
- (i) Calculate all voltage drops with polarity markings. (2 marks)
- (ii) Calculate all currents and show the current direction. (2 marks)
- (iii) Calculate the overall voltage gain, A_v as a ratio and as in decibel unit. (2 marks)
- (c) (i) For the circuit in **Figure Q1(c)(i)**, calculate the feedback current, I_L . (2 marks)
- (ii) For the circuit in **Figure Q1(c)(ii)**, calculate the output voltage, V_o . (2 marks)
- (d) Analyze the circuit in **Figure Q1(d)** and sketch the output voltage versus time graph for the given input voltage. (8 marks)
- Q2**
- (a) Explain with the diagram crossover distortion situation that usually occur in class B amplifier. Suggest a component to be added in order to reduce the crossover distortion. (5 marks)
- (b) Sketch the collector current waveform when amplifier operating as class A, class B, class C and class AB. (4 marks)
- (c) The input voltage of the power amplifier for the **Figure Q2(c)** is $8 V_{\text{rms}}$. Calculate:
- (i) Power input, P_i (dc). (2 marks)
- (ii) Power output, P_o (ac). (2 marks)
- (iii) Efficiency, $\% \eta$. (2 marks)
- (iv) Power dissipated by both power output transistors. (2 marks)

- (d) A 2N3055 power transistor dissipates 20 W during operation. The amplifier circuit is designed to operate over an ambient temperature range of 0°C to 80°C. The worse case condition exists when the ambient temperature is 80°C. The temperature case to heat sink thermal resistance is 0.5°C/W and the heat sink is rated for a thermal resistance of 3°C/W. Calculate the case temperature of the transistor for worst case operating conditions. (3 marks)
- Q3**
- (a) Analyze the operation of the circuit in **Figure Q3(a)**. (4 marks)
- (b) Digital-to-analog conversion can be achieved using a number of different methods. One popular scheme uses a network of resistors called a ladder network. Sketch a ladder network using 01101 input and 15 kΩ resistors. (5 marks)
- (c) Draw the circuit of a one-shot using a 555 timer to provide one time period of 20 μs. If $R_A = 7.5 \text{ k}\Omega$, determine the value of capacitor, C . (5 marks)
- (d) **Figure Q3(d)** shows the phase-locked loop (PLL) connected to work as a FM demodulator.
- (i) Calculate the center frequency of the circuit. (1 marks)
- (ii) Find the value of capacitor, C_I in the circuit to obtain a center frequency of 100 kHz. (2 marks)
- (iii) Find the lock range for $R_I = 4.7 \text{ k}\Omega$ and $C_I = 0.001 \text{ }\mu\text{F}$. (3 marks)
- Q4**
- (a) Describe the principles of oscillator operation in electronic systems by using a diagram. (4 marks)
- (b) State **TWO (2)** types of sine wave oscillator. Define **TWO (2)** examples for each of oscillator. (4 marks)
- (c) For the circuit shown in **Figure Q4(c)**,
- (i) Find t_H and t_L for the output, V_O . (3 marks)
- (ii) Determine the duty cycle. (1 marks)

- (iii) Clearly draw and label the waveforms of V_C and V_O . (3 marks)
- (d) Design a phase-shift oscillator for a frequency of 800 Hz. The capacitors value is 10 nF. (5 marks)
- Q5** (a) With the aid of diagram, show the relation between V_o , V_{in} , V_{ut} and V_{lt} of Schmitt trigger transfer characteristic. (4 marks)
- (b) **Figure Q5(b)** shows the circuit of a Schmitt Trigger and its transfer characteristic respectively. Based on these figures, determine V_{REF} and R_2 . (5 marks)
- (c) Transfer function for two types of active filter are:
- $$H(s) = \frac{28.3 \times 10^8}{2s^2 + (5.684 \times 10^4)s + (8.08 \times 10^8)}$$
- $$H(s) = \frac{6.25s^2}{2.5s^2 + (2.222 \times 10^4)s + (9.875 \times 10^7)}$$
- (i) List type of filter for each transfer function. (2 marks)
- (ii) Find the cut-off frequency for each filter. (3 marks)
- (d) Design a second order low pass Butterworth filter with cut-off frequency of 1 kHz. Select $C = 0.0047 \mu\text{F}$. Then, draw the frequency response of the circuit. (6 marks)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2018/2019
COURSE NAME : ELECTRONIC DEVICES AND
CIRCUITS II / ELECTRONIC DEVICES
AND CIRCUITS

PROGRAMME CODE : BNE
COURSE CODE : BNR 25903 /
BNR 22303

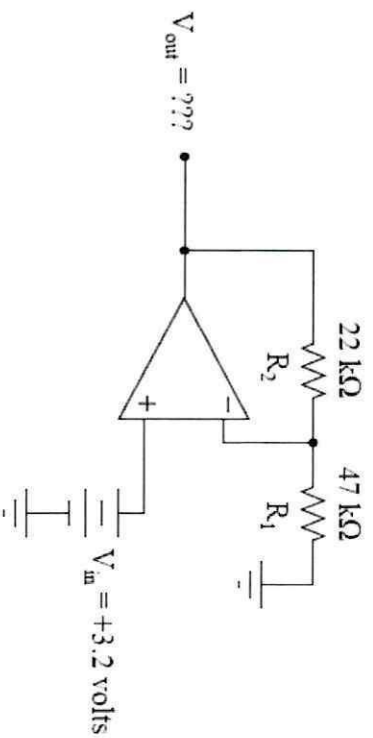


Figure Q1(b)

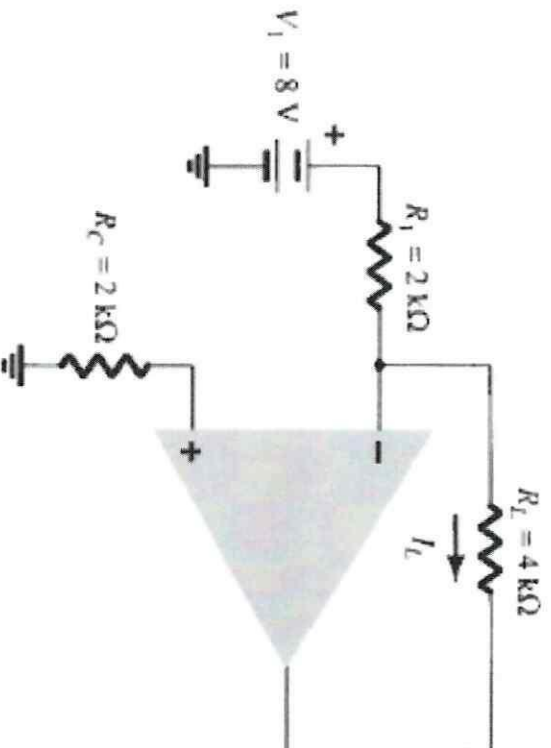


Figure Q1(c)(i)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2018/2019
 COURSE NAME : ELECTRONIC DEVICES AND
 CIRCUITS II / ELECTRONIC DEVICES
 AND CIRCUITS

PROGRAMME CODE : BNE
 COURSE CODE : BNR 25903 /
 BNR 22303

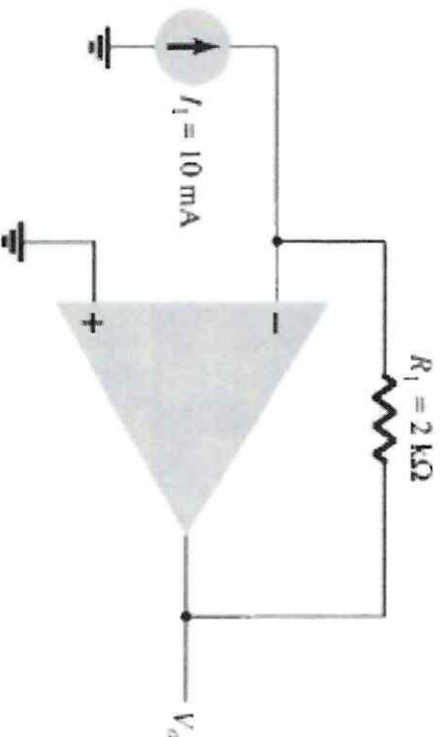


Figure Q1(c)(ii)

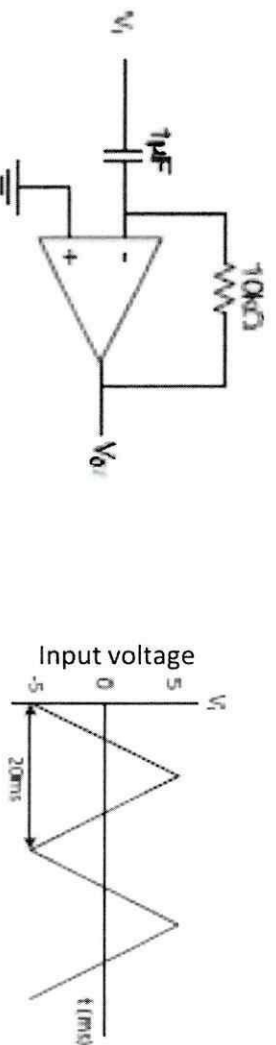


Figure Q1(d)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2018/2019
 COURSE NAME : ELECTRONIC DEVICES AND
 CIRCUITS II / ELECTRONIC DEVICES
 AND CIRCUITS

PROGRAMME CODE : BNE
 COURSE CODE : BNR 25903 /
 BNR 22303

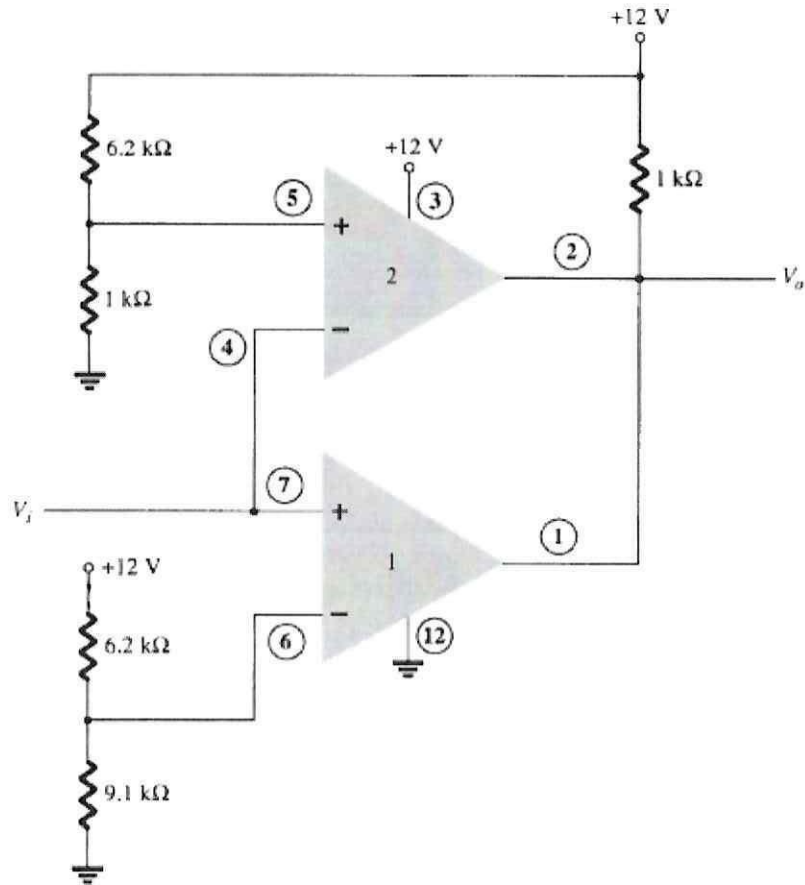


Figure Q3(a)

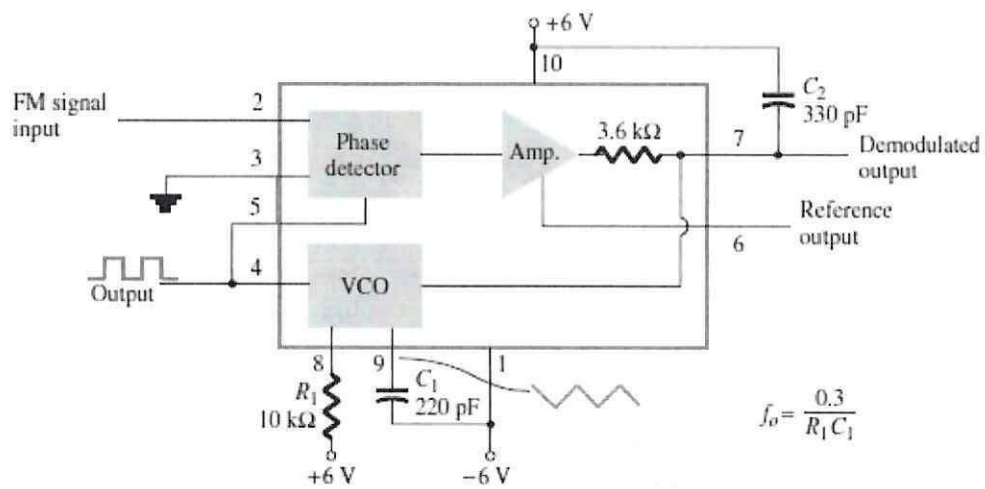


Figure Q3(d)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2018/2019
 COURSE NAME : ELECTRONIC DEVICES AND
 CIRCUITS II / ELECTRONIC DEVICES
 AND CIRCUITS

PROGRAMME CODE : BNE
 COURSE CODE : BNR 25903 /
 BNR 22303

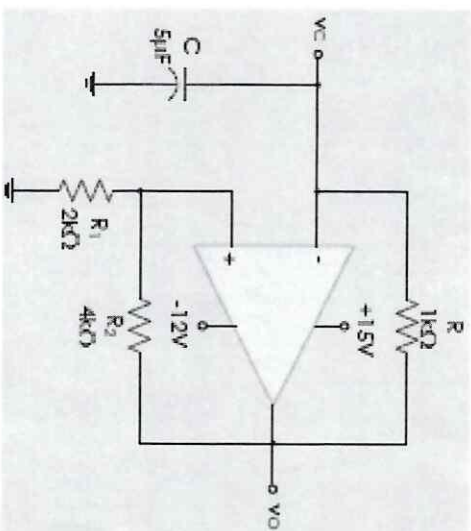


Figure Q4(c)

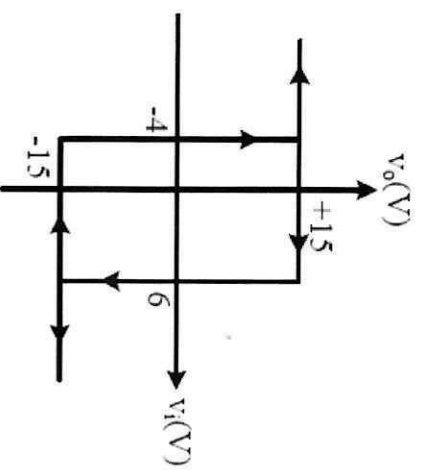
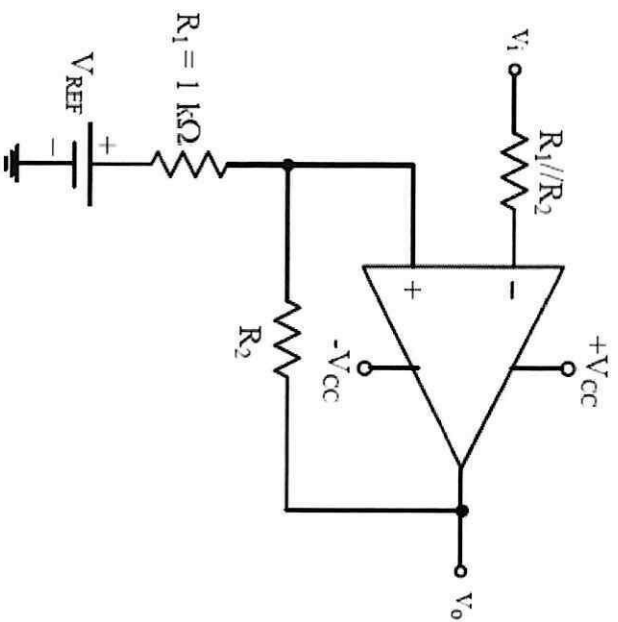


Figure Q5(b)