



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2019/2020**

COURSE NAME : ELECTRICAL MACHINE
COURSE CODE : BNR 35603
PROGRAMME CODE : BND
EXAMINATION DATE : DECEMBER 2019 / JANUARY 2020
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF **SIX (6)** PAGES

- Q1** (a) Name the main components of induction motor and explain briefly their usage. (2 marks)
- (b) Define slip speed and slip. Gives the rotor frequency (f_r) of an induction motor if the synchronous frequency is given as 50 Hz, and the rotor is locked and rotates at 4% slip (6 marks)
- (c) A 415 V, 50 Hz, Y-connected, 4-pole induction motor is rated at 20 horse power (HP). Its per phase equivalent circuit component data are given as:
- Stator circuit:
 $R_1 = 0.44 \Omega$, $X_1 = 1.25 \Omega$
- Rotor circuit:
 $R_2 = 0.40 \Omega$, $X_2 = 1.25 \Omega$
- Magnetizing circuit:
 $R_C = 350 \Omega$, $X_M = 27 \Omega$
- The motor mechanical losses and core losses are 262 W and 150 W, respectively. For slip of 3%, determine:
- (i) the motor's stator, rotor and starting current; (9 marks)
- (ii) the efficiency of the motor; (4 marks)
- (iii) The induced torque and load torque of this motor (4 marks)
- Q2** (a) Explain briefly how to determine the synchronous reactance of a three-phase generator. (6 marks)
- (b) A three-phase, 200 kVA, 400 V, 50 Hz alternator has a per phase armature resistance and synchronous reactance of 0.1 and 0.2 Ω respectively. Determine induced emf when the machine is delivering a rated current at unity power factor. Draw the phasor diagram of the given alternator. (4 marks)

TERBUKA

- (c) A 480 V 200 kVA 0.8 power-factor-lagging, 60 Hz two-pole Y-connected synchronous generator has a synchronous reactance of 0.25Ω and an armature resistance of 0.03Ω . At 60 Hz, its friction and windage losses are 6 kW, and its core losses are 4 kW. The field circuit has a dc voltage of 200 V, and the maximum I_F is 10 A. The resistance of the field circuit is adjustable over the range from 20 to 200 Ω . The OCC of this generator is shown in **Figure Q2(c)**.
- (i) Determine the field current required to make terminal voltage, V equal to 480 V when the generator is running at no load. (1 mark)
- (ii) Determine the internal generated voltage of this machine at rated conditions. (4 marks)
- (iii) Determine the field current when the generator is running at rated conditions. (3 marks)
- (iv) Determine the power and torque supplied by the prime mover. (5 marks)
- (v) Determine the efficiency of the generator at rated load. (2 marks)
- Q3** (a) Explain why a synchronous motor does not have a starting torque. Give **ONE (1)** method to start up a synchronous motor. (4 marks)
- (b) A 460-V, 200-kVA, 0.80-PF-leading, 400-Hz, six-pole, Y-connected synchronous motor has negligible armature resistance and a synchronous reactance of 0.50 per unit. Ignore all losses.
- (i) Determine the speed rotation of this motor. (1 mark)
- (ii) Determine the output torque. (2 marks)
- (iii) Determine the internal generated voltage at rated condition. (7 marks)
- (iv) Determine the maximum possible output power when the armature current are the same in **Q3(b)(iii)**. (1 mark)

TERBUKA

- (c) A plot of I_A versus I_F for a synchronous motor is called as a synchronous motor v curve, for the obvious reason that is shaped like the letter V.
- (i) Draw and label clearly the synchronous motor v curve corresponding to different real power levels. (4 marks)
 - (ii) Based on your drawing in question **Q3(c)(i)**, label where is the minimum armature current, lagging and leading power factor occurs. (3 marks)
 - (iii) Explain, the relationship between I_F and I_A to determine either the reactive power is being supplied to or by motor. (3 marks)

Q4

- (a) A terminal characteristic of a machine is a plot of the machine's output quantities versus each other. For a motor, the output quantities are shaft torque and speed, so the terminal characteristic of a motor is a plot of its output torque versus speed.
- (i) Draw and label clearly the speed-torque characteristic of a series and shunt DC motor. (3 marks)
 - (ii) Based on your drawing in question **Q4(a)(i)**, explain clearly the main disadvantages of DC series motor as can see from the speed-torque characteristic. (2 marks)
 - (iii) Suggest **ONE (1)** solution to avoid the problem stated in question **Q4(a)(ii)** to happen. (1 mark)
- (b) A 50 hp, 250 V, 1200 r/min, DC shunt motor with compensating windings has an armature resistance which including the brushes, compensating windings, and interpoles of 0.06Ω . Its field circuit has a total resistance $R_{adj}+R_F$ of 50Ω , which produces a no load speed of 1200 rpm. There are 1200 turns per pole on the shunt field winding as shown in **Figure Q4(b)**.
- (i) Find the speed of the motor when the input current is 100 A. (3 marks)
 - (ii) Find the speed of the motor when the input current is 300 A. (3 marks)
 - (iii) Plot the torque-speed characteristic of this motor. (7 marks)

TERBUKA

- (c) A series-connected DC motor has an armature resistance of 0.5Ω and field winding resistance of 1.5Ω . In driving a certain load at 1200 rpm, the current drawn by the motor is 20 A from a voltage source of 220 V. The rotational loss is 150 W. Analyse the output power and efficiency.

(6 marks)

- END OF QUESTIONS -

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION: SEM I / 2019/2020
 COURSE NAME : ELECTRICAL MACHINE

PROGRAMME CODE: BND
 COURSE CODE : BNR35603

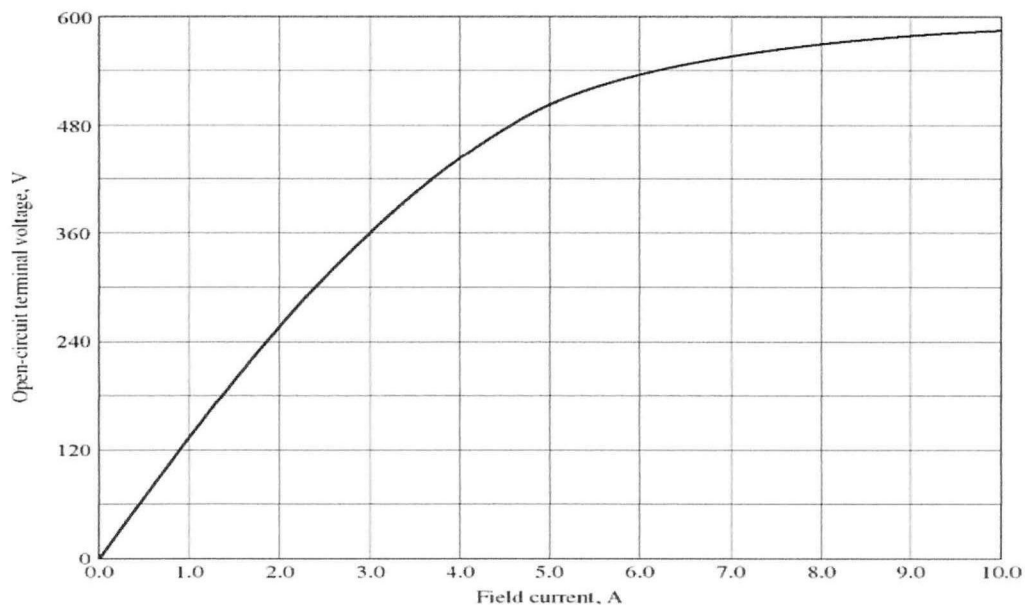


Figure Q2(c)

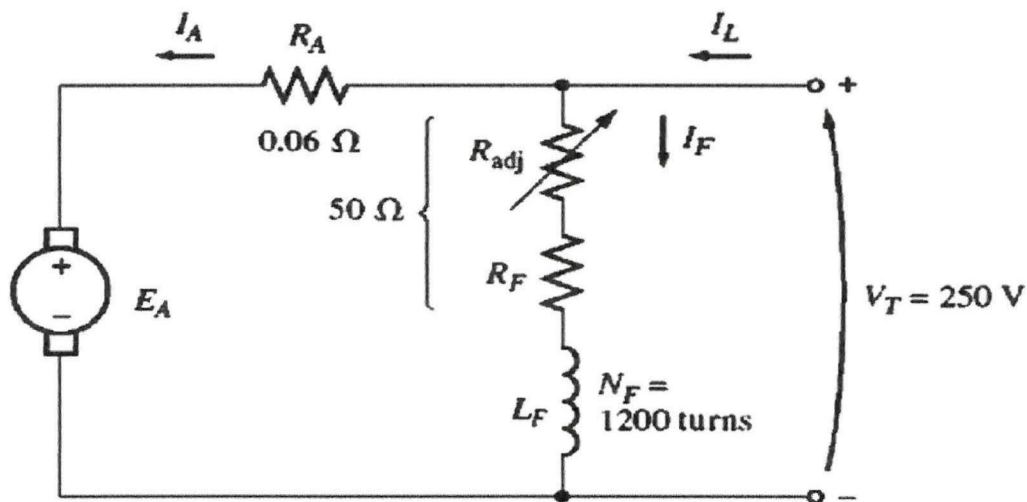


Figure Q4(b)

TERBUKA