



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2019/2020**

COURSE NAME : ELECTRICAL POWER & MACHINE
COURSE CODE : BNJ 20502
PROGRAMME CODE : BNM
EXAMINATION DATE : DECEMBER 2019 / JANUARY 2020
DURATION : 2 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF FIVE (5) PAGES

- Q1**
- (a) Calculate the voltage drop across the 60Ω load in the circuit shown in **Figure Q1 (a)**.
(4 marks)
 - (b) Three identical capacitors are connected in delta to a 415 V, 50 Hz, 3-phase supply. If the line current is 15 A, determine the capacitance of each of the capacitors.
(6 marks)
 - (c) Based on electrical power system, illustrate complete diagram of typical voltage level in a power system from power generator until end user (domestic customer).
(10 marks)
- Q2**
- A coil of inductance 318.3 mH and negligible resistance is connected in series with a 200Ω resistor to a 240 V, 50 Hz supply.
- (a) Draw the equivalent circuit of R-L series A.C circuit.
(2 marks)
 - (b) Calculate the voltage across the coil.
(8 marks)
 - (c) Calculate the voltage across the resistor.
(2 marks)
 - (d) Calculate the circuit phase angle, the leading or lagging condition and the power factor.
(5 marks)
 - (e) Propose **ONE (1)** method to improve power factor. List **TWO (2)** advantages of power factor correction.
(3 marks)
- Q3**
- (a) State Lenz's Law.
(2 marks)
 - (b) A ferromagnetic core is shown in **Figure Q3 (b)**. The depth of the core (into the page) is 5 cm, and the other dimensions are as shown in **Figure Q3 (b)**. There are 500 turns coil wrapped around the left side of the core. Assume that the relative permeability of the core is 1000.
 - (i) Determine the value of current that will produce a flux of 0.003 Wb.
(10 marks)
 - (ii) Determine the flux density at the right side of the core.
(2 marks)

TERBUKA

- (iii) Demonstrate the flow of the magnetic flux induced in the ferromagnetic core in a magnetic circuit analogy. (2 marks)
- (c) A 10 kVA, single-phase transformer has a turns ratio of 12:1 and is supplied by a 2.4 kV voltage. Neglecting losses, determine the full-load secondary current. (4 marks)
- Q4** (a) Differentiate any **THREE (3)** types of DC motors by sketching their equivalent circuit diagrams. (6 marks)
- (b) A 230 V, 10-HP DC series motor delivers power to a load at 1200 rpm. The armature current drawn by the motor is 20 A. The armature circuit resistance of the motor is 0.2 Ω and the field resistance is 1.5 Ω . If the rotational losses are 500 W, determine the load torque and the efficiency of the motor. (14 marks)
- Q5** (a) Describe **TWO (2)** advantages of squirrel-cage motor compared to wound-rotor motor. (4 marks)
- (b) Explain the working principle of squirrel-cage motor with the aid of **Figure Q5 (b)**. (4 marks)
- (c) An induction motor rotates at 2000 rpm has a power flow as shown in **Figure Q5 (c)**. The vertical arrow indicates the losses at several stages in the motor. Given the $P_{js} = 1000$ W, $P_r = 2000$ W, $P_{jr} = 2500$ W, $P_m = 50000$ W, $P_v = 1000$ W and the slip is 6 %.
- (i) Analyze the diagram, then, determine the efficiency of the motor. (8 marks)
- (ii) Calculate the torque at the given speed. (4 marks)

-END OF QUESTIONS-

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNM

COURSE NAME : ELECTRICAL POWER AND MACHINE

COURSE CODE : BNJ 20502

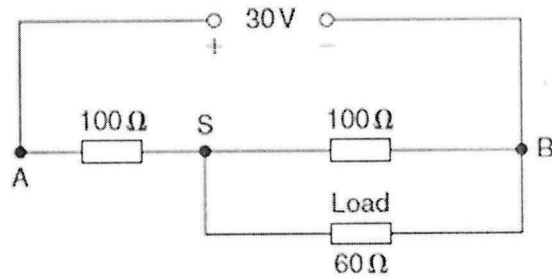


Figure Q1 (a)

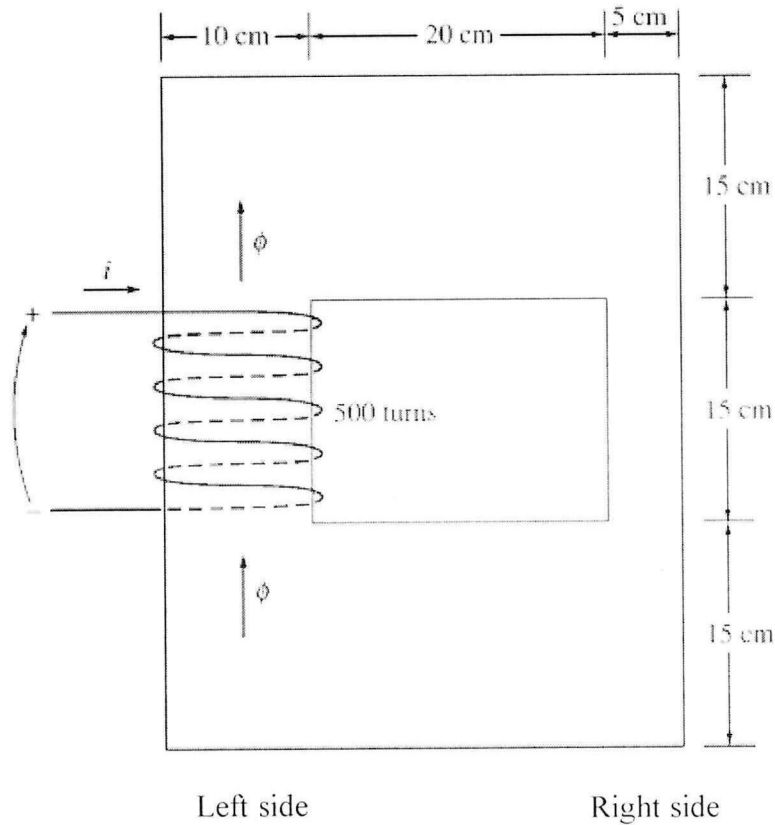


Figure Q3 (b)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNM

COURSE NAME : ELECTRICAL POWER AND MACHINE

COURSE CODE : BNJ 20502

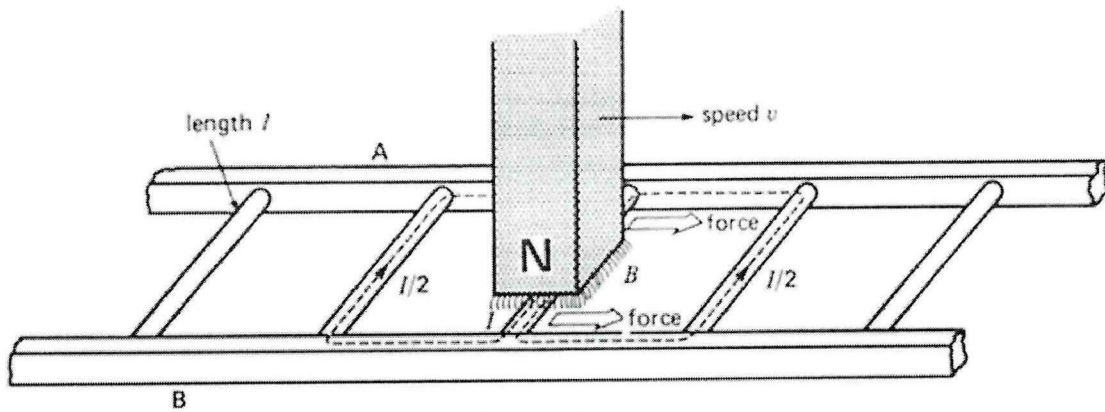


Figure Q5 (b)

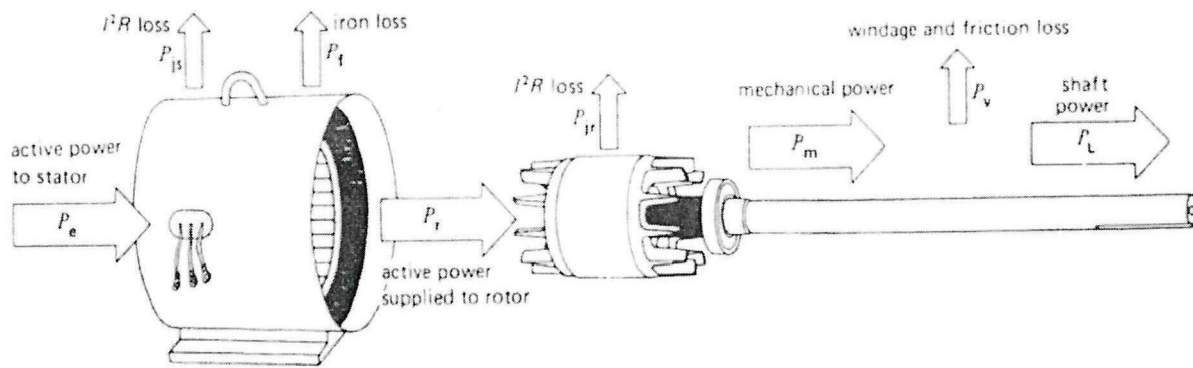


Figure Q5 (c)

TERBUKA