



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2019/2020**

COURSE NAME : ELECTRICAL PRINCIPLES II
COURSE CODE : BNR 10303
PROGRAMME CODE : BNF
EXAMINATION DATE : DECEMBER 2019 / JANUARY 2020
DURATION : 3 HOURS
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS
ONLY

TERBUKA

THIS QUESTION PAPER CONSISTS OF **EIGHTEEN (18)** PAGES

- Q1 (a) Given a sinusoidal voltage $v(t) = 5\sin(40\pi t - 60^\circ)$ V, compute:
- (i) the amplitude $v(t)$, (0.5 mark)
 - (ii) the phase ϕ , (0.5 mark)
 - (iii) the period T , (1 mark)
 - (iv) the frequency f . (1 mark)
- (b) Calculate these complex numbers and express your results in rectangular form.
- (i) $(40 \angle 50^\circ + 20 \angle -30^\circ)^{\frac{1}{2}}$ (2 marks)
 - (ii) $\frac{8 \angle -20^\circ}{(2 + j)(3 - j4)}$ (3 marks)
 - (iii) $(8 \angle 50^\circ)(5 - j12)$ (2 marks)
- (c) A voltage $v(t) = 100\cos(60t + 20^\circ)$ V is applied to a parallel combination of a 40 k Ω resistor and a 50 μ F capacitor. Compute the steady-state currents through the resistor and the capacitor? (3 marks)
- (d) Calculate current i in the circuit of **Figure Q1 (d)**, when $v_s(t) = 50\cos(200t)$ V (5 marks)
- (e) Calculate current I in the circuit of **Figure Q1 (e)**. (7 marks)
- Q2 (a) Determine V_x in the circuit of **Figure Q2 (a)**. TERBUKA (5 marks)
- (b) Using the superposition principle, compute v_o in the circuit of **Figure Q2 (b)**. (12marks)
- (c) Find I_o in the circuit of **Figure Q2 (c)** using the concept of source transformation. (8 marks)

- Q3** (a) If $v(t) = 160\cos(50t)V$ and $i(t) = -20\sin(50t - 30^\circ)A$, calculate the instantaneous power and the average power. (3 marks)
- (b) The Thevenin impedance of a source is $Z_{TH} = 120 + j60\Omega$, while the peak Thevenin voltage is $V_{TH} = 110 + j0V$. Determine the maximum available average power from the source. (3 marks)
- (c) Calculate the effective value of the voltage waveform in **Figure Q3 (c)**. (4 marks)
- (d) For the entire circuit in **Figure Q3 (d)**, calculate
- (i) the power factor (1 mark)
 - (ii) the average power delivered by the source (1 mark)
 - (iii) the reactive power (1 mark)
 - (iv) the apparent power (1.5 marks)
 - (v) the complex power (1.5 marks)
- (e) Determine the value of parallel capacitance needed to correct a load of 140 kVAR at 0.85 lagging pf to unity pf. Assume that the load is supplied by a 110-V (rms), 60-Hz line. (9 marks)
- Q4** (a) Provide **TWO (2)** advantages of a three phase circuit? (2 marks)
- (b) If $V_{ab} = 4000V$ in a balanced Y-connected three-phase generator, identify the phase voltages, assuming the phase sequence is:
- (i) abc (2.5 marks)
 - (ii) acb (2.5 marks)
- (c) A positive-sequence, balanced Δ -connected source supplies a balanced Δ -connected load. If the impedance per phase of load is $18 + j12\Omega$ and $I_a = 19.202 \angle 35^\circ A$, calculate I_{AB} and V_{AB} . (6 marks)

- (d) Refer to the circuit in **Figure Q4 (d)**. Determine the total average power, reactive power and complex power at the source and at the load. (6 marks)
- (e) The unbalanced Y-load of **Figure Q4 (e)** has balanced voltages of 100 V and the *acb* sequence. Calculate the line currents and the neutral current. Take $Z_A = 15\Omega$, $Z_B = 10 + j5\Omega$ and $Z_C = 6 - j8\Omega$. (6 marks)

- Q5** (a) Determine the voltage V_o in the circuit of **Figure Q5 (a)**. (5 marks)
- (b) Consider the circuit in **Figure Q5 (b)**. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time $t = 1$ s if $v(t) = 60\cos(4t + 30^\circ)$ V (10 marks)
- (c) Compute the input impedance of the circuit in **Figure Q5 (c)** and the current from voltage source. (5 marks)
- (d) The primary current to an ideal transformer rated at 3300/110 V is a 5 A. Calculate
- (i) the turns ratio (1.5 marks)
 - (ii) the kVA rating (1.5 marks)
 - (iii) the secondary current. (2 marks)

- END OF QUESTION -

TERBUKA


FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

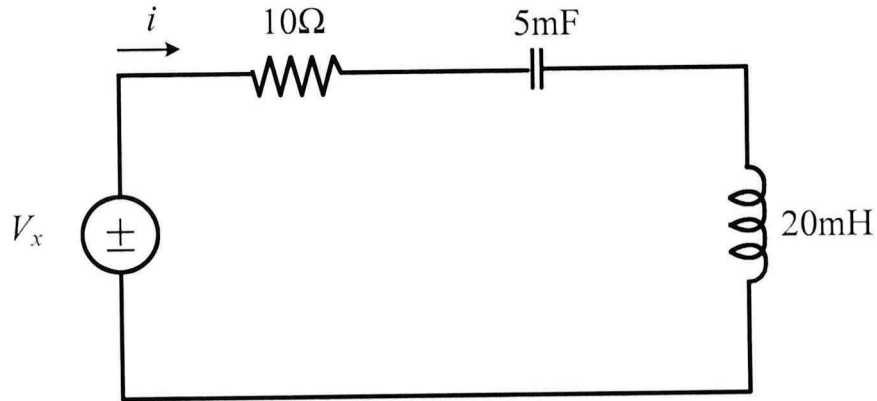

Figures Q1(d)

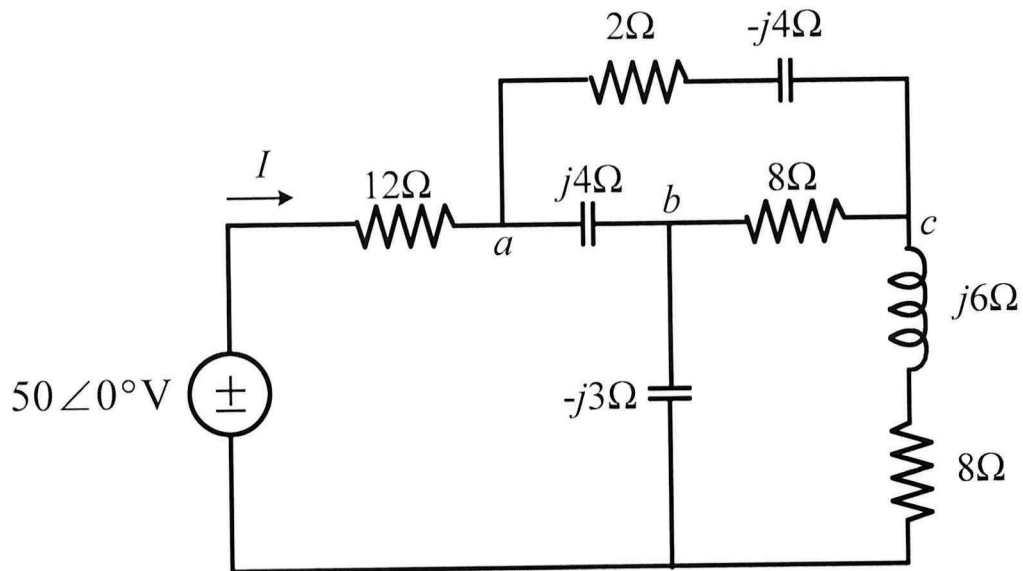


Figure Q1 (e)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

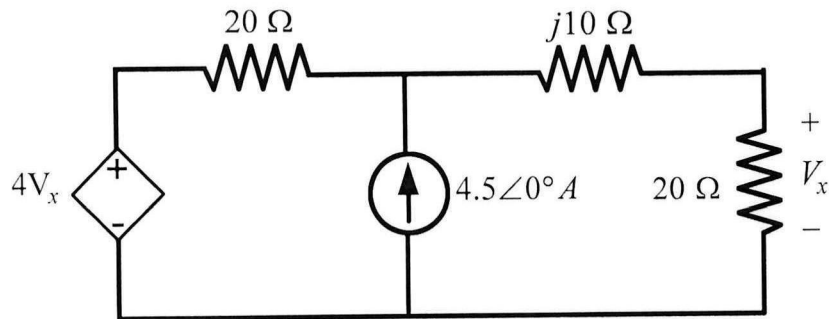


Figure Q2 (a)

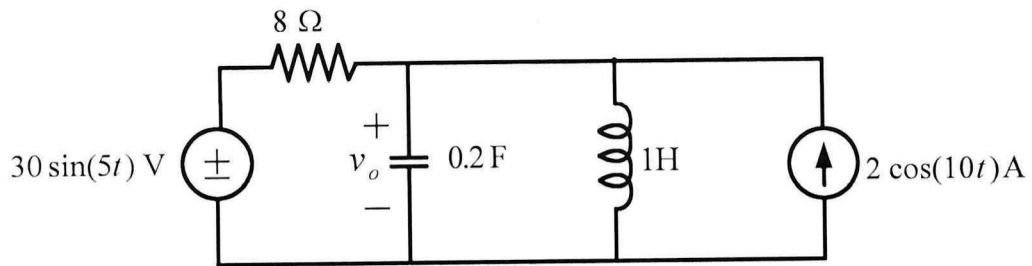


Figure Q2 (b)

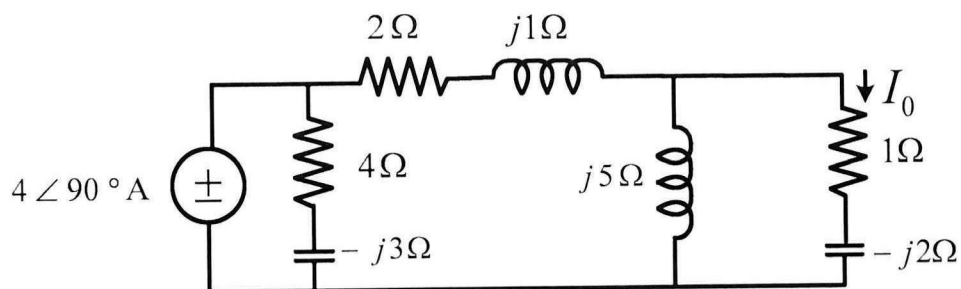


Figure Q2 (c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

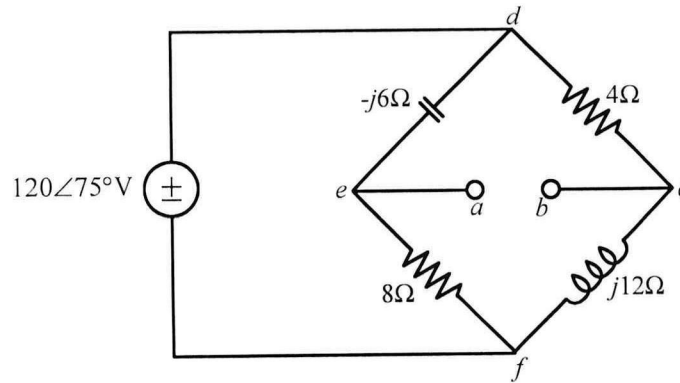


Figure Q2 (d)

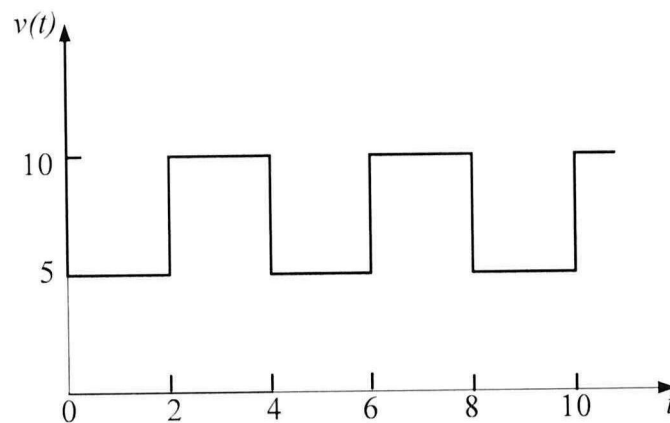


Figure Q3 (c)

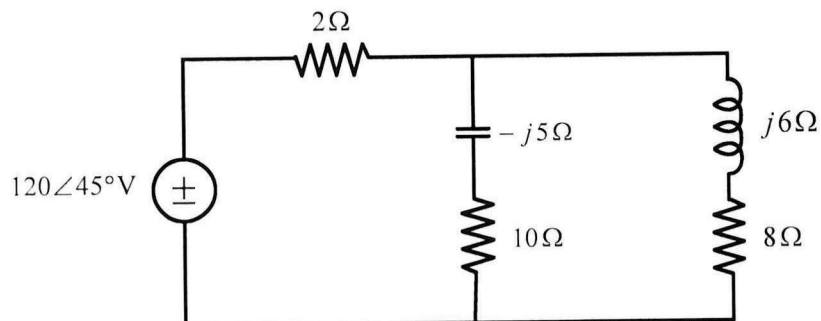


Figure Q3 (d)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

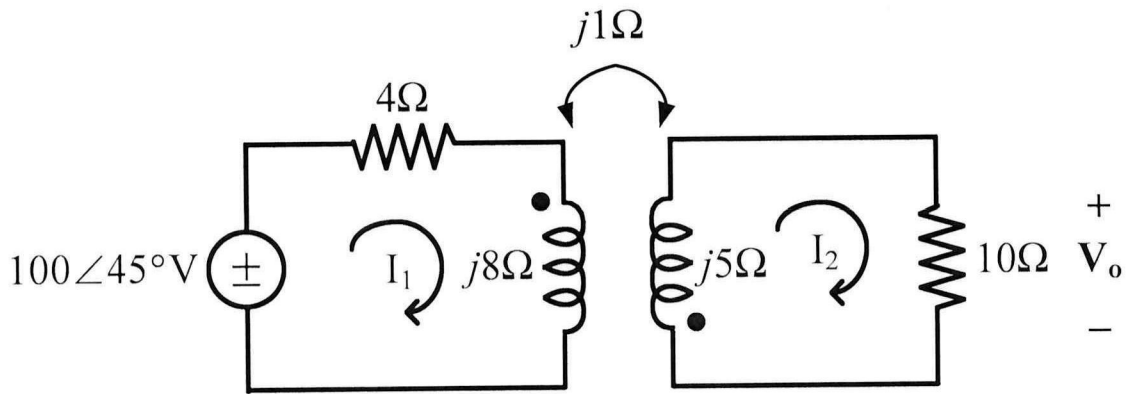


Figure Q5 (a)

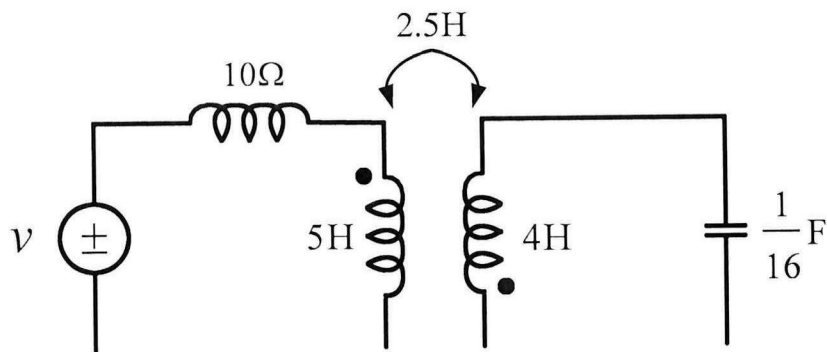


Figure Q5 (b)

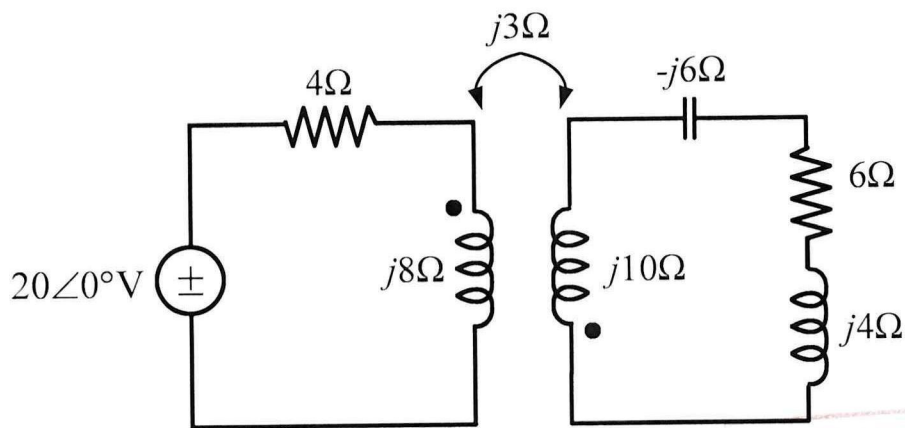


Figure Q5 (c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Chapter 1***A general expression for the sinusoid***

Frequency: $f = \frac{1}{T}$ Hz

Angular frequency: $\omega = 2\pi f$ Hz

Trigonometric identities

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

Mathematic operation of complex number

Addition: $z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$

Subtraction: $z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$

Multiplication: $z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$

Division: $\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$

Reciprocal: $\frac{1}{z} = \frac{1}{r} \angle -\phi$

Square root: $\sqrt{z} = \sqrt{r} \angle \phi/2$

Complex conjugate: $z^* = x - jy = r \angle -\phi = r e^{-j\phi}$

Euler's identity: $e^{\pm j\phi} = \cos \phi \pm j \sin \phi$

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Summary of voltage-current relationship		
Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

Impedances and admittances of passive elements		
Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

Relationship between differential, integral operation in phasor listed as follow:

$$v(t) \rightarrow V = V \angle \phi$$

$$\frac{dv}{dt} \rightarrow j\omega V$$

$$\int v dt \rightarrow \frac{V}{j\omega}$$

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303


Chapter 2

Superposition Theorem


When a circuit has sources operating at different frequencies,

- The separate phasor circuit for each frequency must be solved independently,
- The total response is the sum of time-domain responses of all the individual phasor circuits.

Thevenin and Norton Equivalent Circuits

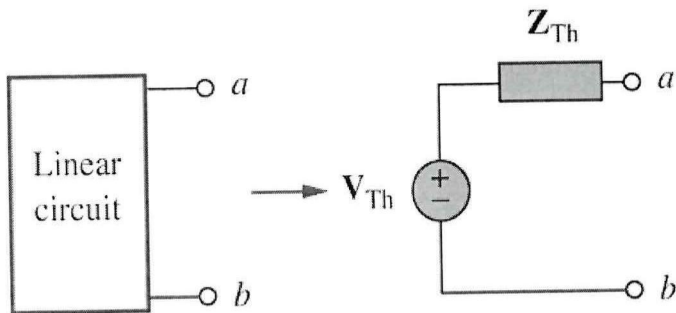

Thevenin transform

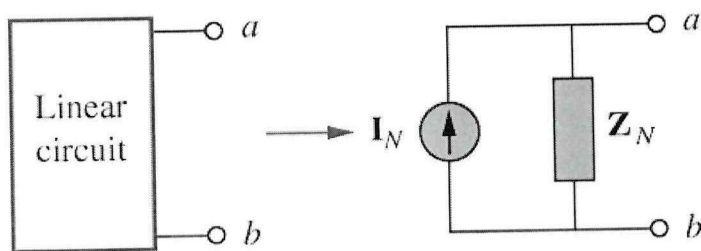

Norton transform

TERBUKA

FINAL EXAMINATION


SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Source Transformation

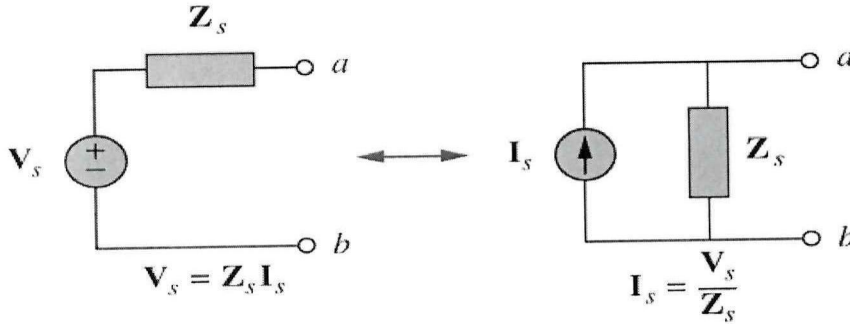

Chapter 3

Average of Instantaneous Power:
$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Load Impedance:
$$Z_L = Z_{TH} = R_{TH} + jX_{TH}$$

$$Z_{TH}^* = R_{TH} - jX_{TH}$$

Maximum Average Power:
$$P_{max} = \frac{|V_{TH}|^2}{8 R_{TH}}$$

If the load is purely real :
$$R_L = \sqrt{R_{TH}^2 + X_{TH}^2} = |Z_{TH}|$$

Effective Current:
$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{rms}$$

The rms value of a sinusoid $i(t) = I_m \cos(\omega t)$ is given by:
$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

TERBUKA

The average power can be written in terms of the rms values:

$$I_{eff} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II


COURSE CODE : BNR 10303

Apparent Power and Power Factor:

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$

Apparent Power, S Power Factor, pf

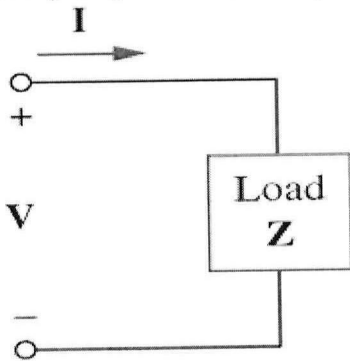Complex power S is the product of the voltage and the complex conjugate of the current:



$$V = V_m \angle \theta_v \quad I = I_m \angle \theta_i$$

$$\frac{1}{2} V I^* = V_{rms} I_{rms} \angle \theta_v - \theta_i$$

$$S = \underbrace{V_{rms} I_{rms} \cos(\theta_v - \theta_i)}_P + j \underbrace{V_{rms} I_{rms} \sin(\theta_v - \theta_i)}_{+j Q}$$

P: is the average power in watts delivered to a load and it is the only useful power.
 Q: is the reactive power exchange between the source and the reactive part of the load. It is measured in VAR.

- Q = 0 for *resistive loads* (unity pf).
- Q < 0 for *capacitive loads* (leading pf).
- Q > 0 for *inductive loads* (lagging pf).

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Average Power Absorbed: $P = I_{rms}^2 R = \frac{V_{rms}^2}{R}$

Conservation of AC Power : $\bar{S} = \frac{1}{2} \overline{V I^*} = \frac{1}{2} \overline{V (I_1^* + I_2^*)} = \frac{1}{2} \overline{V I_1^*} + \frac{1}{2} \overline{V I_2^*} = \bar{S}_1 + \bar{S}_2$

Power Factor Correction : $C = \frac{Q_c}{\omega V_{rms}^2} = \frac{P (\tan \theta_1 - \tan \theta_2)}{\omega V_{rms}^2}$

$Q_c = Q_1 - Q_2$, $Q_1 = S_1 \sin \Theta_1 = P \tan \Theta_1$, $Q_2 = P \tan \Theta_2$

Chapter 4

The voltages can be expressed in phasor form as

$V_{an} = 200 \angle 10^\circ V$

$V_{bn} = 200 \angle -230^\circ V$

$V_{cn} = 200 \angle -110^\circ V$

A balanced Y-Y system

$V_L = \sqrt{3} V_p$, where

$V_p = |V_{an}| = |V_{bn}| = |V_{cn}|$

$V_L = |V_{ab}| = |V_{bc}| = |V_{ca}|$

A balanced Y-Δ system

$I_L = \sqrt{3} I_p$, where

$I_L = |I_a| = |I_b| = |I_c|$

$I_p = |I_{AB}| = |I_{BC}| = |I_{CA}|$

Power loss in a single-phase system: $P'_{loss} = 2R \frac{P_L^2}{V_L^2}$

Power loss in a three-phase system: $P'_{loss} = R' \frac{P_L^2}{V_L^2}$

Unbalanced Three-Phase Systems:

$I_a = \frac{V_{AN}}{Z_A}$, $I_b = \frac{V_{BN}}{Z_B}$, $I_c = \frac{V_{CN}}{Z_C}$,

$I_n = -(I_a + I_b + I_c)$



FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Summary of phase and line voltages/currents for balanced three-phase system

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ <p>Same as line currents</p>	$V_{ab} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{ab} \angle +120^\circ$ $I_a = \frac{V_{an}}{Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Y-Δ	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ $I_{AB} = \frac{V_{AB}}{Z_\Delta}$ $I_{BC} = \frac{V_{BC}}{Z_\Delta}$ $I_{CA} = \frac{V_{CA}}{Z_\Delta}$	$V_{ab} = V_{AB} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ-Δ	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ $I_{AB} = \frac{V_{ab}}{Z_\Delta}$ $I_{BC} = \frac{V_{bc}}{Z_\Delta}$ $I_{CA} = \frac{V_{ca}}{Z_\Delta}$	<p>Same as phase voltages</p> $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020


PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II


COURSE CODE : BNR 10303

Δ -Y	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ Same as line currents	Same as phase voltages $I_a = \frac{V_p \angle -30^\circ}{\sqrt{3}Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
-------------	--	--

Chapter 5

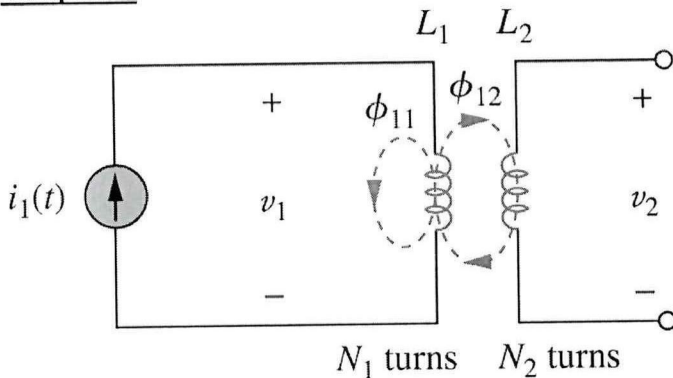

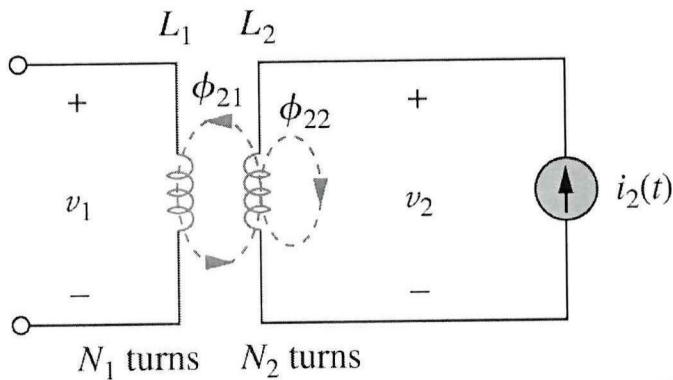The open-circuit mutual voltage across coil 2: $v_2 = M_{21} \frac{di_1}{dt}$



The open-circuit mutual voltage across coil 1: $v_1 = M_{12} \frac{di_2}{dt}$

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020

PROGRAMME CODE : BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Series-Aiding Connection: $L = L_1 + L_2 + 2M$

Series-Opposing Connection $L = L_1 + L_2 - 2M$

Coefficient of Coupling k : $M = k\sqrt{L_1L_2}$

Instantaneous Energy Stored: $w = \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 \pm MI_1I_2$

TERBUKA