



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2019/2020**

COURSE NAME : ELECTRONICS CIRCUITS AND
DEVICES/ ELECTRONICS
PRINCIPLE/ ELECTRONICS
PRINCIPLE I

COURSE CODE : BNR 25803/ BNR 20503/ BNR 27103

PROGRAMME CODE : BND / BNE / BNF

EXAMINATION DATE : DECEMBER 2019/ JANUARY 2020

DURATION : 3 HOURS

INSTRUCTION : ANSWER ALL QUESTIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF **FIVE (5)** PAGES

- Q1**
- (a) Define extrinsic semiconductors. (2 marks)
 - (b) Distinguish **TWO (2)** differences between n-type and p-type semiconductors. (4 marks)
 - (c) Draw relevant energy level diagrams of n-type and p-type semiconductors. (4 marks)
 - (d) Explain **TWO (2)** reasons a pure semiconductor behaves like an insulator at absolute zero temperature. (4 marks)
 - (e) Photodiode is usually operated under reverse biased condition.
 - (i) Define reverse biased condition (2 marks)
 - (ii) Sketch voltage-current graph for the reverse biased p-n junction (3 marks)
 - (f) With the help of a circuit diagram, explain how to use zener diode as a voltage regulator. (6 marks)
- Q2**
- (a) Sketch current-voltage (IV) characteristic of forward-biased and reverse-biased p-n junction practical diode. (7 marks)
 - (b) Calculate the current for the circuit in **Figure Q2 (b)**. (8 marks)
 - (c) Illustrate and completely label the output waveform for the circuits as shown in **Figure Q2 (c)**. Assume all the diodes are Silicon with clipping applications. Show all steps in obtaining the waveforms. (10 marks)
- Q3**
- (a) Design a voltage divider bias circuit in **Figure Q3 (a)** having $I_{BQ} = 60\mu A$, $V_E = 0.1V_{CC}$ and $I_{C_{sat}} = 8mA$ with $R_1 = 47k\Omega$ and $R_2 = 4.7k\Omega$. The supply voltage is 20V. Assume $\beta_{RE} \geq 10R_2$.
 - (b) Sketch the DC load line and determine the Q-points, I_{CQ} and V_{CEQ} .
 - (c) If β is changed two times than previous, construct the new Q-point and calculate the % of changes in the I_c and V_{CE}
- (25 marks)

TERBUKA

Q4 (a) List the comparison between BJT and MOSFET. (10 marks)

(b) Consider NMOS circuit in **Figure Q4 (b)** with $K = 0.25 \text{ mA/V}^2$ and $V_t = 2 \text{ V}$. Find V_o when $V_i = 0, 6, \text{ and } 12 \text{ V}$ for $R_D = 1 \text{ K}$ and $V_{DD} = 12 \text{ V}$. Find the status circuit of each V_i . (15 marks)

- END OF QUESTIONS -

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020
COURSE NAME : ELECTRONICS PRINCIPLE I

PROGRAMME CODE : BND / BNE / BNF
COURSE CODE : BNR 27103

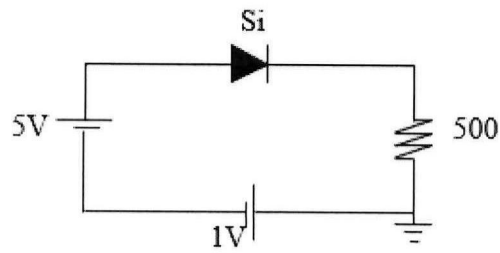


Figure Q2 (b)

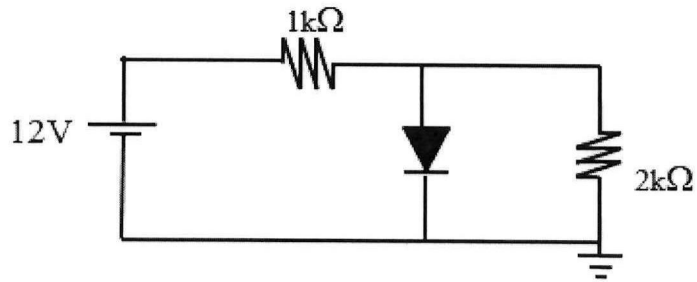


Figure Q2 (c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020
 COURSE NAME : ELECTRONICS PRINCIPLE I

PROGRAMME CODE : BND / BNE / BNF
 COURSE CODE : BNR 27103

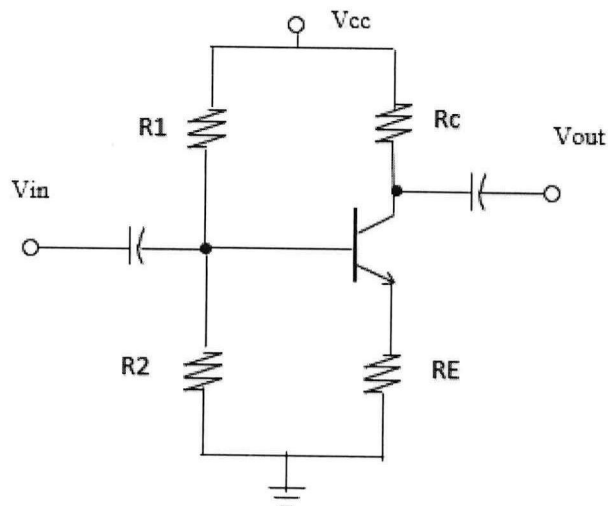


Figure Q3 (a)

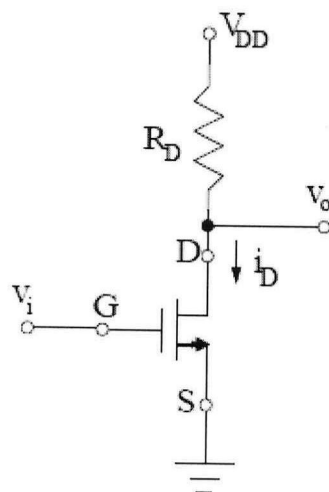


Figure Q4 (b)

TERBUKA