

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2012/2013**

COURSE NAME : ELECTRICAL MACHINES AND DRIVES

COURSE CODE : DEK 3143 / DAE 32303

PROGRAMME : 3 DET/ DAE/ DAL

EXAMINATION DATE : OCTOBER 2012

DURATION : 3 HOURS

INSTRUCTIONS : ANSWER **FOUR (4)** QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF FOUR (4) PAGES

CONFIDENTIAL

- Q1 (a) With the help of drawings, describe the physical construction of a DC machines.

(5 marks)

- (b) A compound DC motor rated at 240 V, 50 Hz, 1800 rpm has armature resistance, 0.2Ω , series field resistance, 0.6Ω and shunt field resistance, 120Ω . The rotational losses are 150 W. The full load line current is 40 A.

- (i) Find the back emf, E_c
- (ii) Find the developed mechanical power, P_{mech}
- (iii) Find the output power, P_{out}
- (iv) Find the output torque, τ_{out}
- (v) Find the efficiency of the motor, η
- (vi) Draw the power flow diagram for this type of motor

(20 marks)

- Q2 (a) The following test results were obtained for a 20 kVA, 50 Hz, 2400/240 V distribution transformer as tabulated below. Assuming step-down operation, supplying a rated load at 0.85 lagging power factor, determine the voltage regulation referred to the high voltage side.

Table Q2(a) : Data of short-circuit and open-circuit test

Short-Circuit	Open-Circuit
$V_{\text{sc}} = 57.5 \text{ V}$	$V_{\text{oc}} = 240 \text{ V}$
$I_{\text{sc}} = 8.34 \text{ A}$	$I_{\text{oc}} = 1.066 \text{ A}$
$P_{\text{sc}} = 284 \text{ W}$	$P_{\text{oc}} = 126.6 \text{ W}$

(25 marks)

- Q3 (a) With the help of drawings, explain briefly the derivation of
- (i) the applied voltage and induced voltage transformation of an ideal transformer,
 - (ii) the current transformation of an ideal transformer
 - (iii) the impedance transformation of an ideal transformer.

(10 marks)

- (b) The purpose of open circuit and short circuit test is to determine the shunt and series branch parameter of a practical transformer. Briefly explain open circuit and short circuit test to determine circuit parameter of the practical transformer.

(15 marks)

- Q4** (a) A 415 V, 50 Hz, 20hp, 3-phase, star connection, 4-poles, induction motor has the following impedances in ohms per phase referred to the stator circuit:

$$\begin{array}{ll} R_s = 0.65\Omega & R_R = 0.45\Omega \\ X_s = 1.25\Omega & X_R = 0.65\Omega \\ R_C = \infty & X_m = 25\Omega \end{array}$$

At full load condition, the rotational losses are 1.2 kW and assumed to be constant. The core loss is lumped in with the rotational losses. For a rotor slip of 3% at the rated voltage and rated frequency, using approximate equivalent circuit, find the motor's

- (i) Speed
- (ii) Stator current
- (i) Power factor
- (ii) Input power
- (iii) Air gap power
- (iv) Converted power
- (v) Torque induced by the motor
- (vi) Load torque
- (vii) Efficiency
- (viii) Power flow diagram

(25 marks)

- Q5** (a) With the help of a phasor diagram, outline the three loading conditions of the synchronous motor.

(9 marks)

- (b) A 2300V 100hp, 50Hz, eight pole, star connected synchronous motor has a rated power factor of 0.8 leading. Motor operate at rated load of efficiency is 0.85 percent. The armature resistance is 1.1 Ω /phase and synchronous inductance is 63.666 mH/phase. Find the following quantities for this machine when it is operating at full load.

- (i) output torque
- (ii) input power
- (iii) The induced emf per phase
- (iv) Converted power
- (v) The voltage regulation
- (vi) Draw the phasor diagram.

(16 marks)

Q6 (a) Describe the following aspect of a Stepper motor.

- (i) The physical construction of the motor
- (ii) The performance of the motor

(12 marks)

(b) Illustrate the following with regard to a Reluctance Motor

- (i) The constructional design of the motor
- (ii) The operating fundamentals of the motor

(13 marks)