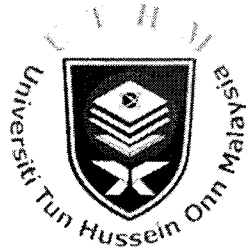


CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2012/2013**

COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY

COURSE CODE : BDA14303 / BEX17003 / BEE1803

PROGRAMME : BDD

EXAMINATION DATE : JUNE 2013

DURATION : 3 HOURS

INSTRUCTIONS : 1. **SECTION A** CONSIST OF **TWO(2)** QUESTIONS. ANSWER **ALL** QUESTIONS.
2. **SECTION B** CONSISTS OF **FIVE(5)** QUESTIONS. ANSWER ANY **THREE(3)** QUESTIONS.

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

CONFIDENTIAL

PART A (ANSWER ALL QUESTIONS)

- Q1** (a) State the difference between direct current and alternating current with the aid of suitable figures.

(4 marks)

- (b) In an electrochemistry cell consists of two electrodes immersing in an ionic solution and the two electrodes (cathodes and anodes) are connected to the positive and negative terminals of a battery. The current flowing through the electrodes is

$$i(t) = \begin{cases} 2A, & 0 < t < 2 \\ 5e^{-2t}, & t > 2 \end{cases}$$

- (i) Determine the charge entering the cell from $t = 0$ s to $t = 3$ s

(6 marks)

- (ii) If the energy to move the charge from one electrode to another electrode is 30J, find the voltage drop across the two electrodes.

(2 marks)

- (c) Referring to **Figure Q1(c)**, calculate the power absorbed by each resistors.

(8 marks)

- Q2** (a) Referring to **Figure Q2(a)**, how many branches and nodes does the circuit have?

(2 marks)

- (b) Define Kirchoff's Voltage Law (KVL).

(2 marks)

- (c) For the circuit in **Figure Q2(c)**, determine:

- (i) Equivalent resistance

(2 marks)

- (ii) Total current

(2 marks)

- (iii) Currents through each resistor

(2 marks)

- (iv) Power for each element

(2 marks)

- (v) Power supply by the source

(2 marks)

- (d) Apply mesh analysis to find V_o in the circuit of **Figure Q2(c)**.

(6 marks)

PART B (ANSWER ANY THREE (3) QUESTIONS)

Q3 (a) Capacitor is one of the energy storage elements in electrical circuit. Explain with the aid of suitable figures and/or equation for the following questions:

(i) Construction of capacitor. (2 marks)

(ii) Calculate the amount of charge stored if a $0.01\mu\text{F}$ capacitor is supplied with a 9V voltage source. (3 marks)

(iii) Determine the current through a $200\mu\text{F}$ capacitor whose voltage is shown in **Figure Q3(a)(iii)** below and draw the resultant current. Given that,

$$V(t) = \begin{cases} 50t \text{ V} & 0 < t < 1 \\ 100 - 50t \text{ V} & 1 < t < 3 \\ -200 + 50t \text{ V} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases} \quad (9 \text{ marks})$$

(b) Determine the equivalent inductors for the circuit in **Figure Q3(b)** and then find the total voltage from $t = 1\text{s}$ to $t = 2\text{s}$. Given that the current is $i(t) = (2 - 2e^{-t})\text{A}$. (6 marks)

Q4 (a) Explain the following terms.

(i) Magnetomotive force (MMF) (2 marks)

(ii) Magnetic flux (2 marks)

(iii) Reluctance (2 marks)

(b) Draw with a diagram to explain how a magnetic field is generated when a current passes through a conductor. (2 marks)

(c) An iron ring of mean diameter 15 cm and 10 cm^2 in cross-section is wound with 200 turns of wire. There is an air gap of 2 mm cut in the ring. For a flux density of 1 Wb/m^2 and a relative permeability of 500;

(i) Draw the schematic diagram of this ring and the configuration. (2 marks)

(ii) Determine the exciting current, inductance and the stored energy. (10 marks)

- Q5** (a) Explain the importance of power factor in power delivery. (2 marks)
- (b) A current source of $i(t) = 1.789 \cos(4t + 26.57^\circ)$ A is applied to a single element load. The resulting voltage across the element is $v(t) = 4.47 \cos(4t - 63.43^\circ)$ v.
- (i) What type of element is this? Calculate its value. (6 marks)
- (ii) Which signal leads and by how much? (2 marks)
- (c) A sinusoidal voltage is applied to the AC circuit in **Figure Q5(c)**.
- (i) Find the output power of the voltage source. (8 marks)
- (ii) Find the power dissipation in resistor, R_1 and R_2 . (2 marks)
- Q6** (a) Define the term of AC Motor? (2 marks)
- (b) Give **ONE (1)** advantage of AC motor compare to DC motor? (2 marks)
- (c) List **ONE (1)** way to increase the turning force (or torque) that the DC motor can create. (2 marks)
- (d) Define the following DC motor term as below:
- (i) Armature (2 marks)
- (ii) Commutator (2 marks)
- (iii) Brushes (2 marks)
- (e) Give **TWO (2)** examples DC motor for
- (i) residential and commercial (2 marks)
- (ii) industrial (2 marks)

- (f) A three-phase 300V, 60 Hz, six pole, induction motor delivers 10kW at a slip of 3%.

Calculate:

(i) synchronous speed (2 marks)

(ii) rotor speed (2 marks)

- Q7** (a) Use diagram to show electron flow of a diode when it is forward biased.

(3 marks)

- (b) Draw a I-V characteristic curve of the diode and explain the operation of the diode.

(4 marks)

- (c) A 5V D C supply is required to power a microcontroller in a device. Sketch the schematic diagram of the DC power supply circuit and the clean output waveforms. Explain the function of each component sketched.

(8 marks)

- (d) Explain why analog-to-digital converter is needed in many electronic circuit applications.

(5 marks)

-END OF QUESTION-

FINAL EXAMINATION

SEMESTER/SESSION : II/2012/2013
COURSE NAME : ELECTRICAL & ELECTRONIC TECHNOLOGY

PROGRAMME : BDD
COURSE CODE : BDA14303 /
BEX 17003/BEE1803

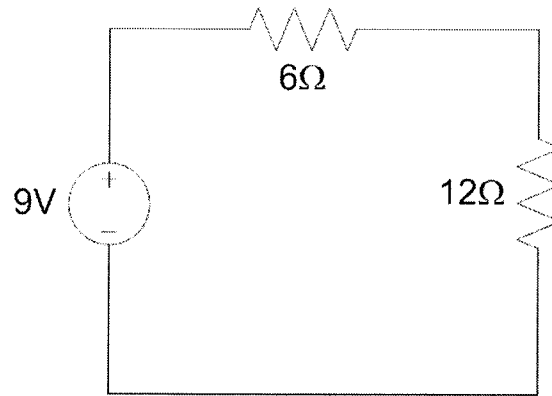


FIGURE Q1(c)

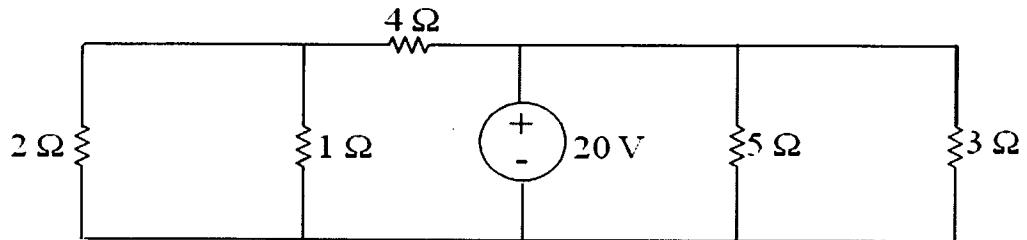


FIGURE Q2(a)

FINAL EXAMINATION

SEMESTER/SESSION : II/2012/2013
 COURSE NAME : ELECTRICAL & ELECTRONIC TECHNOLOGY

PROGRAMME : BDD
 COURSE CODE : BDA14303 /
 BEX17003/BEE1803

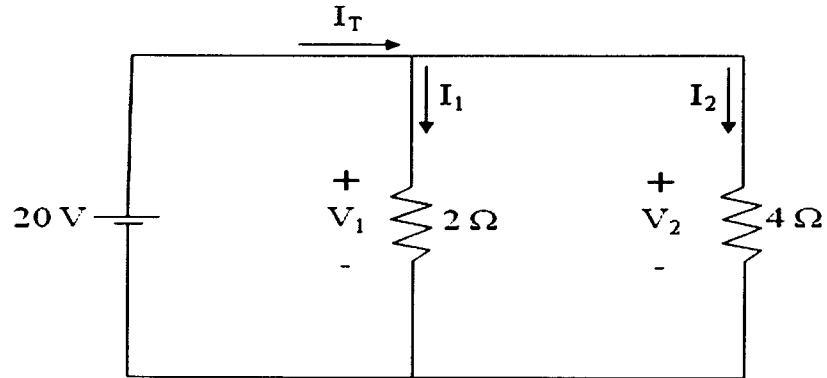


FIGURE Q2(b)

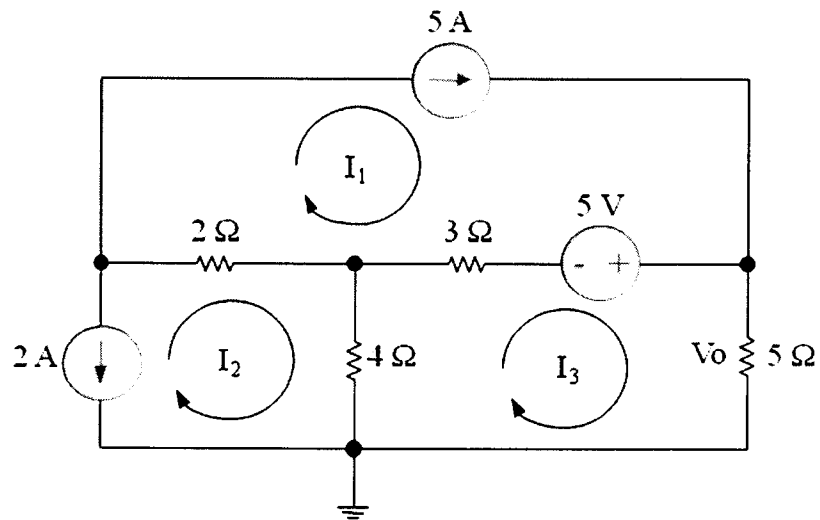


FIGURE Q2(c)

FINAL EXAMINATION

SEMESTER/SESSION : II/2012/2013
 COURSE NAME : ELECTRICAL & ELECTRONIC TECHNOLOGY

PROGRAMME : BDD
 COURSE CODE : BDA14303 /
 BEX17003/ BEE1803

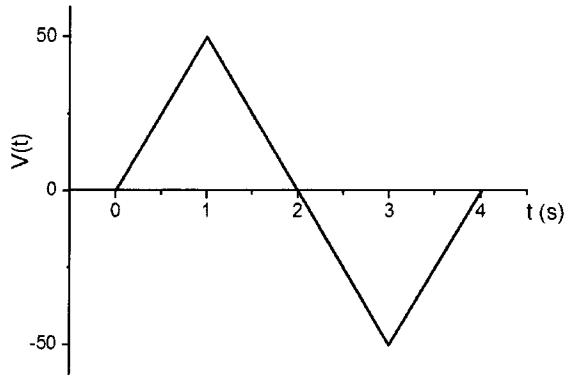


FIGURE Q3(a)(iii)

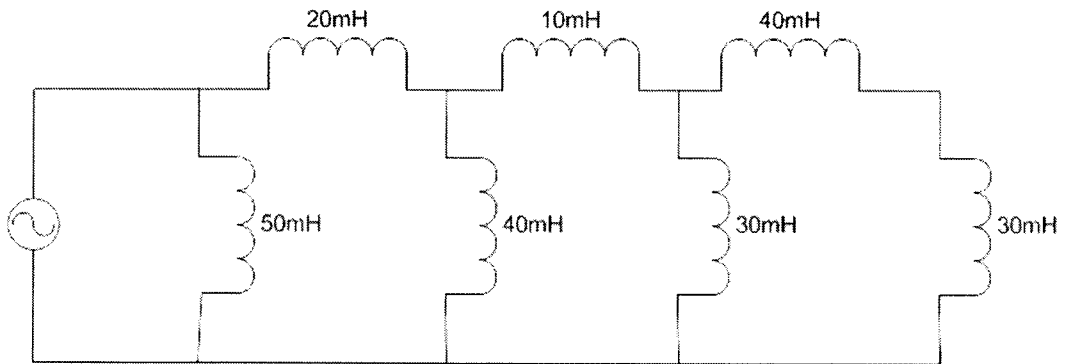


FIGURE Q3(b)

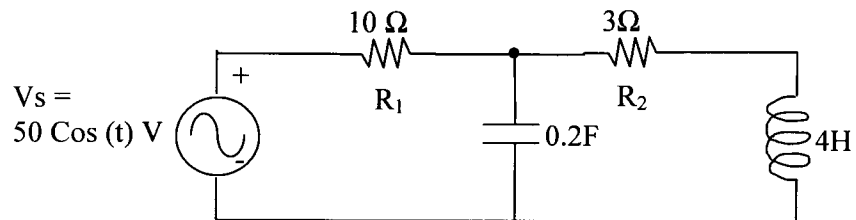


FIGURE Q5(c)