

SULIT



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**PEPERIKSAAN AKHIR
SEMESTER III
SESI 2012/2013**

NAMA KURSUS : ELECTRICAL TECHNOLOGY
AND MICRO PROCESSING

KOD KURSUS : DAJ 32302

PROGRAM : DAJ

TARIKH PEPERIKSAAN : MEI 2013

JANGKA MASA : 2 JAM

ARAHAN : JAWAB LIMA (4) SOALAN
DARIPADA ENAM (6) SOALAN

KERTAS SOALAN INI MENGANDUNGI TUJUH (7) MUKA SURAT BERCETAK

SULIT

SOALAN DI DALAM BAHASA MELAYU

- Q1** (a) Berikan perbezaan di antara semikonduktor jenis-P dan jenis-N, termasuk gambaran struktur atom.

(10 markah)

- (b) Lukis dan terangkan rektifikasi gelombang penuh menggunakan kapasitor pelicinkan dengan beban rintangan dan mencari satu ungkapan untuk faktor riak merentasi beban.

(10 markah)

- Q2** (a) Andaikan diod adalah diod-kuasa rendah dengan nilai rintangan hadapan 6 ohm seperti yang ditunjukkan dalam **Rajah S1**. Potensi voltan halangan masih: $V_{\phi} = 0.45 \text{ volt}$ (khas untuk diod germanium) Tentukan nilai I_D jika $V_A = 6 \text{ volt}$.

(15 markah)

- (b) Senaraikan tiga jenis diod dan kegunaannya dalam litar elektronik.

(5 markah)

- Q3** (a) Lukis rekabentuk untuk pemandu motor dc menggunakan empat transistor NPN. Jelaskan aliran arus pemandu dan arah motor.

(20 markah)

- Q4** (a) Terangkan perbezaan besar antara mikropemproses dan mikropengawal, termasuk ciri-ciri tipikal mikropengawal.

(15 markah)

- (b) Terangkan faedah utama dan had menggunakan mikropengawal.

(5 markah)

Q5 (a) Jelaskan organisasi asas memori data PIC.

(10 markah)

(b) Jelaskan organisasi asas timbunan PIC.

(10 markah)

Q6 (a) Merujuk kepada litar dalam **Rajah Q2**, apakah tujuan litar RC yang disambungkan ke input RESET mikropengawal.

(5 markah)

(b) Apakah kesan melaksanakan arahan berikut

```
movlw    b'11110000'  
movwf   trisb
```

(10 markah)

(c) Menganggap bahawa kod berikut baru sahaja dilaksanakan. Apa kandungan biner daftar kerja.

```
movlw   2f  
addlw  55
```

(5 markah)

SOALAN DI DALAM BAHASA INGGERIS

- Q1** (a) Give the differences between P-type and N-type semiconductors. Include atomic structure illustration.

(10 marks)

- (b) Draw and explain full wave rectifier using a smoothing capacitor with a resistance load and find an expression for ripple factor across load.

(10 marks)

- Q2** (a) Assume the diode is a low-power diode with a forward resistance value of 6 ohms as shown in **FIGURE Q1**. The barrier potential voltage is still: $V_{\phi} = 0.45$ volts (typical for a germanium diode) Determine the value of I_D if $V_A = 6$ volts.

(15 marks)

- (b) List down the three types of diodes and their uses in electronic circuit.

(5 marks)

- Q3** (a) Draw the design for dc driver motor using four NPN transistors. Describe the driver current flow and motor direction.

(20 marks)

- Q4** (a) Explain the major differences between a microprocessor and a microcontroller, including the typical features of a microcontroller.

(15 marks)

- (b) Explain the major benefits and limitations of using a microcontroller.

(5 marks)

Q5 (a) Explain the basic organization of the PIC data memory. (10 marks)

(b) Explain the basic organization of the PIC stack. (10 marks)

Q6 (a) For the following circuit in **FIGURE Q2**, what is the purpose of RC circuit that is connected to the RESET input of the microcontroller. (5 marks)

(b) What is the effect of executing the following instructions?

```
movlw    b'11110000'  
movwf   trisb
```

(10 marks)

(c) Assume that the following code has just been executed. What the binary content of the working register.

```
movlw   2f  
addlw  55
```

(5 marks)

- END OF QUESTION -

PEPERIKSAAAN AKHIR
FINAL EXAMINATION

SEMESTER / SESI : SEM III / 2012/2013

SEMESTER / SESSION

KURSUS : ELECTRICAL TECHNOLOGY


COURSE & MICRO C

PROGRAM : 1 DAJ

PROGRAMME

KOD KURSUS : DAJ32302

COURSE CODE

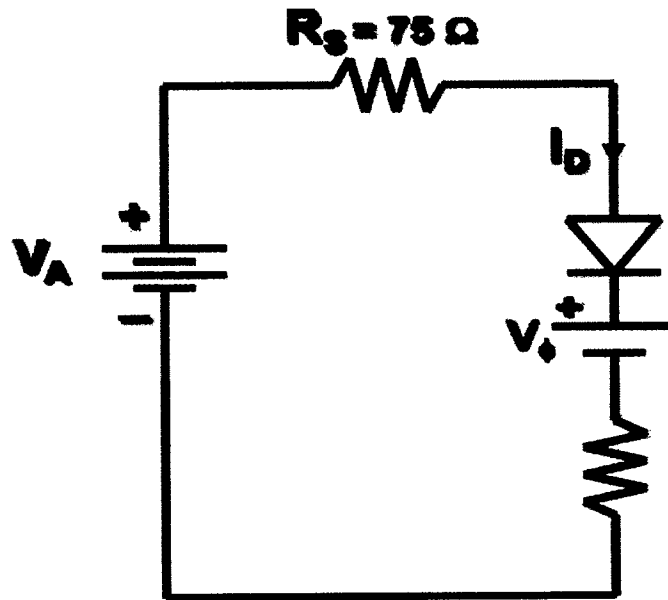

RAJAH S1 / FIGURE Q1


PEPERIKSAAAN AKHIR
FINAL EXAMINATION

SEMESTER / SESI : SEM III / 2012/2013
SEMESTER / SESSION

PROGRAM : 1 DAJ
PROGRAMME

KURSUS : ELECTRICAL TECHNOLOGY
COURSE **& MICRO C**

KOD KURSUS : DAJ32302
COURSE CODE

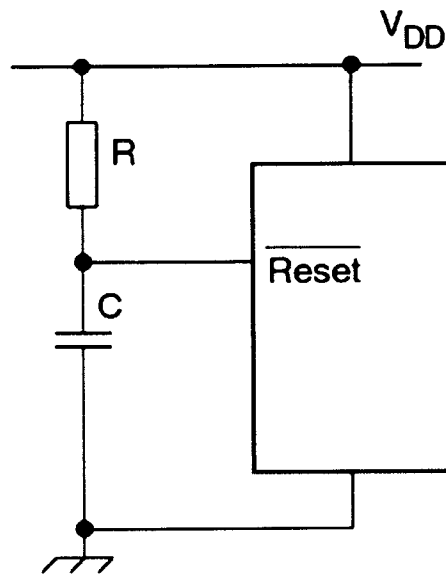

RAJAH S2 / FIGURE Q2