

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION SEMESTER I SESSION 2018/2019

COURSE NAME

ELECTRICAL & ELECTRONIC

TECHNOLOGY

COURSE CODE

: BDU10803

PROGRAMME

BDC/BDM

EXAMINATION DATE

DECEMBER 2018/JANUARY 2019

DURATION

3 HOURS

:

INSTRUCTION

ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF EIGHT (8) PAGES

TERBUKA

CONFIDENTIAL

CONFIDENTIAL

BDU10803

Q1	(a)	State the function of inductor and the SI unit of inductance. (2	marks)
	(b)	Find L_{eq} at the terminal a-b of the circuit in Figure Q1(b) . (5	marks)
	(c)	Consider the circuit in Figure Q1(c). Under DC conditions, find;	
		(i) current, i , (1)	mark)
		(ii) voltage, v_c , (1	mark)
		(iii) current, i_L , (1	mark)
		(iv) the energy stored in the capacitor and inductor. (4)	marks)
	(d)	Referring to the circuit in Figure Q1(d) ;	
		(i) Express the Kirchoff Voltage Law (KVL) equation. (2)	marks)
		(ii) Determine the value of current, <i>I</i> .	marks)
		(iii) Find the voltage drop across resistor 3 Ω , v_I .	marks)
	(e)	(i) Describe the differences between nodal analysis and mesh analysis.	marks)
		(ii) Determine the voltages at the nodes in Figure Q1(e)(ii) using nodal analysis.	marks)
Q2	(a)	By applying Superposition theorem, find the current, i_T and the voltage, v_T for the circuit given in Figure Q2(a) .	

(8 marks)



CONFIDENTIAL

BDU10803

- (b) Consider the circuit in Figure Q2(b) and calculate;
 - (i) The venin resistance, R_{Th} ,

(2 marks)

(ii) Thevenin voltage, V_{Th} ,

(5 marks)

(iii) value of R_L for maximum power transfer,

(1 mark)

(iv) maximum power, P_{max} .

(2 mark)

- Q3 (a) Apply DeMorgan's theorem to each of the following expressions:
 - (i) $\overline{(A+B+C)D}$

(4 marks)

(ii) $\overline{AB} + \overline{CD} + EF$

(4 marks)

- (b) Referring to the logic diagram in Figure Q3(b);
 - (i) Write Boolean expression;

(3 marks)

(ii) Develop a truth table from the Boolean expression in Q3(b)(i).

(4 marks)

(c) As part of an aircraft's functional monitoring system, a circuit is required to indicate the status of the landing gears prior to landing. A green LED display turns ON if all three gears are properly extended. A red LED display turns on if any of the gears fail to extend. Implement a control circuit to meet this requirement as shown in **Figure Q3(c)**.

(10 marks)

CONFIDENTIAL

BDU10803

Q4 (a) Draw all types of magnetic circuits with their equivalent electric circuit. (5 marks)

- (b) For the series magnetic circuit shown in Figure Q4(b);
 - (i) Calculate the value of current, I required to develop a magnetic flux of $\Phi=4x10-4$ Wb if the magnetic field, H (cast steel) = 170 At/m.

(3 marks)

(ii) Determine the permeability of material, μ under these conditions.

(2 marks)

(c) Explain **THREE** (3) classifications of DC motors with their applications.

(6 marks)

(d) Determine the total dissipated power in three identical coils that contains resistor 100 Ω and inductance 42 mH when connected in a star to a 415 V, 50 Hz, 3-phase supply.

(9 marks)

END OF QUESTIONS -



FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019

COURSE NAME

: ELECTRICAL & ELECTRONIC

TECHNOLOGY

PROGRAMME CODE : BDC/BDM

COURSE CODE : BDU 10803

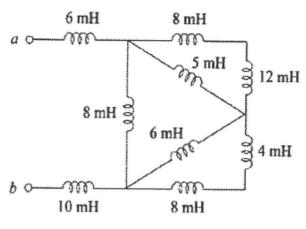


Figure Q1(b)

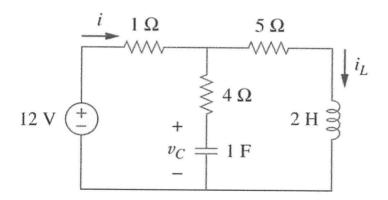


Figure Q1(c)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019

COURSE NAME

: ELECTRICAL & ELECTRONIC

TECHNOLOGY

PROGRAMME CODE : BDC/BDM

COURSE CODE

: BDU 10803

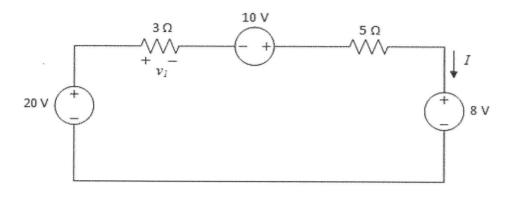


Figure Q1(d)

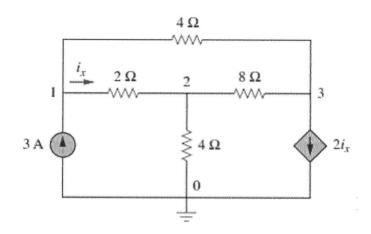


Figure Q1(e)(ii)

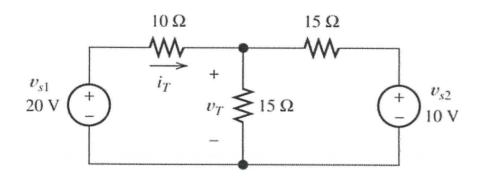


Figure Q2(a)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019

COURSE NAME

: ELECTRICAL & ELECTRONIC

TECHNOLOGY

PROGRAMME CODE : BDC/BDM

COURSE CODE : BDU 10803

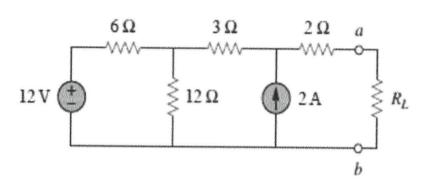


Figure Q2(b)

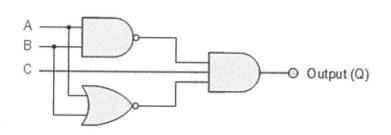


Figure Q3(b)

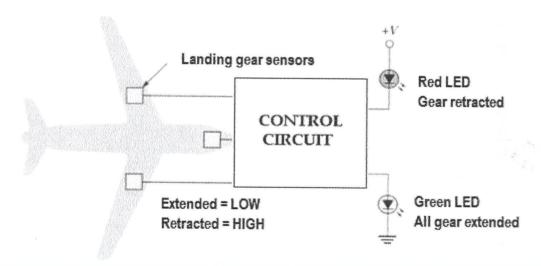


Figure Q3(c)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019

COURSE NAME

: ELECTRICAL & ELECTRONIC

TECHNOLOGY

PROGRAMME CODE : BDC/BDM

COURSE CODE : BDU 10803

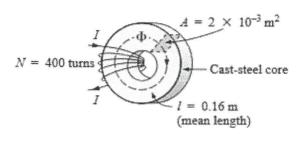


Figure Q4(b)