

CONFIDENTIAL



UTHM
Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2018/2019**

COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY
COURSE CODE : BDA 14303
PROGRAMME CODE : BDD
EXAMINATION DATE : DECEMBER 2018/ JANUARY 2019
DURATION : 3 HOURS
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF TWELVE (12) PAGES

CONFIDENTIAL

TERBUKA

- Q1**
- (a) Explain the definition of terms below in electricity.
- (i) Voltage
 - (ii) Current
- (2 marks)
- (b) Give two (2) examples of DC voltage sources.
- (2 marks)
- (c) The voltage across an electric element is 4V. The energy used by the element is 30 Joules within 5 minutes. Determine the current, I flow through the element.
- (4 marks)
- (d) As shown in **Figure Q1(d)**, calculate the currents I_1 and I_2 that flow in the circuit.
- (5 marks)
- (e) Referring to **Figure Q1(e)**, use the Wye-Delta Transformation to determine the total resistance, R_T and the voltage V_o . Given the source current, I is 5 mA.
- (12marks)
- Q2**
- (a) (i) Explain the steps required to obtain the solution in electric circuits by mesh analysis.
- (4 marks)
- (ii) As shown in **Figure Q2(a)**, use mesh analysis to find the current i_o . Given at node A; $i_1 = i_2 + i_o$.
- (8 marks)
- (b) As shown in **Figure Q2(b)**, a 120Ω resistor (R_1), a 360Ω resistor (R_2) and a 240Ω resistor (R_3) are connected to a 28V voltage source (V_{s1}) and a 12V voltage source (V_{s2}). Using nodal analysis, determine the current flows in R_2 and the power consumption of R_3 .
- (6 marks)
- (c) As shown in **Figure Q2(c)**, a 3Ω resistor (R_1), a 6Ω resistor (R_2) and a 5Ω resistor (R_3) are connected to a 10V voltage source (V_{s1}). Using Thevenin's Theorem calculate the value of V_{th} and the R_{th} of the circuit.
- (7 marks)

- Q3**
- (a) With simple sketches, illustrate how circuits with energy storage elements behave differently than circuits without energy storage elements. (4 marks)
 - (b) Determine the equivalent capacitance and inductance by simplify the circuit in **Figure Q3(b)** to a single inductor and a single capacitor. (6 marks)
 - (c) You need a 3 pF capacitor, but the electronics component store only has 1.8 pF, 4.7 pF and 5.6 pF capacitors. The owner proposed to you a configuration of these capacitors as shown in **Figure Q3(c)**. Will this combination give you the desired value? (5 marks)
 - (d) The switch in the circuit in **Figure Q3(d)** has been closed for a long time. It is opened at $t = 0$. Calculate the capacitor voltage $v(t)$ for $t > 0$. (10 marks)
- Q4**
- (a) Sketch the sin waveform and the cosine waveform for ac voltage and ac current. (4 marks)
 - (b) An AC circuits with 60 Hz voltage of 240V effective value is impressed on an inductance of 0.256 H.
 - (i) Write the time equation for the voltage and the resulting current. Let the zero axis of the voltage wave be at $t=0$. (3 marks)
 - (ii) Sketch the phasor diagram for this circuit (3 marks)
 - (iii) Find the maximum energy stored in the inductance. (3 marks)
 - (c) Consider the circuit as shown in **Figure Q4(c)** with $v(t) = 3 + 6t^2 + 2 \sin 8t$ V .
 - (i) At $t=0$, what will the current $i_R(0)$ in the resistor be? (2 marks)
 - (ii) Write the current equation of $i_R(t)$ (2 marks)
 - (iii) Determine the current equation of $i_C(t)$ (3 marks)

TERBUKA (3 marks)

(iv) With the assumption of $i_L(0) = 9A$, determine the value of $i(t)$ at $t=0$. Write the current equation of $i_L(t)$. (3 marks)

(v) Determine the current equation of $i(t)$. (2 marks)

Q5 (a) (i) With simple sketches, illustrate the working principles of DC motor. (5 marks)

(ii) State three (3) differences between AC and DC motor. (3 marks)

(b) (i) Construct a truth table for the logical functions at the points P, Q and R in the logic diagram of **Figure Q5(b)(i)**. Identify a single logic gate that can be applied to replace the whole circuit. (5 marks)

(ii) Derive the Boolean expression for the logic circuit shown in **Figure Q5(b)(ii)**. (6 marks)

(iii) Construct the logic circuit based on the Boolean expression.

$$Q = (A \cdot B \cdot C) + A \cdot (\bar{B} + \bar{C})$$

(6 marks)

-END OF QUESTIONS -



FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019
COURSE NAME: ELECTRICAL AND ELECTRONIC
TECHNOLOGY

PROGRAMME CODE: BDD
COURSE CODE: BDA 14303

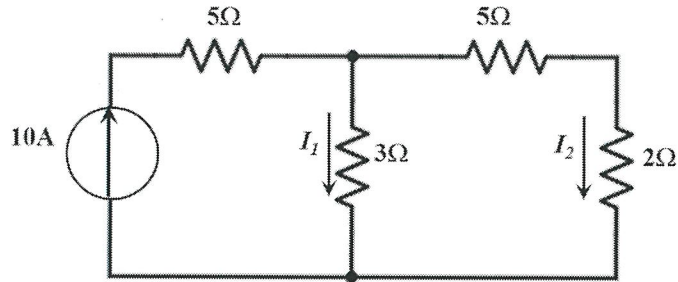


Figure Q1(d)

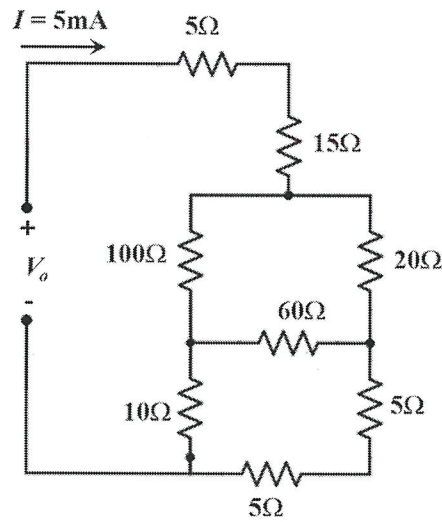


Figure Q1(e)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019
 COURSE NAME: ELECTRICAL AND ELECTRONIC
 TECHNOLOGY

PROGRAMME CODE: BDD
 COURSE CODE: BDA 14303

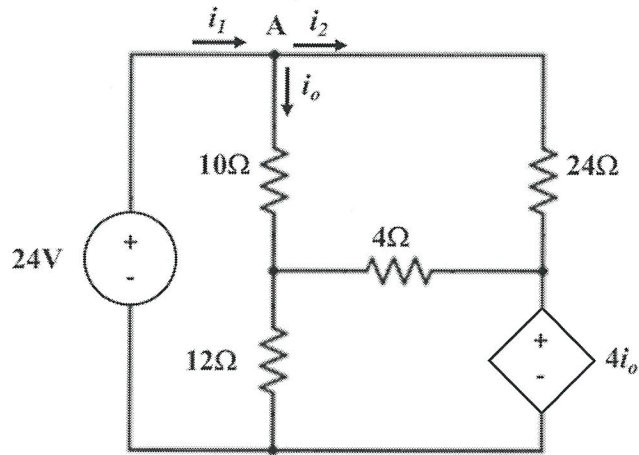


Figure Q2(a)

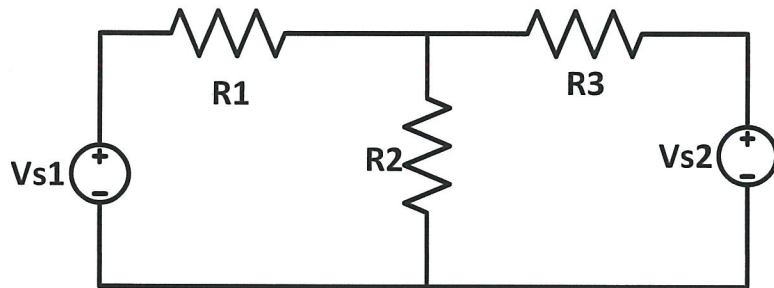


Figure Q2(b)

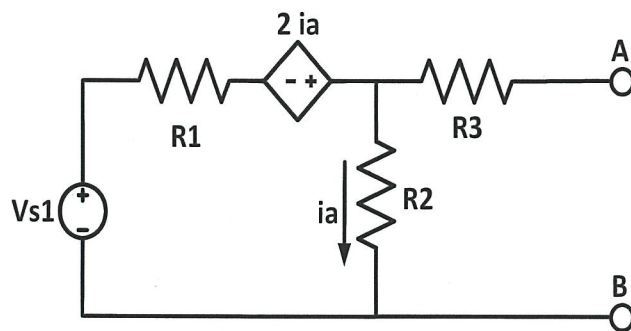


Figure Q2(c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019
COURSE NAME: ELECTRICAL AND ELECTRONIC
TECHNOLOGY

PROGRAMME CODE: BDD
COURSE CODE: BDA 14303

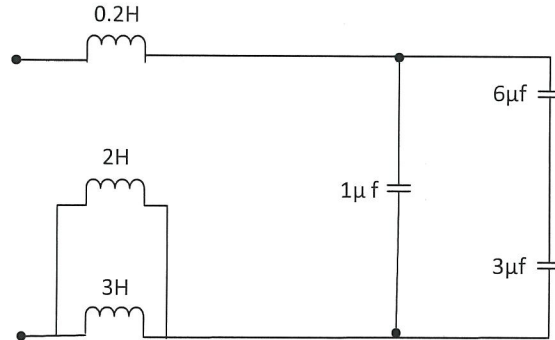


Figure Q3(b)

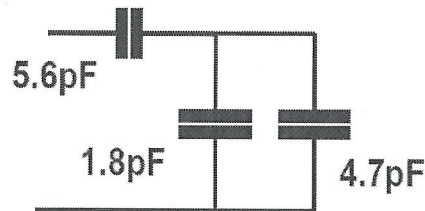


Figure Q3(c)

TERBUKA

CONFIDENTIAL

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019
COURSE NAME: ELECTRICAL AND ELECTRONIC
TECHNOLOGY

PROGRAMME CODE: BDD
COURSE CODE: BDA 14303

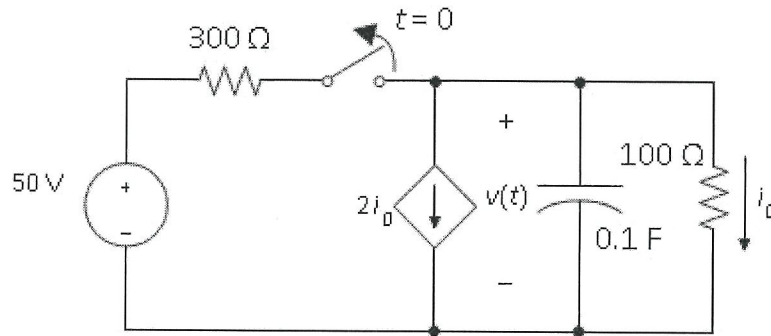


Figure Q3(d)

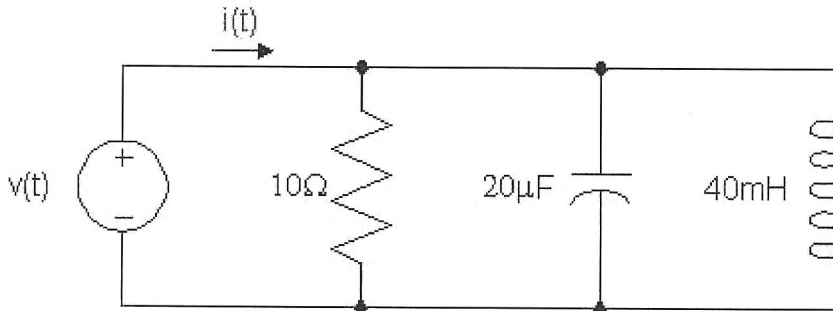


Figure Q4(c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019
COURSE NAME: ELECTRICAL AND ELECTRONIC
TECHNOLOGY

PROGRAMME CODE: BDD
COURSE CODE: BDA 14303

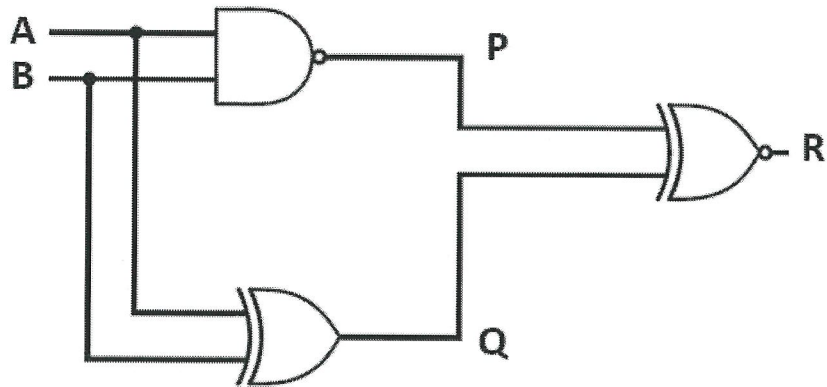


Figure Q5(b)(i)

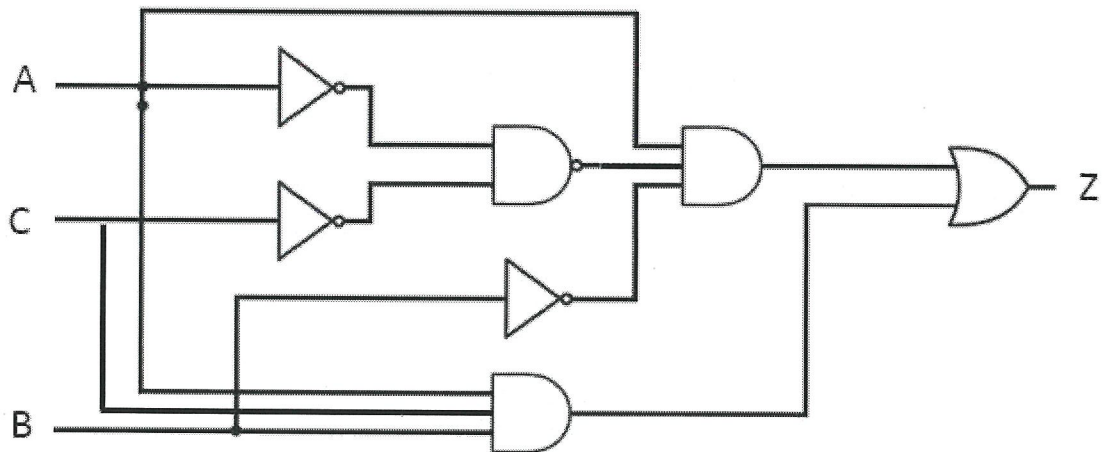


Figure Q5(b)(ii)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019
 COURSE NAME: ELECTRICAL AND ELECTRONIC
 TECHNOLOGY

PROGRAMME CODE: BDD
 COURSE CODE: BDA 14303

LIST OF FORMULA

OHMS LAW

$$V = IR$$

JOULE'S LAW


$$P = IV$$

KIRCHHOFF LAW

$$\sum_{k=1}^n i_k = 0$$

$$\sum_{v=1}^n v_k = 0$$

WYE-DELTA TRANSFORMATION

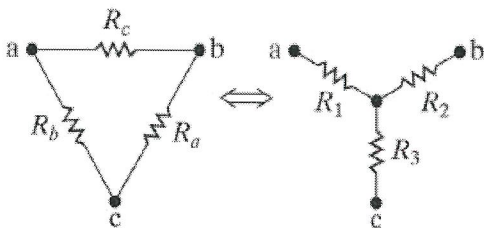

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

SOURCE TRANSFORMATION

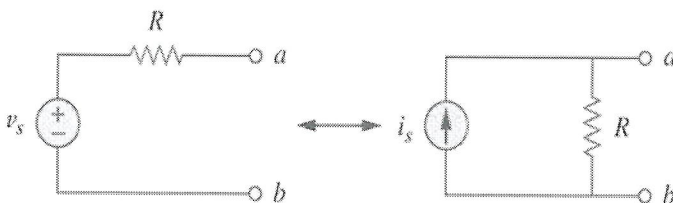

$$V_s = I_s R$$

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019
 COURSE NAME: ELECTRICAL AND ELECTRONIC

PROGRAMME CODE: BDD
 COURSE CODE: BDA 14303

THEVENIN AND NORTON EQUIVALENT CIRCUIT

$$R_{TH} = R_N$$

$$I_N = \frac{V_{TH}}{R_{TH}}$$


$$P = i^2 R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

When $R_L \neq R_{TH}$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

When $R_L = R_{TH}$

MAXIMUM POWER TRANSFER

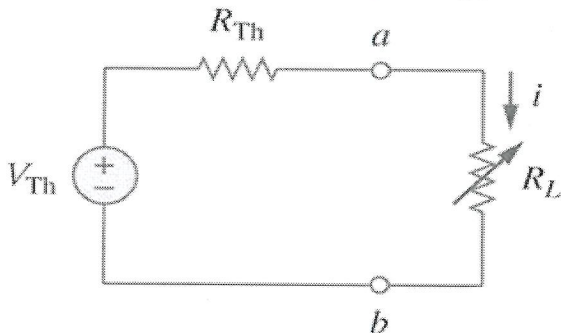

$$P = i^2 R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

CAPACITOR AND INDUCTOR

$$C = \frac{\epsilon A}{d}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt + v(t_0)$$

$$i = C \frac{dv}{dt}$$

$$w = \frac{1}{2} C v^2$$

$$L = \frac{N^2 \mu A}{l}$$

$$v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$w = \frac{1}{2} L i^2$$

$$\tau = RC$$

$$\tau = \frac{L}{R}$$

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019
 COURSE NAME: ELECTRICAL AND ELECTRONIC

PROGRAMME CODE: BDD
 COURSE CODE: BDA 14303

PHASOR REALTIONSHIP

$$v(t+T) = v(t)$$

$$f = \frac{1}{T}$$

$$z = x + jy = r\angle\phi = r(\cos\phi + j\sin\phi)$$

ALTERNATING CURRENT POWER CALCULATION

$$P(t) = v(t)i(t)$$

Instantaneous power

$$P = \frac{1}{2} \operatorname{Re}[VI^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Average power

$$i_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$P_{RMS} = I_{RMS}^2 R = \frac{V_{RMS}^2}{R}$$

TRANSFORMERS

$$\frac{V_P}{V_S} = \frac{N_P}{N_S}$$

LOGIC GATES

Name	NOT	AND	NAND	OR	NOR	XOR	XNOR																																																																																																
Alg. Expr.	\bar{A}	AB	\overline{AB}	$A+B$	$\overline{A+B}$	$A\oplus B$	$\overline{A\oplus B}$																																																																																																
Symbol																																																																																																							
Truth Table	<table border="1"> <tr><th>A</th><th>X</th></tr> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </table>	A	X	0	1	1	0	<table border="1"> <tr><th>B</th><th>A</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	B	A	X	0	0	0	0	1	0	1	0	0	1	1	1	<table border="1"> <tr><th>B</th><th>A</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	B	A	X	0	0	1	0	1	1	1	0	1	1	1	0	<table border="1"> <tr><th>B</th><th>A</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	B	A	X	0	0	0	0	1	1	1	0	1	1	1	1	<table border="1"> <tr><th>B</th><th>A</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	B	A	X	0	0	1	0	1	0	1	0	0	1	1	0	<table border="1"> <tr><th>B</th><th>A</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	B	A	X	0	0	0	0	1	1	1	0	1	1	1	0	<table border="1"> <tr><th>B</th><th>A</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	B	A	X	0	0	1	0	1	0	1	0	0	1	1	1
A	X																																																																																																						
0	1																																																																																																						
1	0																																																																																																						
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	1																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	1																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	1																																																																																																					

TERBUKA

TERBUKA