



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2016/2017**

COURSE NAME : ELECTRICAL MACHINE
COURSE CODE : BBV 30203
PROGRAMME CODE : BBE
EXAMINATION DATE : JUNE 2017
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF **THREE (3)** PAGES

- Q1**
- (a) By using a suitable diagram, explain how a DC voltage is generated from a DC generator. (7 marks)
- (b) Describe the function of the following parts in electrical machinery (8 marks)
- (i) rotor
 - (ii) stator
 - (iii) brush
 - (iv) commutator
- (c) A DC shunt generator supplies a 16 kW load at 220 V through cable of resistance, $R = 100 \text{ m}\Omega$. If the field winding resistance $R_f = 60 \text{ }\Omega$ and the armature resistance, $R_a = 40 \text{ m}\Omega$, determine (10 marks)
- (i) the terminal voltage
 - (ii) generated e.m.f in the armature
- Q2**
- (a) Draw and label the equivalent circuit of DC motor listed below (6 marks)
- (i) shunt-wound motor
 - (ii) series-wound motor
 - (iii) compound-wound motor
- (b) A 240 V shunt motor takes a total current of 30 A. If the field winding resistance $R_f = 150 \text{ }\Omega$ and the armature resistance $R_a = 0.3 \text{ }\Omega$, determine (9 marks)
- (i) the armature current
 - (ii) back e.m.f
 - (iii) maximum efficiency of the motor
- (c) A separately excited DC generator is connected to a $50 \text{ }\Omega$ load and a current of 8 A flows. The armature resistance is $0.8 \text{ }\Omega$ and the excitor voltage is 240 V. Calculate (10 marks)
- (i) the terminal voltage
 - (ii) the generated e.m.f

TERBUKA

- Q3** (a) Describe type of losses below
- (i) copper loss
 - (ii) iron loss
 - (iii) windage loss
 - (iv) friction loss
- (8 marks)
- (b) A synchronous generator with 4 poles is attached to prime mover. Determine the speed of the generator in order to produce a voltage with frequency of
- (i) 50 Hz
 - (ii) 60 Hz
- (4 marks)
- (c) Explain the advantages of AC generator compared with DC generator.
- (5 marks)
- (d) For the large AC three phase generator, it is more practical to rotate the magnetic field and fix armature winding. By using a suitable diagram, explain how the three phase AC voltage is generated by the large three phase generator.
- (8 marks)
- Q4** (a) By using a suitable diagram, explain the stage of losses for an induction motor.
- (7 marks)
- (b) A three phase squirrel cage induction motor with 4 poles running 1460 rpm at full load. If the motor supplied by 415 V / 50 Hz, determine
- (i) synchronous speed
 - (ii) slip percentage
- (6 marks)
- (c) A six (6)-pole three phase, 400 V / 60 Hz induction motor rotate at 1140 rpm. The motor power input is 40 kW and the stator losses is 1 kW. If the windage and friction losses is 2 kW, determine
- (i) slip
 - (ii) rotor copper losses
 - (iii) mechanical output power
 - (iv) efficiency
- (12 marks)

TERBUKA

- END OF QUESTIONS -