

CONFIDENTIAL



UTHM
Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2017/2018**

COURSE NAME : ELECTRICAL MACHINE
COURSE CODE : BBV 30203
PROGRAMME CODE : BBE
EXAMINATION DATE : DECEMBER 2017/JANUARY 2018
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF **FOUR(4)** PAGES

CONFIDENTIAL

Q1 (a) Describe types of losses below

- (i) Copper loss
- (ii) Iron loss
- (iii) Windage loss
- (iv) Friction loss

(8 marks)

(b) A separately excited DC generator is connected to a 50Ω load and a current of 8 A flows. If the armature resistance is 0.8Ω . The excitor voltage is 240 V

- (i) draw and label the equivalent of this generator
- (ii) state the equation for the equivalent circuit of the DC generator
- (iii) calculate the terminal voltage
- (iv) calculate the generated EMF

(12 marks)

Q2 (a) Describe why an induction motor have a lagging power factor.

(3 marks)

(b) By using a suitable diagram explain the stage of losses for an induction motor.

(5 marks)

(c) A six(6)-pole three phase, 415 V, 50 Hz induction motor rotate at 940 rpm at 0.8 lagging power factor. Stator losses is 1 kW and windage and friction losses is 2 kW. Determine

- (i) slip
- (ii) rotor copper losses
- (iii) mechanical output power
- (iv) efficiency

(12 marks)

TERBUKA

- Q3** (a) Draw and label the equivalent circuit of DC motor listed below:
- (i) shunt-wound motor.
 - (ii) series-wound motor.
 - (iii) compound wound motor.
- (6 marks)
- (b) Explain how reversal of rotation can be made for shunt wound DC motor.
- (4 marks)
- (c) A 240 V shunt motor takes a total current of 30 A. If the field winding resistance $R_f = 150 \Omega$ and the armature resistance $R_a = 0.3 \Omega$, determine
- (i) the armature current.
 - (ii) back EMF.
 - (iii) efficiency of the motor.
- (10 marks)
-
- Q4** (a) Define what is a generator
- (2 marks)
- (b) By using a suitable diagram, explain how single phase AC voltage is generated form AC generator
- (4 marks)
- (c) For the large AC three phase generator, it is more practical to rotate the magnetic field and fix armature winding. By using a suitable diagram, explain how the three phase AC voltage is generated by the large three phase generator
- (8 marks)
- (d) A synchronous generator with four (4) poles is attached to prime mover. Determine the speed of generator in order to produce a voltage with frequency of
- i) 50 Hz
 - ii) 60 Hz
- (6 marks)



- Q5** (a) List down two (2) types of single phase induction motor (3 marks)
- (b) Draw the equivalent circuit for two types of single phase induction motor in question Q5 (a) (4 marks)
- (c) Induction motor is a great invention in history of electrical machine evolution. Describe three (3) advantages of induction motor (3 marks)
- (d) The power supplied to a three-phase induction motor is 40 kW and the stator losses are 1200 W. If the slip is 5%, determine (10 marks)
- (i) the rotor copper loss
 - (ii) the total mechanical power developed by the rotor
 - (iii) the output power of the motor if friction and windage losses are 750 W
 - (iv) the efficiency of the motor, neglecting rotor copper loss

- END OF QUESTIONS -

TERBUKA