

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2013/2014**

COURSE NAME : DIGITAL ELECTRONICS
COURSE CODE : DAR 21303
PROGRAMME : 2 DAR
EXAMINATION DATE : DECEMBER 2013/JANUARY 2014
DURATION : 2 ½ HOURS
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

CONFIDENTIAL

- Q1** (a) Perform the following arithmetic operations. Check the answer with its decimal equivalent.
- (i) $1101_2 + 0101_2 + 1011_2$
 - (ii) $10011010_2 + 00101011_2$
 - (iii) $+26_{10} - 35_{10}$ using 2's complement
- (7 marks)
- (b) A full adder has three (3) inputs: A, B and C_{in} and two (2) outputs: SUM and C_{out} .
- (i) Produce a truth table for the full adder.
 - (ii) Obtain the minimum Boolean expression for SUM by using Boolean algebra rules and Karnaugh map for C_{out} .
 - (iii) Draw the simplified circuit for the full adder.
- (15 marks)
- (c) Convert 285_{10} to hexadecimal.
- (3 marks)
- Q2** (a) Explain the importance of Boolean theorems in digital systems and write four (4) examples of Boolean algebra rules.
- (4 marks)
- (b) Simplify the following Boolean expression using Boolean algebra and verify the result using a Karnaugh map.
- $$Z = AB + A\bar{B}C + AB\bar{C}$$
- (7 marks)
- (c) The logic circuit in **Figure Q2(c)** has inputs A, B, C.
- (i) Write the expression for the outputs X, Y and F.
 - (ii) Build a truth table for the logic circuit.
 - (iii) Sketch the timing diagram for waveforms at X, Y and F if the inputs A, B and C are as shown in **Figure Q2(c)(iii)**.
- (14 marks)

- Q3** (a) For the following Boolean expressions:
- (i) Obtain the minimum sum of product (SOP) expression by using a Karnaugh map.
 - (ii) Implement the simplified expression using basic logic gates.
- $$f(A, B, C, D) = \sum m(0, 2, 7, 8, 9) + d(4, 5, 10, 14)$$
- (9 marks)

- (b) An automobile has digital sensors with the following logic states:
 Key: 0 – Not in ignition, 1 – In ignition
 Door: 0 – Open, 1 – Closed
 Lights: 0 – OFF, 1 – ON.
 An alarm signal will sound the buzzer for the following conditions:
- The key is in the ignition and the door is open
 - The key is not in the ignition and the lights are on
- Design this automobile alarm system.
- (i) Obtain the truth table of the circuit.
 - (ii) Simplify the output function.
 - (iii) Draw the simplified logic diagram of this circuit using NAND gates only.
- (16 marks)

- Q4** (a) Briefly describe the difference between a decoder and an encoder.
 (4 marks)
- (b) A 2-input Multiplexer circuit whose output (Y) is equivalent to one of two possible data inputs (A or B). A control input (S) selects either the data on A input (if S is low) or data on the B input (if S is high) to be routed to the output (Y) line. Do the following:
- (i) Draw the block diagram of this multiplexer circuit showing all inputs and output.
 - (ii) Build the truth table and write the Boolean expression for the output function.
 - (iii) Simplify the output function using K-map and implement the simplified function using NAND gates only.
- (11 marks)

- (c) Use the 74138 IC in **Figure Q4(d)** to implement the following function:
- (i) $F(A, B, C) = AB + C$
 - (ii) $W(X, Y, Z) = \overline{X}\overline{Y} + \overline{Y}Z + XY\overline{Z}$
- (10 marks)

- Q5** (a) **Figure Q5(a)(i)** shows a clocked RS flip flop and **Figure Q5(a)(ii)** shows waveforms applied to the circuit:
- (i) Construct the truth table
 - (ii) Draw the output waveform Q.
- (6 marks)
- (b) Show how to create the following flip-flops from JK flip-flop:
- (i) D flip-flop
 - (ii) T flip-flop
- (4 marks)
- (c) State TWO(2) differences between synchronous and asynchronous counters.
- (4 marks)
- (d) For the counter circuit in **Figure Q5(d)**
- (i) Draw the timing diagram for the 4-bit counter.
 - (ii) Determine its counting sequence.
 - (iii) Determine the frequency of each output (A,B,C,D) if the clock frequency is 1 kHz.
 - (iv) Explain its operation.
- (11 marks)
- Q6** (a) The 4-bit serial input register in **Figure Q6(a)** has 1101 (Q,R,S,T) stored in it and data inputs are low. Show the register operations for four clock transitions by doing the following:
- (i) Draw a table showing the state sequence
 - (ii) Draw the timing diagram.
- (10 marks)
- (b) Briefly explain two (2) essential differences between analog and digital signals.
- (3 marks)
- (c) Two conversions are necessary to interface real world, analog signals with a digital circuit. Name and describe briefly the function of the two circuits used.
- (4 marks)
- (d) The circuit in **Figure Q6(d)(i)** is used in digital and analog interface. What

is the purpose of this circuit? Determine the output V_{out} and record its value in **Table Q6(d)** if the waveform representing a sequence of 4-bit numbers ($D_3 D_2 D_1 D_0$) in **Figure Q6(d)(ii)** is applied to the inputs.
(8 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2013/2014
 COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : 2DAR
 COURSE CODE: DAR 21303

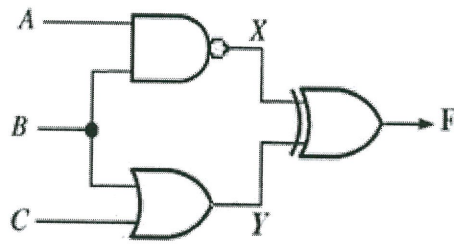


FIGURE Q2(c)

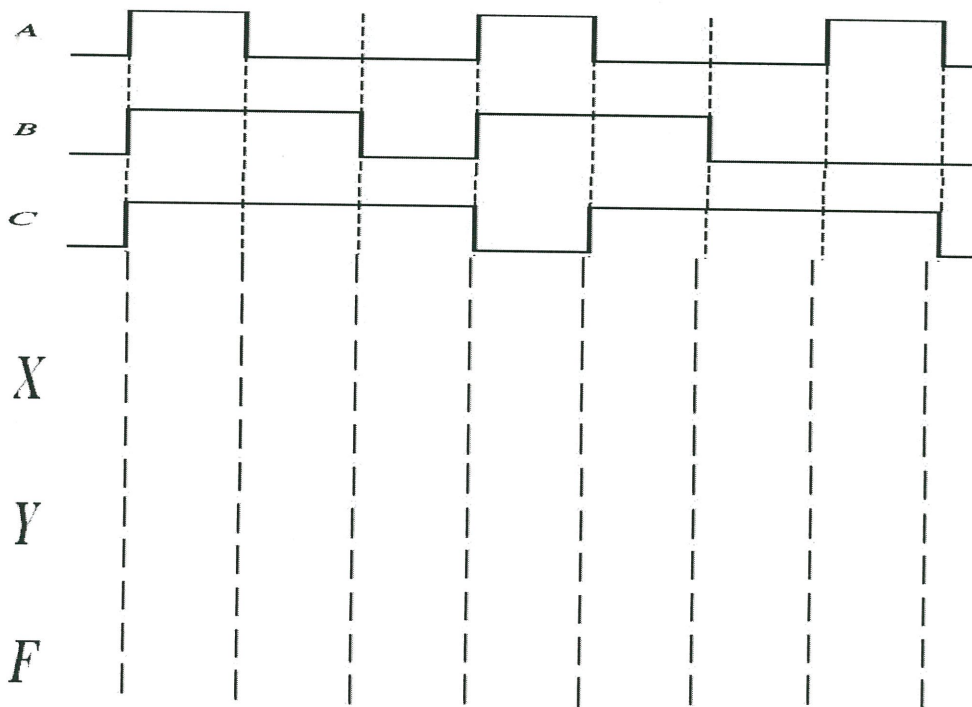


FIGURE Q2(c)(iii)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2013/2014
 COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : 2DAR
 COURSE CODE: DAR 21303

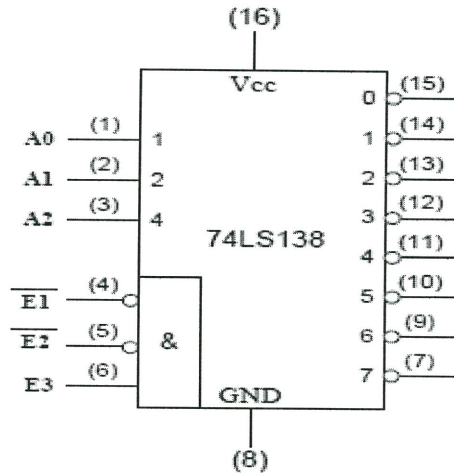


FIGURE Q4(d)

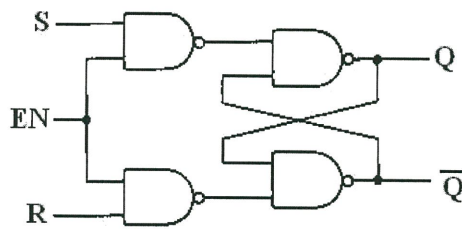


FIGURE Q5(a)(i)


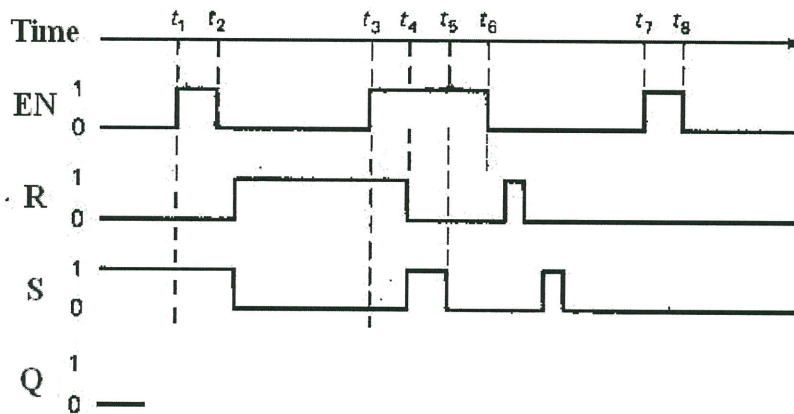


FIGURE Q5(a)(ii)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2013/2014
 COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : 2DAR
 COURSE CODE: DAR 21303

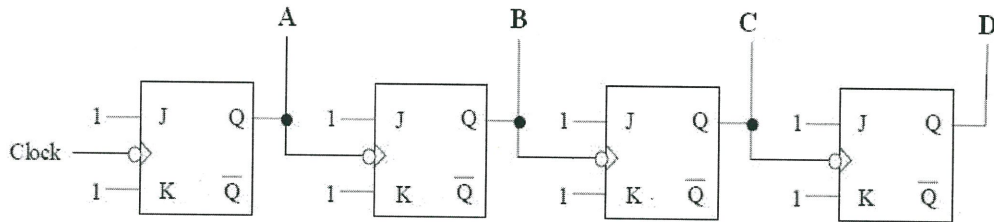

Timing diagram

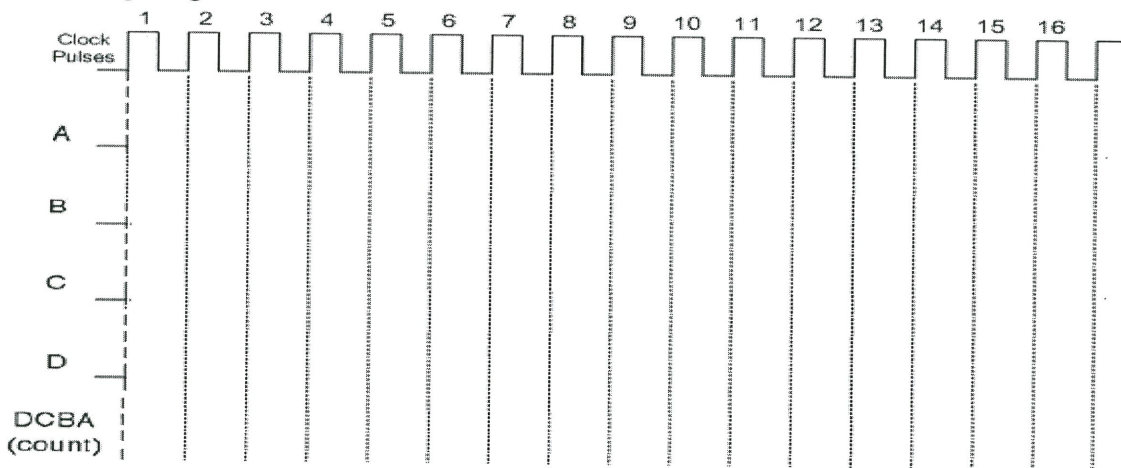


FIGURE Q5(d)

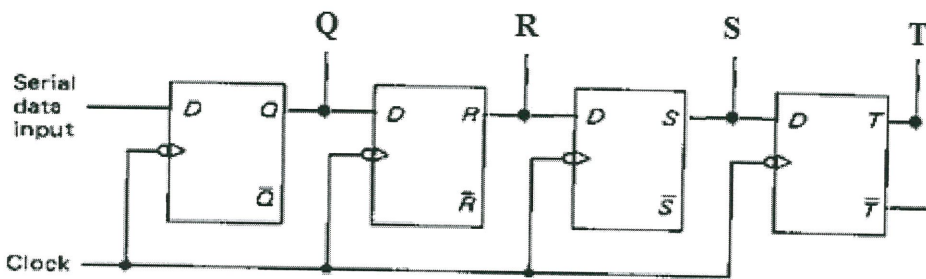


FIGURE Q6(a)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2013/2014
 COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : 2DAR
 COURSE CODE: DAR 21303


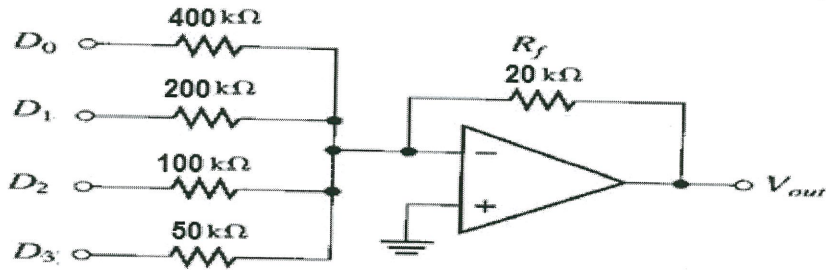


FIGURE Q6(d)(i)

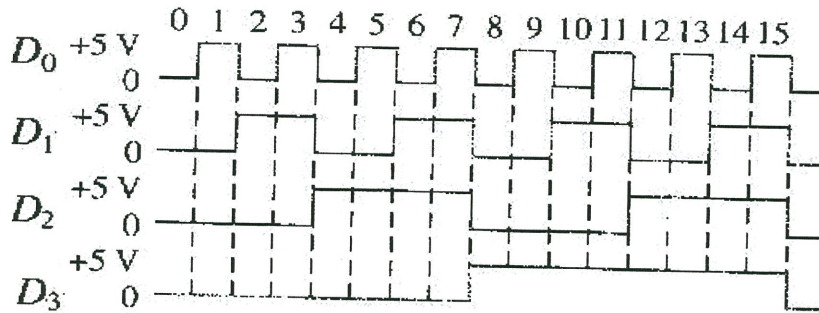

(b)

FIGURE Q6(d)(ii)

Table Q6

D_3	D_2	D_1	D_0	V_{out} (V)
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	