

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION **SEMESTER I SESSION 2013/2014**

COURSE NAME

ELECTRICAL MEASUREMENT

AND INSTRUMENTATION

COURSE CODE

: DAE 21402

PROGRAMME

: 2 DAE

EXAMINATION DATE : DECEMBER 2013/JANUARY 2014

DURATION

: 2½ HOURS

INSTRUCTION

: ANSWER FOUR (4) QUESTIONS

ONLY

THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES

CONFIDENTIAL

Q1 (a) Describe the difference between accuracy and precision.

(3 marks)

(b) The output of an amplifier was measured by 10 different students using the same analog votmeter with the following results:

36.3 V 34.2 V 35.3 V 33.1 V 39.0 V 38.4 V 32.6 V 35.5 V 35.3 V 33.8 V

- (i) Calculate the precision of each measuremnet and hence state the most precise measurement.
- (ii) Determine the arithmetic mean and the standard deviation of the readings.

(8 marks)

(c) Draw and label the block diagram of an electronic measuring system and give the function of each component in that system.

(8 marks)

(d) A 0-150 V voltmeter has a guaranteed accuracy of 1 percent of full scale reading. The voltage measured by this instrument is 75 V. Calculate the limiting error in percent. Comment on the result.

(6 marks)

Q2 (a) State three(3) differences between analog and digital multimeters.

(3 marks)

- (b) Given a PMMC meter movemnet with a full scale deflection current of 100 uA and internal resistance of 2 k Ω . Design and draw the schematic circuit of the following meters with this meter.
 - (i) A 0-5 V and 0 10 V multirange DC voltmeter.
 - (ii) A 0-25 mA and 0-0.25 A multirange ammeter.
 - (iii) A full wave AC voltmeter with a range of 0 10 Vrms.

(16 marks)

(c) Figure **Q2(c)** shows the block diagram of a Thermocouple temperature measuring system. Describe how this measuring system operates.

(6 marks)

- Q3 (a) Define sensitivity rating of a measuring instrument and give its unit.
 (3 marks)
 - (b) Two voltmeters with different sensitivity but same range of $0-10~\rm V$ is used to measure the voltage across resistor $10~\rm k\Omega$ in the circuit of **Figure Q3(b)**. Redraw the circuit showing how the voltmeter is connected. Find the % error due to voltmeter loading effect if the following meters are used and compare the two results:
 - (i) Voltmeter (range 0 10 V) with sensitivity of $4 \text{ k}\Omega/\text{V}$
 - (ii) Voltmeter (range 0 10 V) with sensitivity of 1 k Ω /V (8 marks)
 - (c) Design and draw an ohmmeter with a PMMC meter movement having a full scale current of 0.1 mA and internal resistance of 1 k Ω using a 10 V battery.

(6 marks)

- (d) For the circuit in **Figure Q3(d)**, an ammeter having an internal resistance of 2 Ω is used to measure the current in the 5 Ω resistor.
 - (i) Redraw the circuit to show the ammeter connections.
 - (ii) Calculate the percent error of the reading due to ammeter insertion. (8 marks)
- Q4 (a) There are many special forms of the bridge circuit. With the aid of simple bridge diagram, identify at least four (4) commonly used bridges.

 (8 marks)
 - (b) From the circuit in **Figure Q4(b)**, analyze the circuit mathematically to produce an equation of unknown resistance, R_4 , when the bridge is balance.

(7 marks)

(c) An AC bridge is balanced at 1000 Hz and has the following constants:

Arm $AB - 0.2 \mu F$ pure capacitance

Arm BC - 500 Ω pure resistance

Arm CD - unknown

Arm $DA - R = 300 \Omega$ in parallel with $C = 0.1 \mu F$

The supply is connected between A and C and the detector is between D and B. Find the R and C or L constants of arm CD, considered as a series circuit.

(10 marks)

Q5 Describe the four(4) basic control functions of an oscilloscope. (a)

(8 marks)

- (b) Figure Q5(b) shows a trace on the screen of an oscilloscope. The Ysensitivity of the oscilloscope is set at 5.0 V per division and the time base is set at 0.50 ms per division. For the trace, determine
 - (i) the maximum positive value of potential difference,
 - (ii) the maximum negative value of potential difference,
 - the frequency of the signal. (iii)

(5 marks)

(c) A Lissajous pattern on an oscilloscope is stationary and has 5 horizontal tangencies and 2 vertical tangencies. The frequency of horizontal input is 1000 Hz. Determine the frequency of vertical input.

(3 marks)

(d) What is a signal generator?

(3 marks)

(e) Name two(2) types of signal generator and describe its difference.

(6 marks)

- **Q6** (a) Name and describe (with the help of diagrams) a sensor used to measure the following quantity:
 - Light (i)
 - (ii) Temperature
 - (iii) Sound

(9 marks)

(b) State the function of transducer and explain its importance in electronic measurements.

(3 marks)

- The circuit in Figure Q6(c)(i) is to be used for temperature measurement. (c) A "15 k Ω " thermistor (**Figure Q6(c)(ii)**) is used. The meter is a 2-mA ammeter with a resistance of 1800 Ω . R_C is set to 8 $k\Omega$ and the supply voltage V_T is 10 V. What will be the meter readings at 50 °F and at 300°F?
- (d) A strain gauge having a gauge factor of 4 is used in testing a machine. If the gauge resistance is 90 Ω and the strain is 2 x 10⁻⁵, how much will the resistance of the strain gauge change?

(4 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2013/2014

COURSE NAME

: ELECTRICAL MEASUREMENT

AND INSTRUMENTATION

PROGRAMME: 2 DAE COURSE CODE: DAE 21402



FIGURE Q2(c)

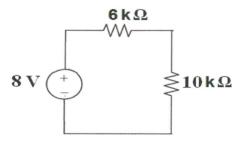


FIGURE Q3(b)

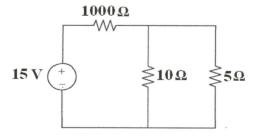


FIGURE Q3(d)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2013/2014

COURSE NAME : ELECTRICAL MEASUREMENT

AND INSTRUMENTATION

PROGRAMME: 2 DAE COURSE CODE: DAE 21402

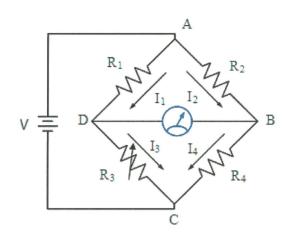


FIGURE Q4(b)

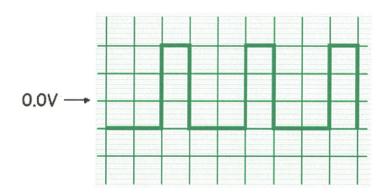


FIGURE Q5(b)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2013/2014

COURSE NAME : ELECTR

: ELECTRICAL MEASUREMENT AND INSTRUMENTATION

PROGRAMME: 2 DAE COURSE CODE: DAE 21402

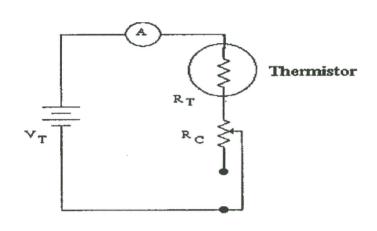


FIGURE 6(c)(i)

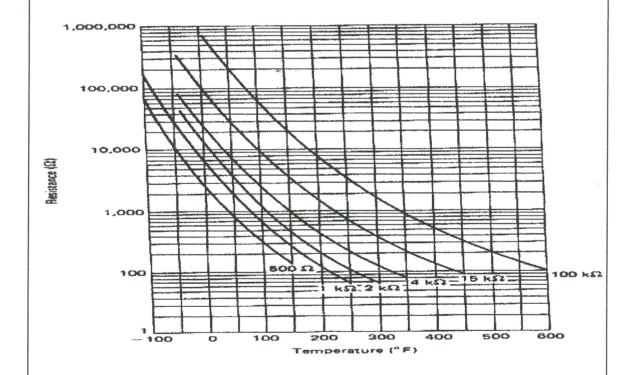


FIGURE 6(c)(ii)